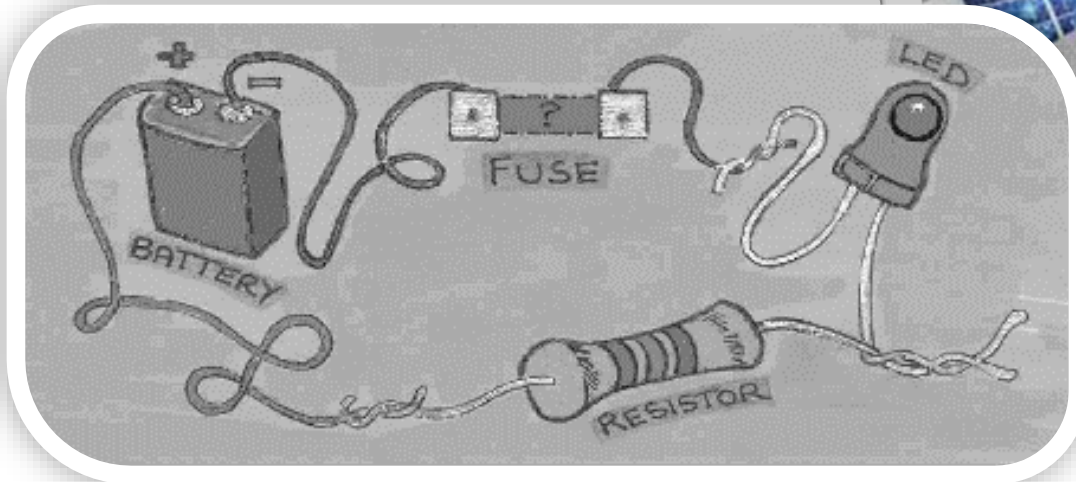


EHB222E QUESTIONS

4th week



A p-n diode is modeled with the exponential model. The diode currents are measured 1.36 mA and 7.20 mA when 0.7 V and 0.75 V applied, respectively. Determine the saturation current I_S and the emission factor n (from nV_T). Suppose that $V_T = 25$ mV.

($V_T = 25$ mV alınız)

Çözüm: $I_D = I_S (e^{\frac{V_D}{nV_T}} - 1)$ olmak üzere iletim durumunda $e^{\frac{V_D}{nV_T}} \gg 1$
kabul edersek $I_D \cong I_S \cdot e^{\frac{V_D}{nV_T}}$ olur. Buna göre;

$$\left. \begin{array}{l} I_{D1} = I_S \cdot e^{\frac{V_{D1}}{nV_T}} \\ I_{D2} = I_S \cdot e^{\frac{V_{D2}}{nV_T}} \end{array} \right\} \frac{I_{D2}}{I_{D1}} = e^{\frac{V_{D2} - V_{D1}}{nV_T}} \Rightarrow \ln\left(\frac{I_{D2}}{I_{D1}}\right) = \frac{V_{D2} - V_{D1}}{nV_T}$$

$$\Rightarrow nV_T = \frac{V_{D2} - V_{D1}}{\ln\left(\frac{I_{D2}}{I_{D1}}\right)} \Rightarrow n = \frac{V_{D2} - V_{D1}}{V_T \ln(I_{D2}/I_{D1})} = \frac{0.75 - 0.7}{25 \times 10^{-3} \times \ln(7.20/1.36)}$$


$= 1.2$ olarak bulunur.

$$I_S = \frac{I_D}{e^{\frac{V_D}{nV_T}} - 1} = \frac{7.2 \text{ mA}}{e^{\frac{0.75 \text{ V}}{1.2 \times 25 \text{ mV}}} - 1} \cong 10^{-13} \text{ A} \text{ olarak bulunur}$$

↪ yine ihmal edilebilir !

İhmal yaptıktan sonra geri dönüp bulunan sonuç ile tutarlı bir ihmal mi kontrol etmek gerekir !

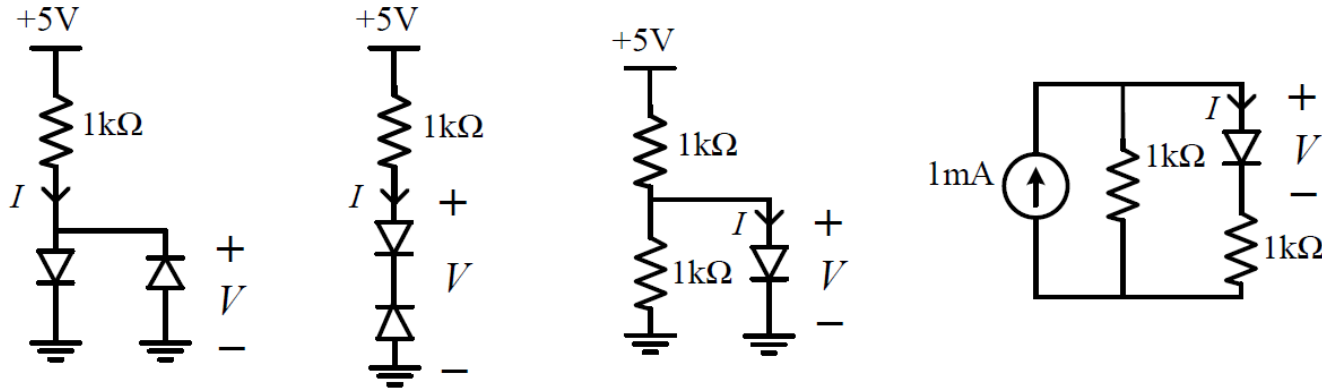Find the values of I and V for the circuits shown. Use ideal diode model ($V_d=0$) for diodes.



Ans. (a) 5 mA, 0V; (b) 0 mA, 5V; (c) 5 mA, 0V;
(d) 0.5 mA, 0V;

Use a modified ideal model for the Zener diode in Figure 1. The model has 0,7 V forward bias and 2V Zener ($V_Z=2V$) voltage. An input signal, shown in Figure 2, is applied. Sketch V_o , i_{D1} and i_{D2} in time domain. Justify your answer.

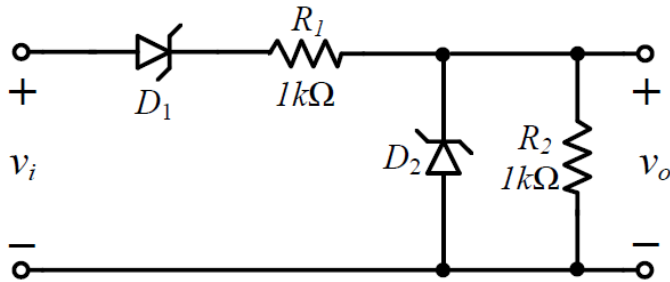


Figure 1



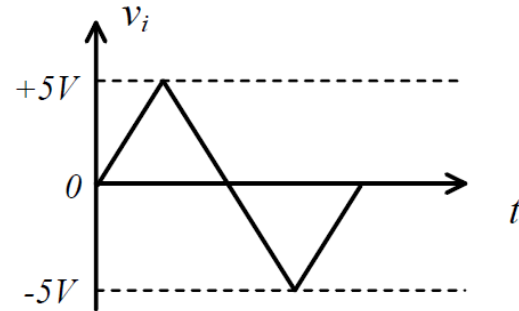
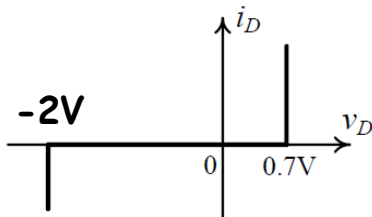
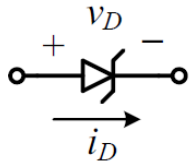


Figure 2

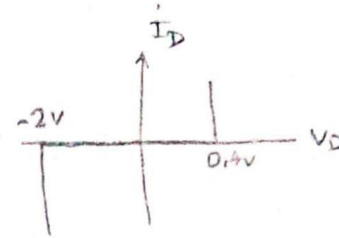

3-

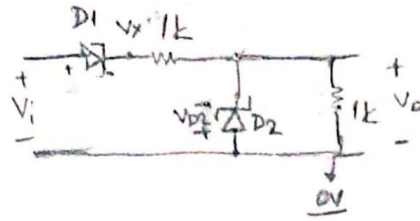

① $V_{D1} = -2V$
 ② $-2V < V_{D1} < 0.7V$

③ $V_{D1} = 0.7V$

1-

$V_{D1} = -2V$ $I_{D1} < 0$

a) $I_{D2} > 0$
 $V_{D2} = 0.7V$

$V_0 = 0 - V_{D2} = -0.7V$

$\frac{0 - V_0}{1k} < \frac{V_0 - V_0}{1k}$

$\frac{0.7V}{1k} < \frac{-0.7 - (V_i + 2V)}{1k}$

$V_i + 2V < -1.4V$

$V_i < -3.4V$

b)

$I_{D2} = 0$
 $V_{D2} < 0.7V$

$V_0 > -0.7V$
 $\frac{0 - V_0}{1k} = \frac{V_0 - (V_i + 2V)}{1k}$

$2V_0 = V_i + 2V$

$V_0 = \frac{V_i + 2V}{2} = \frac{V_i}{2} + 1V$

$\frac{V_i + 2V}{2} > -0.7V$

$V_i > -3.4V$

2

$V_0 = 0V$

$V_i - V_D = 0$

$V_i = V_D$

$-2V < V_i < 0.7V$

2

3-

$$V_D = 0,9V \quad V_X = V_i - 0,9V$$

$$I_{D1} > 0$$

a)

$$V_{D2} > -2V \quad I_{D2} = 0$$

$$V_O < 2V$$

$$\frac{V_i - 0,9V - V_O}{1k} = \frac{V_O}{1k}$$

$$V_i - 0,9V = 2V_O$$

$$\boxed{\frac{V_i - 0,9V}{2} = V_O}$$

$$\frac{V_i - 0,9V}{2} < 2V$$

$$\boxed{V_i < 4,9V}$$

b)


$$\frac{V_{D2} = -2V}{V_O = 2V}$$

$$\frac{V_i - 0,9V - V_O}{1k} > \frac{V_O}{1k}$$

$$\frac{V_i - 0,9V}{2} > V_O$$

$$V_i - 0,9V > 4$$

$$\boxed{V_i > 4,9V}$$

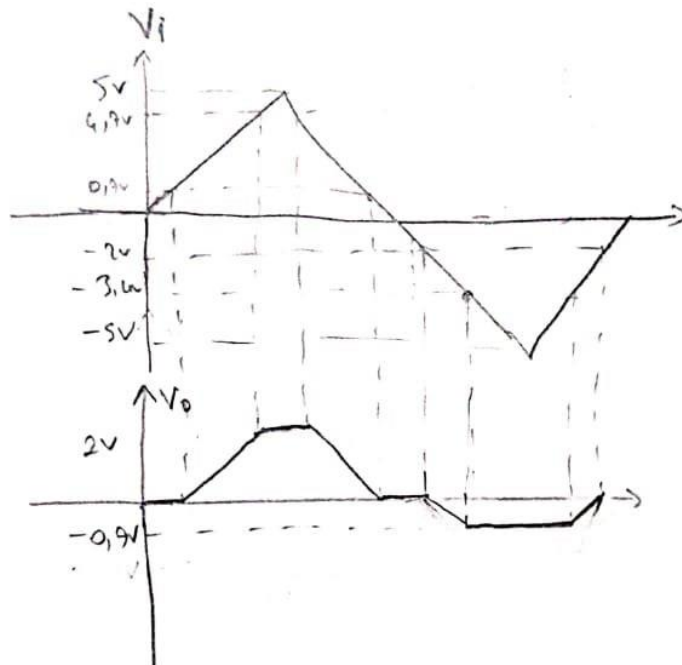

$$-5V < V_i < -3,4V$$

$$-3,4V < V_i < -2V$$

$$-2V < V_i < 0,9V$$


$$0,9V < V_i < 4,9V$$

$$4,9V < V_i < 5V$$

In figure, assume modified diode model ($V_D=0.7V$) for the diodes.

a) Calculate I_{D1} and V_O for $R_1=10\text{ k}\Omega$, $R_2=5\text{ k}\Omega$.

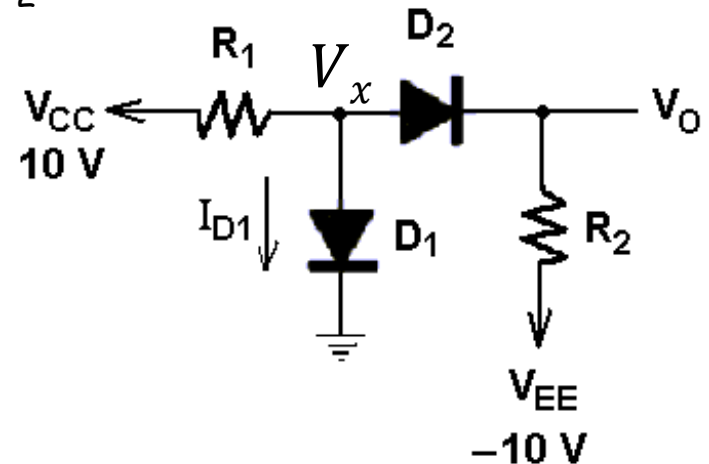b) Calculate I_{D1} and V_O for $R_1=5\text{ k}\Omega$, $R_2=10\text{ k}\Omega$.



D1 ON, D2 OFF

(b) $V_{D2} = V_{D1} - V_{EE} = 10.7V$ (not valid)

D1 OFF, D2 OFF

(b) $V_{D2} = V_{CC} - V_{EE} = 20V$ (not valid)


D1 OFF, D2 ON

(b) $V_{CC} - (R_1 + R_2) I_{D2} - V_{D2} = V_{EE}$

$I_{D2} = (V_{CC} - V_{EE} - V_{D2}) / (R_1 + R_2) = (10 - (-10) - 0.7) / 15k = 12.9mA$ (valid)


$V_x = V_{D1} = -10V + 5k \cdot 12.9mA + 0.7 = -2.86V$ (valid)

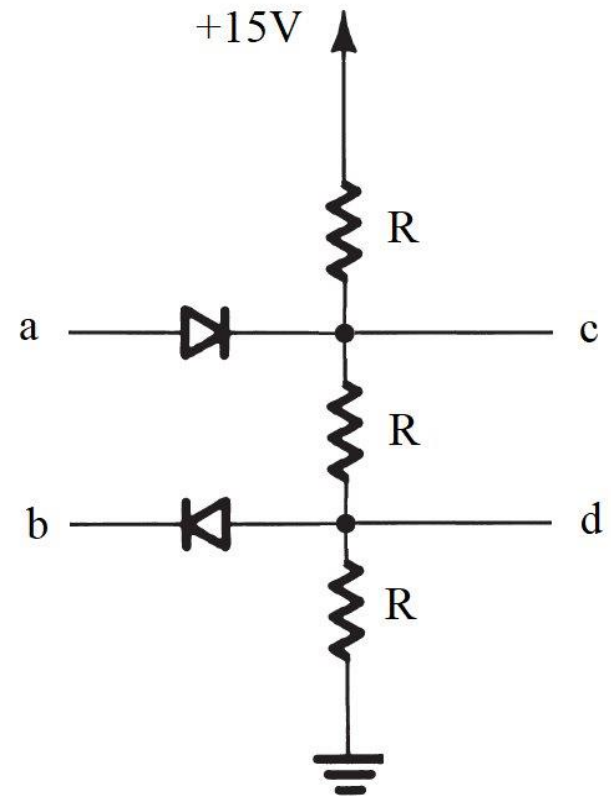In figure, assume ideal diode model ($V_D=0V$) for the diodes. Calculate all possible output voltages. Input voltage (a,b) values are 15V or 0V.




A	B	C	D
0 V	0 V	7,5 V	0 V
0 V	15 V	10 V	5 V
15 V	0 V	15 V	0 V
15 V	15 V	15 V	7,5 V

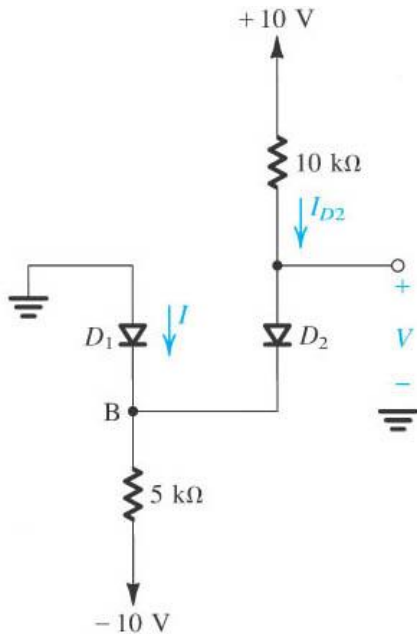In figure, assume modified ideal diode model ($V_D=0.7V$) for the diodes. Calculate output voltage.



(a)

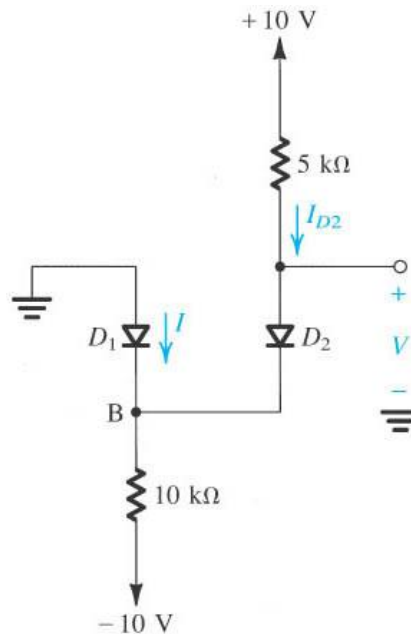

(b)

$D1$ ON, $D2$ OFF

(b) $V_{D2} = 10V - (-V_{D1}) = 10.7V$ (not valid)

$D1$ OFF, $D2$ OFF


(b) $V_{D2} = 10 - (-10) = 20V$ (not valid)


$D1$ OFF, $D2$ ON

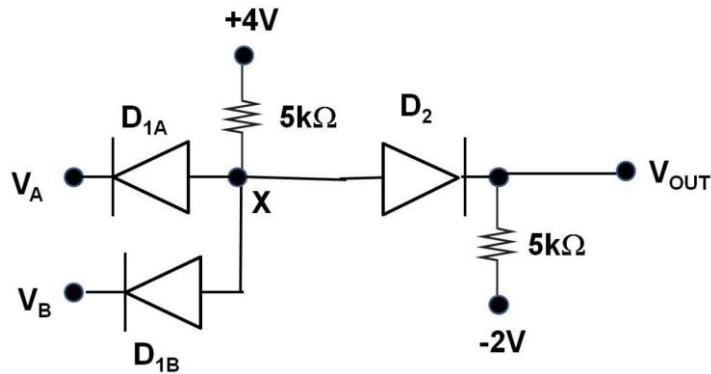(b) $10V - 15k I_{D2} - V_{D2} = -10V$, $I_{D2} = 1.28mA$ (valid)

$V_B = -V_{D1} = -10V + 10k \cdot 1.28mA = 2.8V$ (valid)

All PN diodes shown below have a voltage drop of 0.6V when they are "ON". Calculate output voltage with the given values ($V_a=4\text{V}$, $V_b=3\text{V}$).



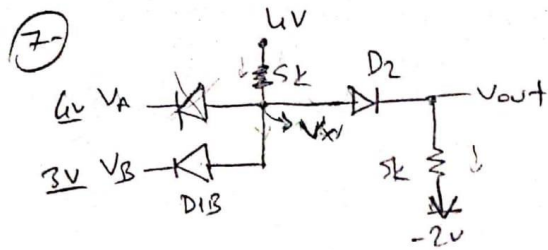

D1B on, D2 on

$$V_x = 3.6V$$

$$V_{out} = 3V$$

$$\frac{4 - 3.6}{5k} = 0.08 \mu A$$

$$\frac{3V - (-2V)}{5k} = \frac{5V}{5k} = 1 \mu A$$

(invalid)

D1B off, D2 on

$$4V - 5k I_{D2} - V_{D2} - 5k I_{D2} = -2V$$

$$5.6V = 10k I_{D2}$$

$$I_{D2} = 0.56 \mu A$$

$$V_x = 4 - 5k \cdot 0.56 \mu A = 1.3V$$

$$V_{D1B} = 1.3V - 3V = -1.7V$$

(Valid)

$$V_{out} = -2V + 5k \cdot 0.56 \mu A = 0.7V$$