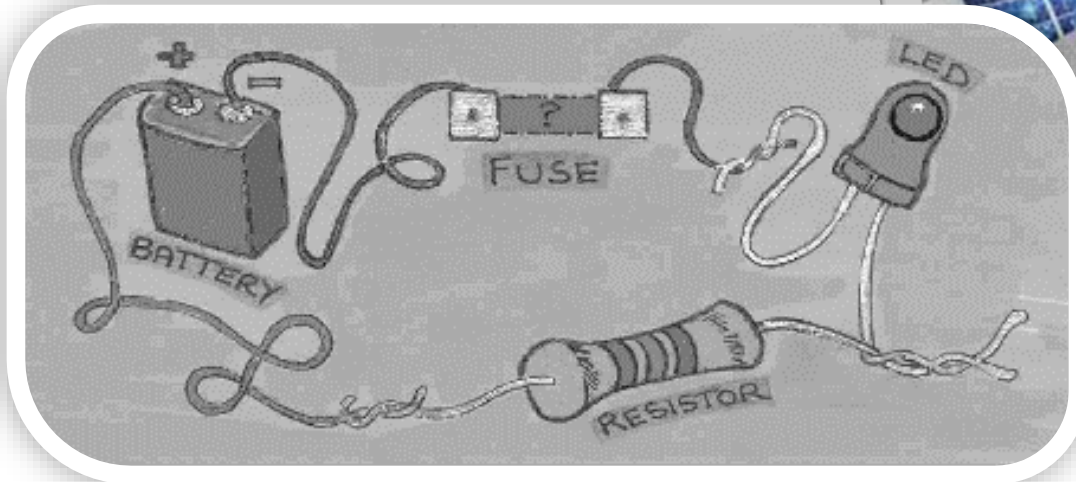


EHB222E QUESTIONS

5th week




Consider the amplifier shown below. Use the following parameters for your calculations.


Transistor parameters : $\beta=200$, $V_{BE}=0.7V$, $V_T=25mV$, $V_A=100V$.

Zener diode voltage: $V_z=6.7V$

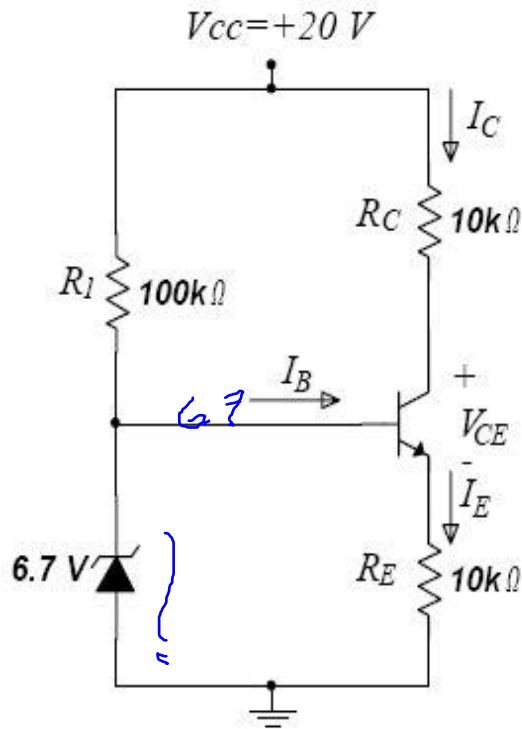a. Find diode current and operating point values of the transistor.



(1)

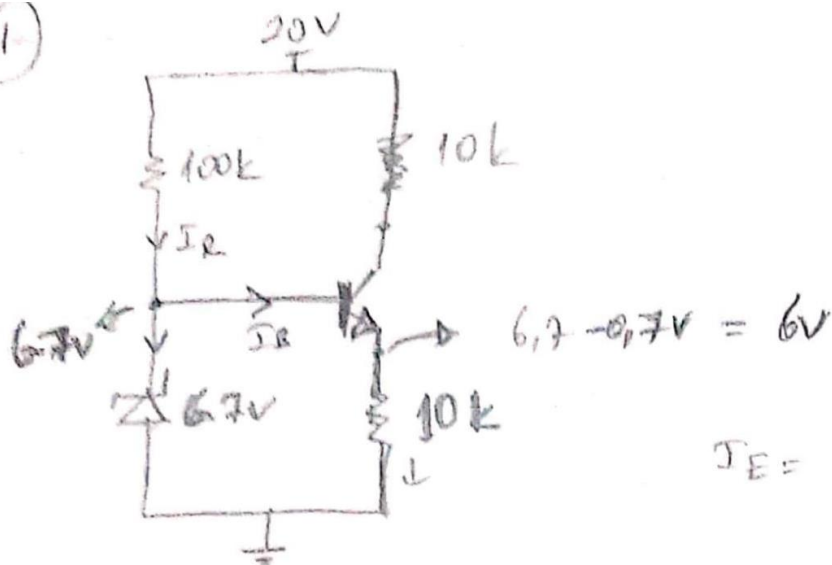

assume ^{that} transistor at active mode

$$I_E = \frac{6V - 0V}{10k} = 0.6 \text{ mA}$$

$$V_C = 20V - 10k \cdot 0.6 \text{ mA}$$

$$V_C = 14V$$

$$V_{CE} = 8V$$

$$V_{BE} = 0.7V$$



$$I_E = \underbrace{(\beta + 1)}_{201} \cdot I_B$$

$$I_B \approx 3 \mu A$$


$$I_R = \frac{20V}{100k} = 0.2 \text{ mA} = 200 \mu A$$

$$I_Z = 197 \mu A$$

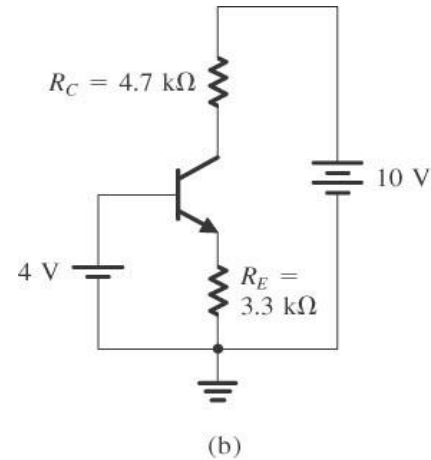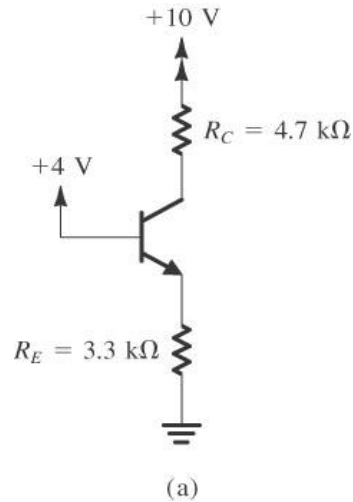For the transistors shown below $\beta = h_{fe} = h_{FE} = 100$, $V_{BE} = 0.7V$. Calculate operating point current and voltage values. Assume that transistor is in active mode. Check this assumption.




Works in active region

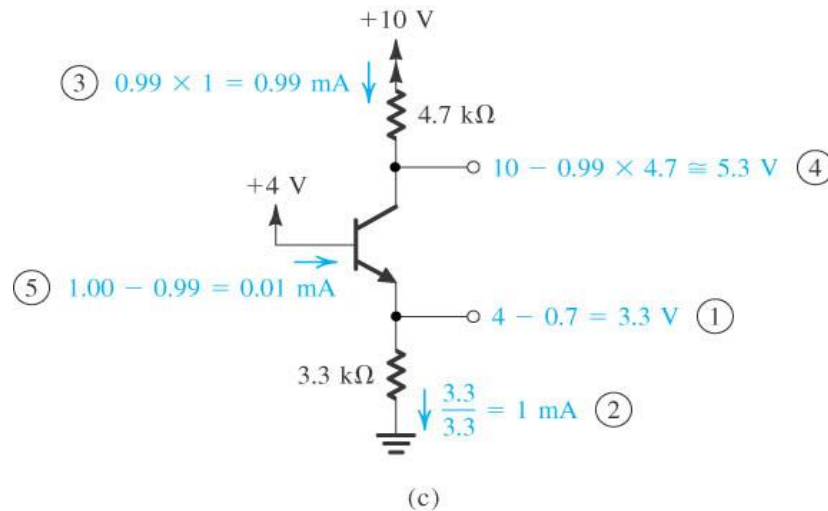


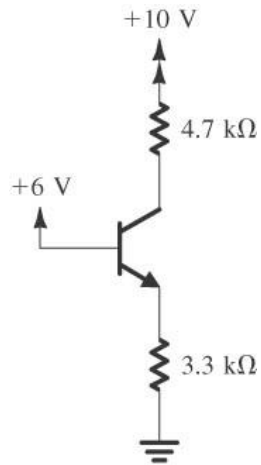(a) circuit; (b) circuit redrawn (c) analysis with the steps numbered.


For the transistors shown below $\beta = h_{fe} = h_{FE} = 100$, $V_{BE} = 0.7V$. Calculate operating point current and voltage values.




(a)

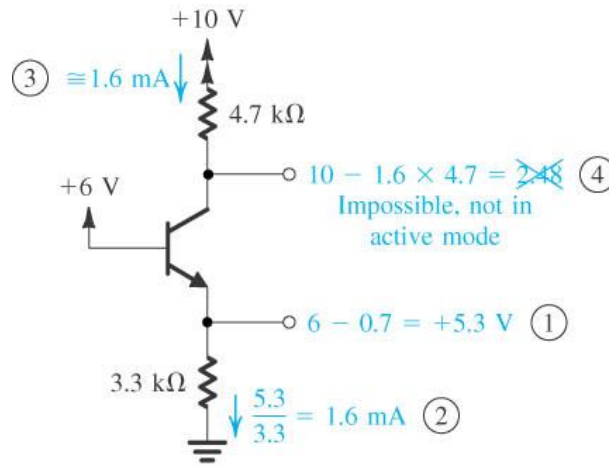

(b)


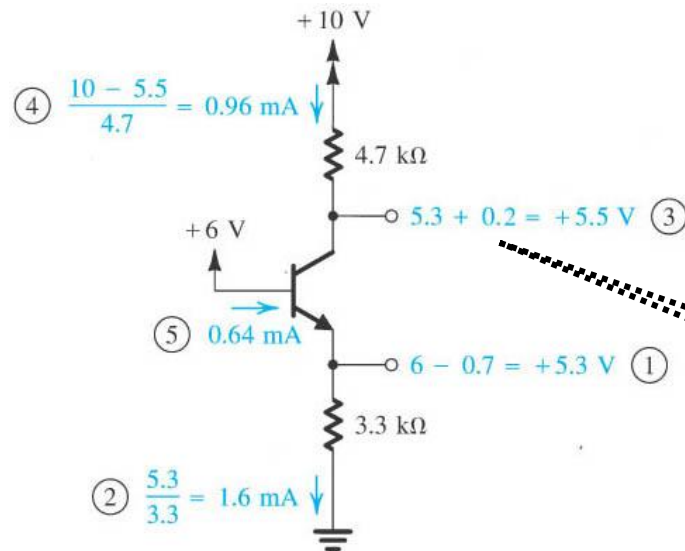


(c)


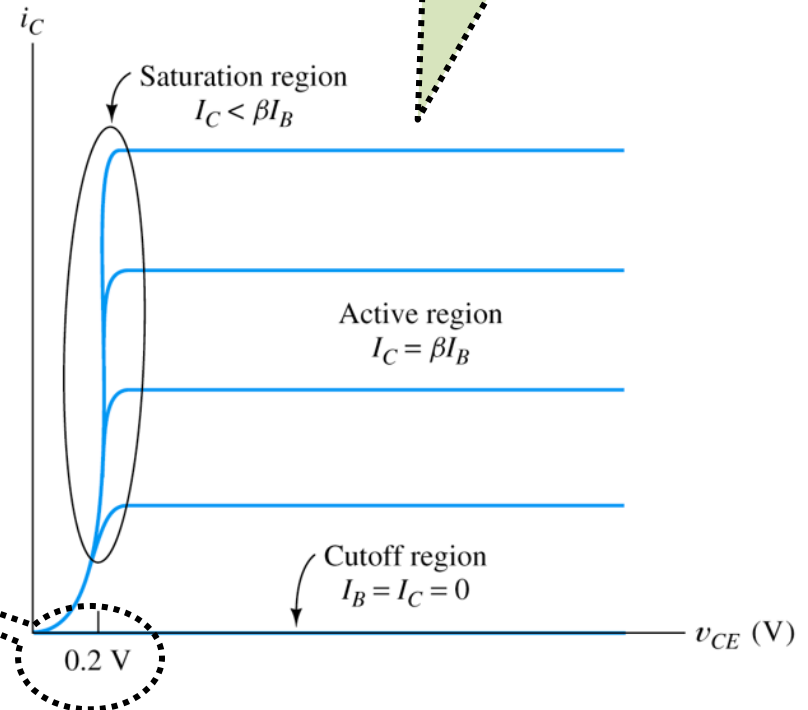


is not valid in saturation mode

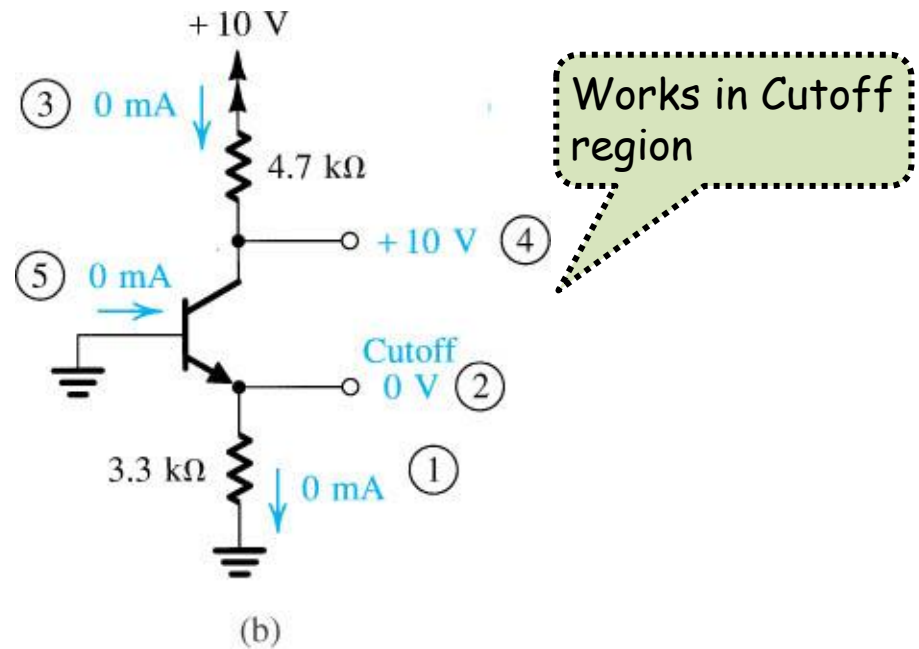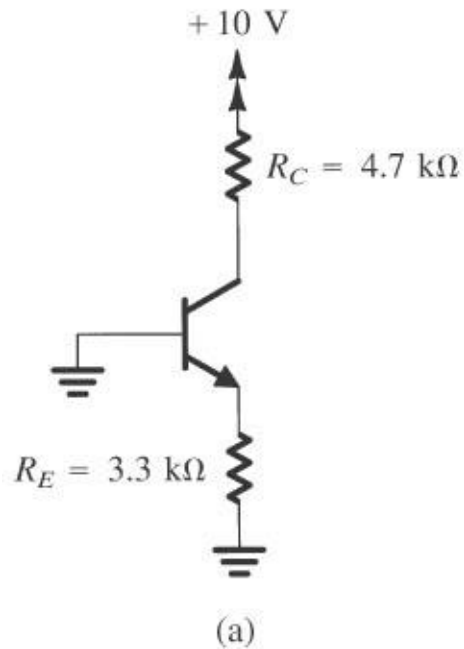For the transistors shown below $\beta = h_{fe} = h_{FE} = 100$, $V_{BE} = 0.7V$. Calculate operating point current and voltage values.





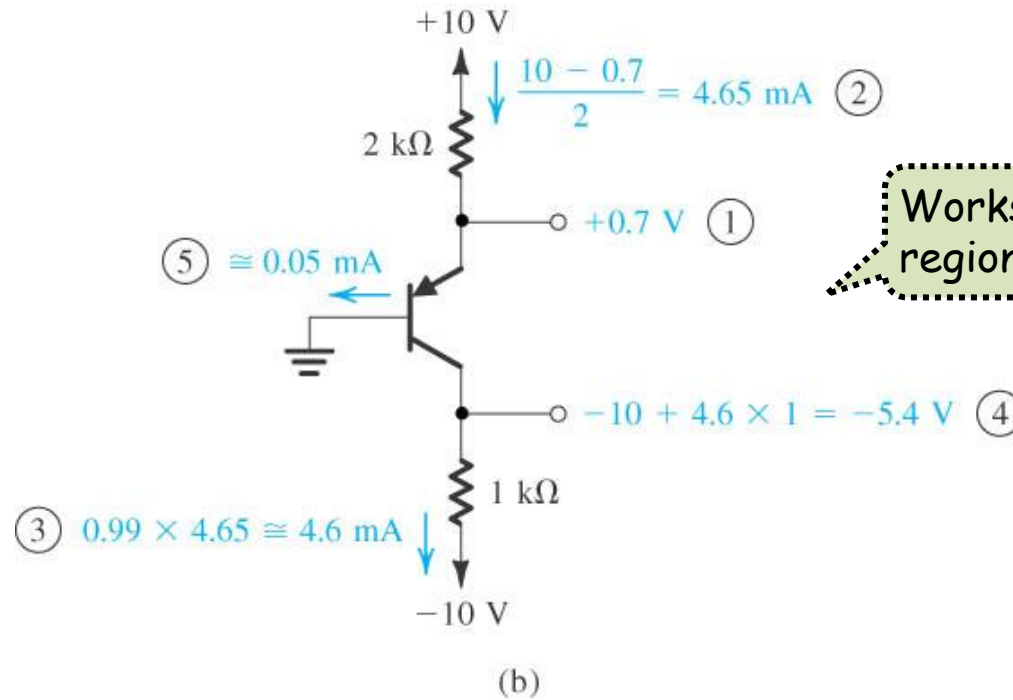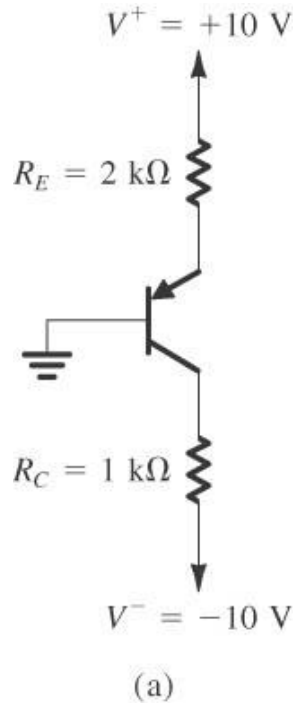For the transistors shown below $\beta = h_{fe} = h_{FE} = 100$, $V_{EB} = 0.7V$. Calculate operating point current and voltage values.





Works in active region

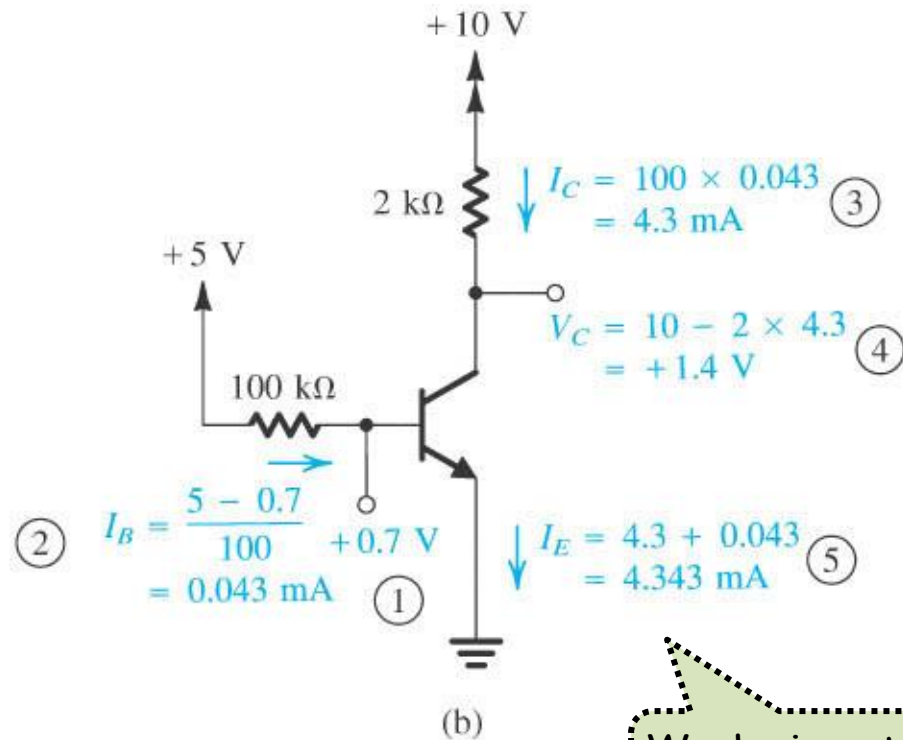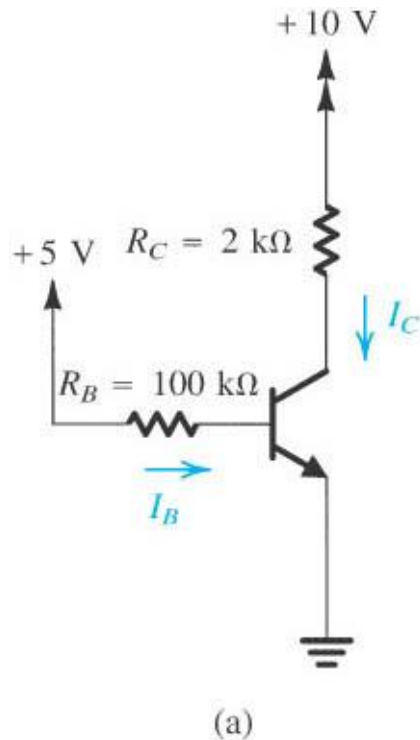For the transistors shown below $\beta = h_{fe} = h_{FE} = 100$, $V_{BE} = 0.7V$. Calculate operating point current and voltage values.



Works in active region

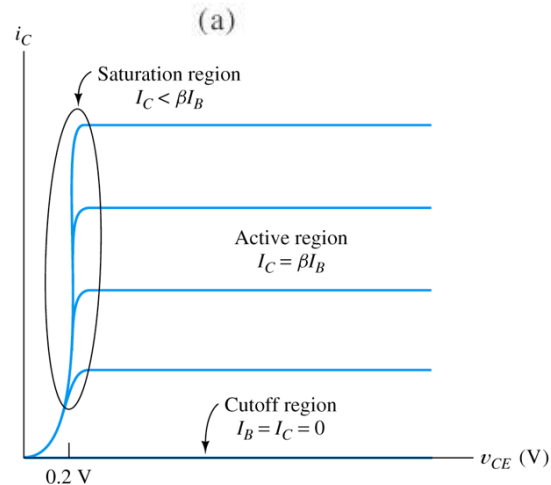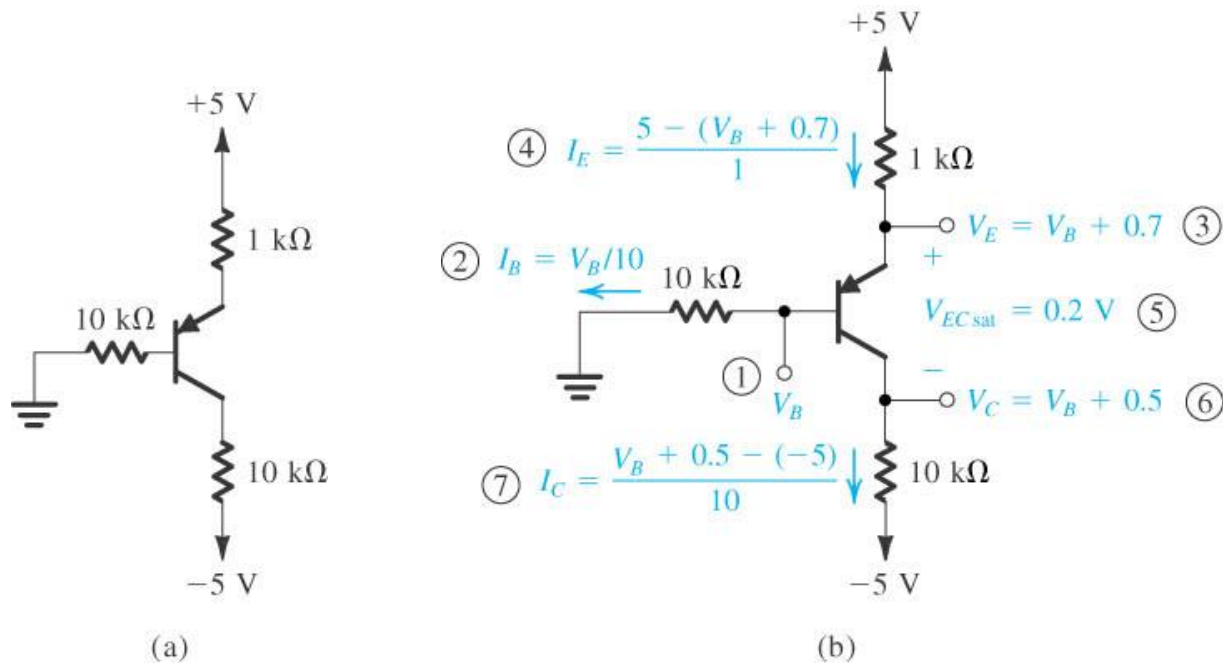For the transistors shown below $\beta = h_{fe} = h_{FE} = 100$, $V_{EB} = 0.7V$. Calculate operating point current and voltage values. Assume that transistor is in saturation mode. Check this assumption.



($\beta = 100$ (active mode) ,saturation mode:
 $V_{EC} = 0.2V$).