

**Instructor:**

Asst. Prof. Onur Kurt

**Student Name:**

**ID:**

**Date:**

**ITU**


**EEF 211E: Basics of Electrical Circuits (Fall 2022)**

**Homework #1**


**Grading Policy:**

- You must submit your homework assignment to the course teaching assistant (TA) before its due date. Late homework will not be accepted/graded.
- Homework should be written clearly and legibly. Your answers should show step-by-step solution of each question. Messy and illegible homework may not be graded.
- You must not ask for answers directly from any aide.
- Academic dishonesty is unacceptable. Plagiarism and cheating on the homework assignment will result in a zero grade.


**Question 1-)** The charge flowing in a conducting wire is plotted in the figure shown below. Sketch graph of the corresponding current.

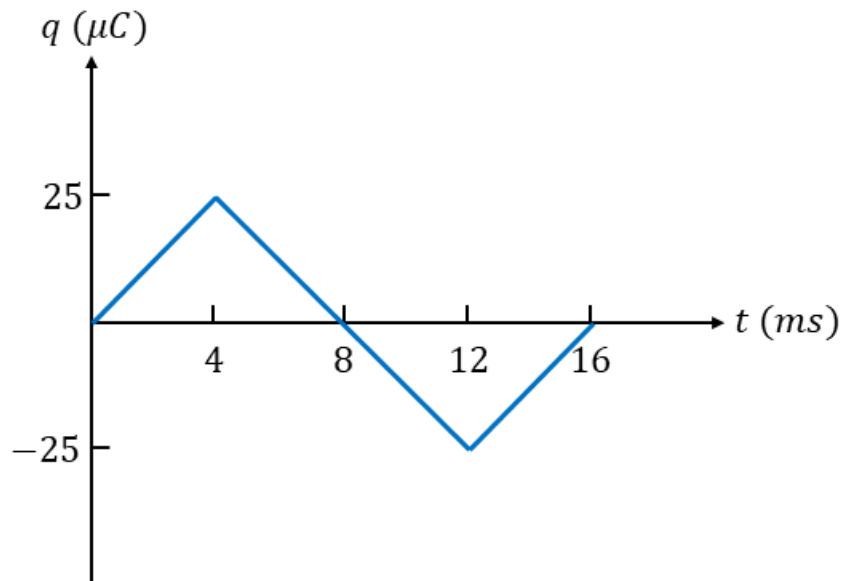

**Question 2-** For the circuit shown below, find  $i_a$ ,  $i_b$ ,  $i_c$ ,  $v_x$  and the power dissipated in the  $50\text{-}\Omega$  resistor.

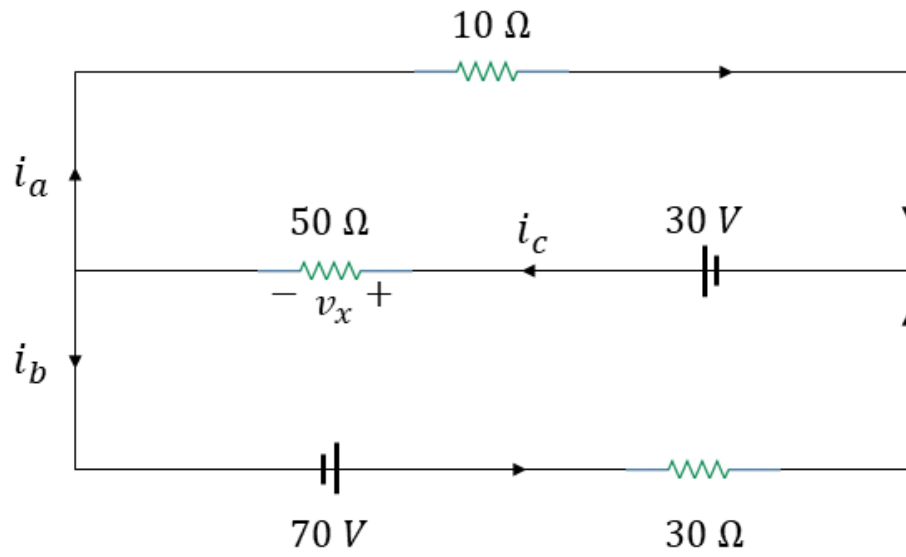

**Question 3-** Calculate the power supplied and absorbed by each element in the figure shown below and verify Tellegen's theorem.

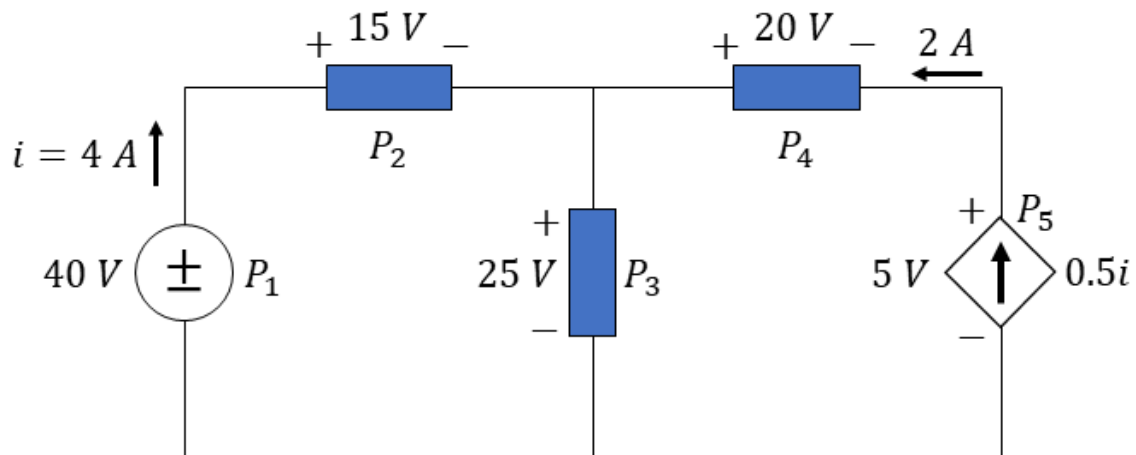

**Question 4-** For the circuit shown below, obtain the equivalent resistance  $R_{eq}$  and use it to find current  $i_0$ .

