



Quiz #1

1. The following questions are according to the memory map given on the side.
- a) Draw the chip select input of *BIOS*, *Main Memory*, and *Graphics Card* separately using the NAND circuit.
- b) Fill the following table according to the address input in which the chip selection area will be enabled or disabled.

Address Input	\overline{CS}_{BIOS}	\overline{CS}_{Memory}	$\overline{CS}_{Graphics}$
0x0523	1	1	1
0xE4C7	1	1	0
0xA4FF	1	1	1
0x6B20	1	0	1


0x0000	
0x3400	
0x37FF	BIOS
0x6800	
0x6BFF	
0xC000	
0xCFFF	
0xFFFF	

2. Build a memory that spans between \$0000 and \$3FFF with 4Kx8 memory chips for a CPU with 8-bit data bus and 16-bit address bus.
- a) Calculate the memory address range for all chips.
- b) How many 4K chips are needed?
- c) Draw the memory design by showing all necessary connections. (Address bus, Data bus, Chip select signals). Use an address decoder (determine its type) and logic gates (determine their types). Assume the decoder select signal and the memory chip select signals are active high.

①

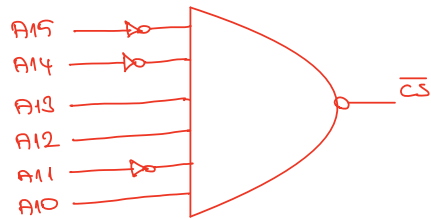
a) BIOS

$0x3400 \Rightarrow 0011 \ 0100 \ 0000 \ 0000$
 $0x37FF \Rightarrow 0011 \ 0111 \ 1111 \ 1111$




MAIN memory

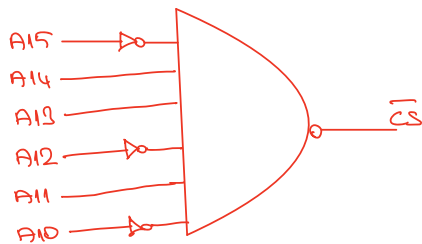$0x6800 \Rightarrow 0110 \ 1000 \ 0000 \ 0000$
 $0x6BFF \Rightarrow 0110 \ 1011 \ 1111 \ 1111$



GRAPHICS CARD

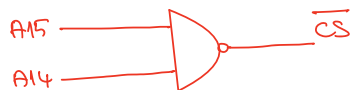$0x0000 \Rightarrow 1100 \ 0000 \ 0000 \ 0000$
 $0xFFFF \Rightarrow 1111 \ 1111 \ 1111 \ 1111$



②

a)

\$0000	⇒	0000	0000	0000	0000
\$0FFF	⇒	0000	1111	1111	1111
<hr/>					
\$1000	⇒	0001	0000	0000	0000
\$1FFF	⇒	0001	1111	1111	1111
<hr/>					
\$2000	⇒	0010	0000	0000	0000
\$2FFF	⇒	0010	1111	1111	1111
<hr/>					
\$3000	⇒	0011	0000	0000	0000
\$3FFF	⇒	0011	1111	1111	1111

b) 4

c)

