

## DENEY PROTOKOL KAĞIDI


Deney No	Deney Tarihi	Deney Adı
05	15.03.2024	Non-linear Applications of Operational Amplifiers

Grup No	Öğrenci No	Adı Soyadı
C10	150200095	Tecrüman Töckçü
C10	150200097	Mustafa Can Çelikkaya
C10	150200107	Erol Kocogly
C10	150200913	Fatma Çelikkaya

Araş Gör Ve imzası	Yusuf Deniz TANBOĞAN Yrd.
-----------------------	---------------------------

Exp 1:

Input Voltage (CH1)

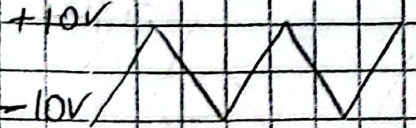

Output Voltages (CH2)

For 0V:



This is a voltage comparator circuit that compares two voltages and determines which of them is the largest in magnitude.

For Min:



It has two input terminals:  
1- Non inverting input + ( $V_{ref}$ )  
2- Inverting input - ( $V_i$ )

For Max:



If the voltage at the non inverting input ( $V_{ref}$ ) is higher than the voltage at the inverting ( $V_i$ ), the difference voltage is positive and the output voltage goes to its maximum positive value. On the other hand, if  $V_{ref}$  is less than  $V_i$ , the difference voltage is negative and the output voltage reaches to its maximum negative value.




Exp 2:

 $V_{out}$ 

This is a voltage limited comparator circuit that restricts the voltage at a particular point in a circuit to a specific level, continuously regulating it to prevent it from exceeding a predetermined threshold. Zener diodes which are semi-conductor devices that conduct in reverse biased direction once a certain voltage (Zener voltage) is reached, are used to regulate the voltage.  $V_0$ , the voltage has not been yet regulated, and  $V_0'$  the voltage after regulation, can be observed on the oscilloscope.

Exp 3, 4:

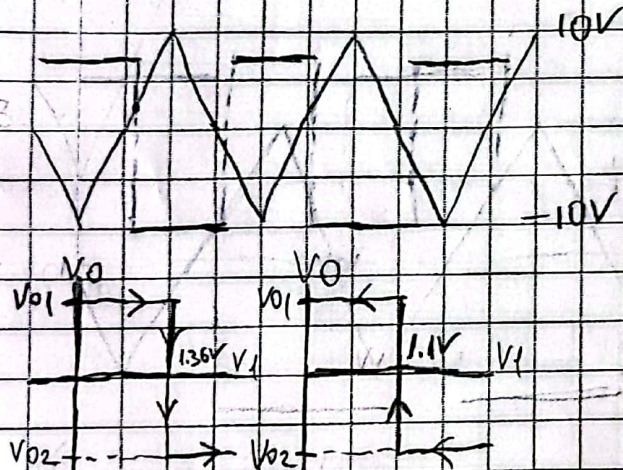

This is a Schmitt trigger circuit that is a comparator circuit with a positive feedback to the noninverting input of an amplifier.

Exp 5:

 $V_0$  $V_0'$