

# **EHB 211E**

## **Basics of Electrical Circuits**


*Asst. Prof. Onur Kurt*

### **Graph Theory**



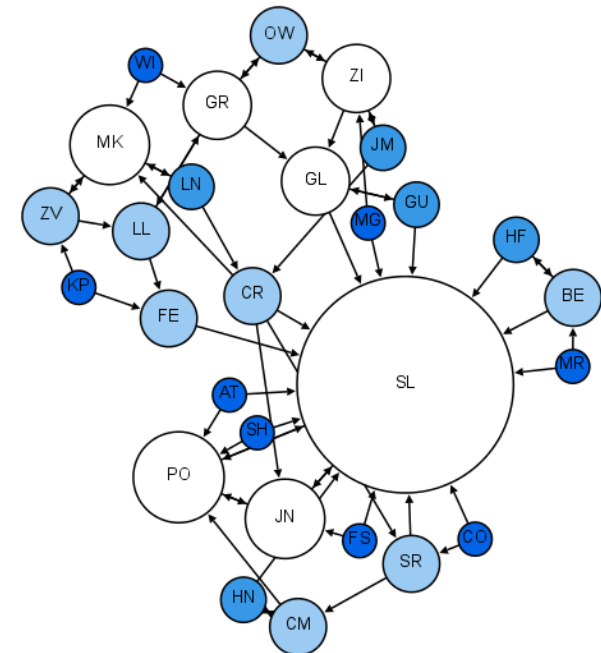
# Introduction

- Graph theory (aka network topology): study and model large number of applications in different fields.
  - ❑ Computer science: flow of computation, data organization
  - ❑ Electrical Engineering: design of circuit connection
  - ❑ Physics and chemistry: study molecules (constructing lattice of molecule)
  - ❑ Mathematics: minimum cost part, scheduling problem
  - ❑ Biology: interaction between species (protein-protein interaction)
  - ❑ Linguistics: grammar of language tree
  - ❑ Represent routes between cities


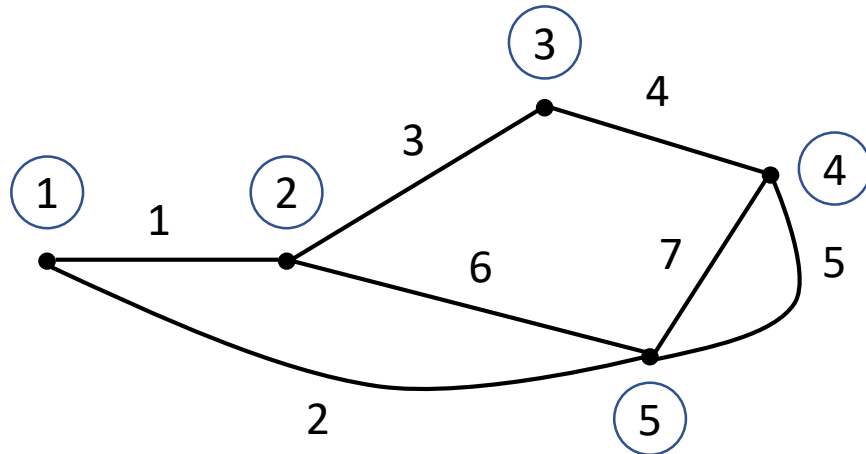
# Basic Terminology

- What is a graph?
  - Set of nodes connected by branches
- Node (aka vertex): common terminal or point of two or more branches. Node is denoted by  $n$
- Branch (aka edge): line segment that replaces the network element and connects two nodes. Branch is denoted by  $b$ .
- Simple example of graph:




5 nodes and 7 branches  
 $n=5$  &  $b=7$


# Types of Graphs

- Two types of graphs
  - Undirected graph: direction not specified
  - Directed graph (digraph): all branches are represented with arrows.

Undirected graph

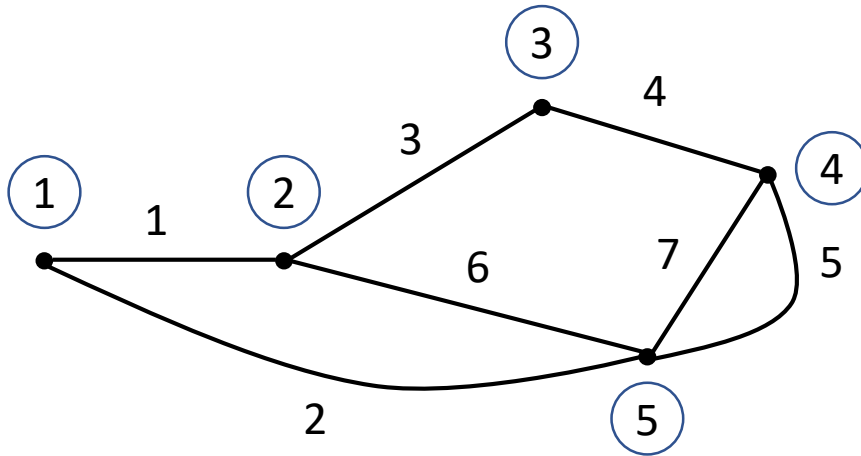

Directed graph

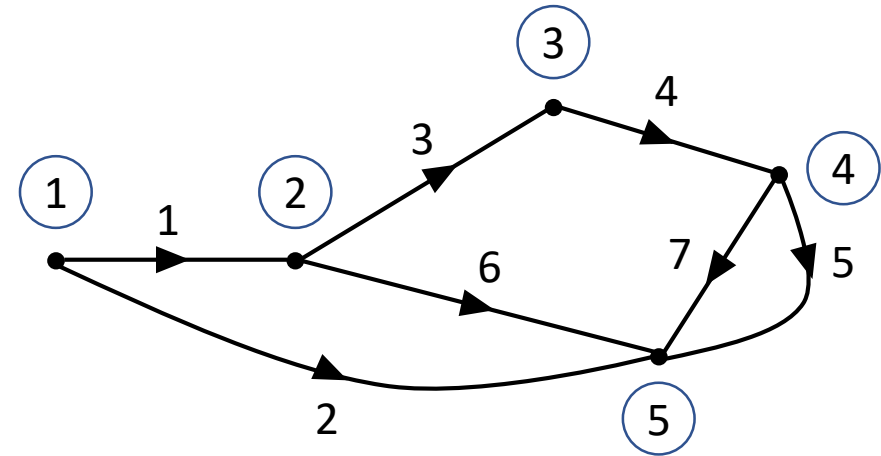


Arrows indicate the direction of current flow in each branch

# From Circuits to Graphs

- Graph retains all interconnection properties of the circuit but suppresses the information on the circuit elements.

Two terminal element

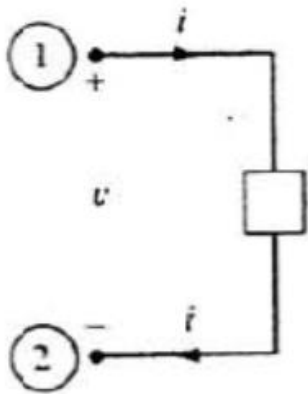

digraph




Digraph representation of two terminal element with two nodes and one branch


Voltage in branch: branch voltage  
Current in branch: branch current

Power delivered to element:  $p(t) = v(t)i(t)$

Three terminal element

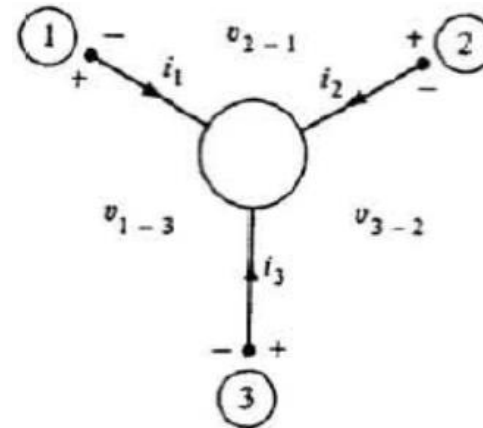

digraph

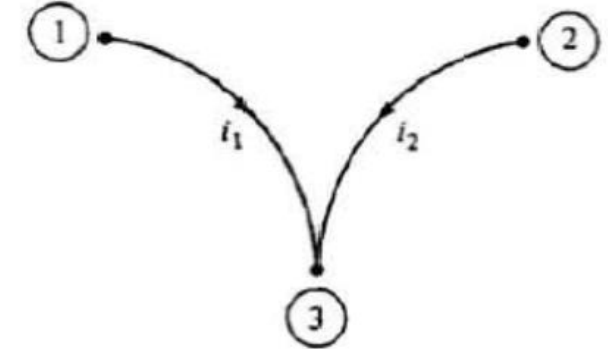


Digraph representation of a three terminal element with node 3 chosen as datum (reference node).  
Three nodes and two branches.

Apply KVL: Two independent voltages  
Apply KCL: Two independent currents

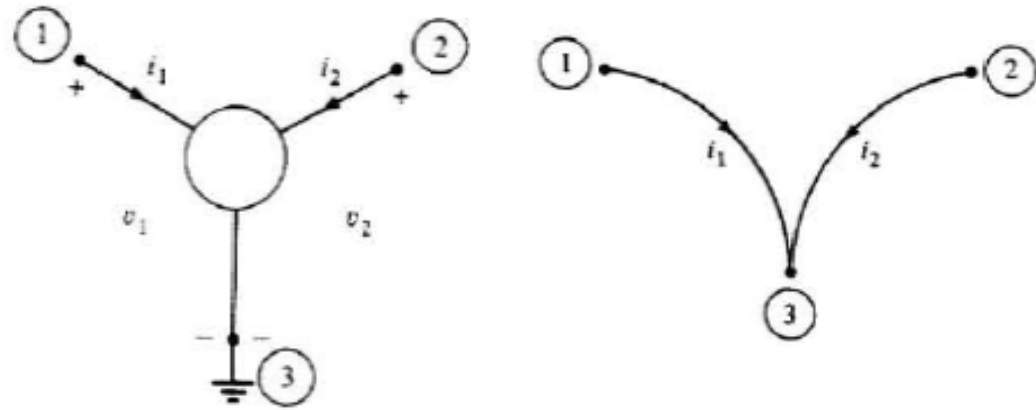
# From Circuits to Graphs

- All possibilities for digraph representation of three terminal elements depending on which node chosen as the datum (reference) node.


Node 3 (datum node):  $v_1 > v_3$  &  $v_2 > v_3$



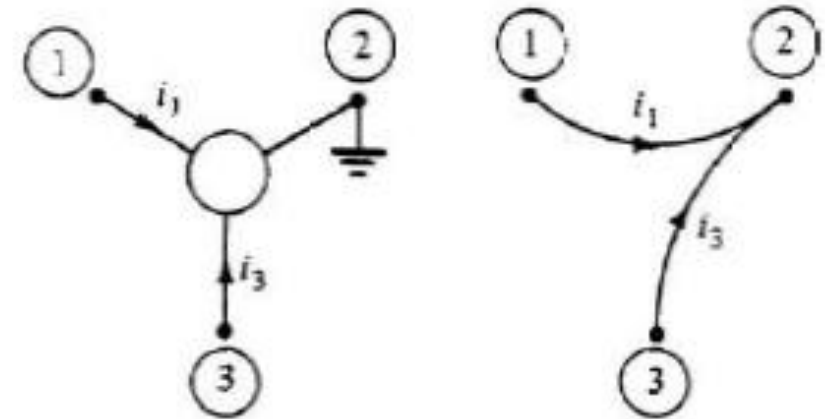Node 2 (datum node):  $v_1 > v_2$  &  $v_3 > v_2$




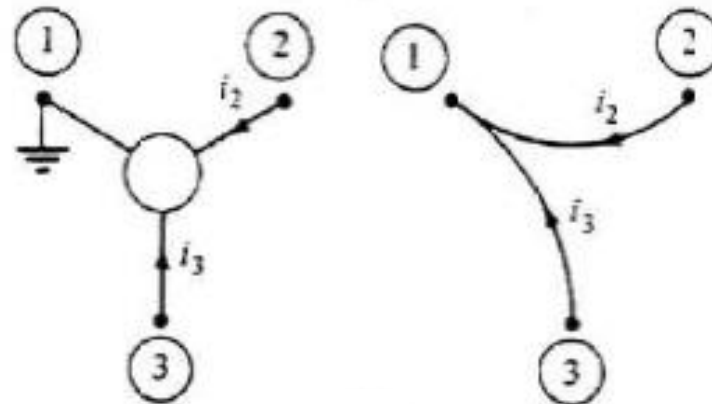
Node 1 (datum node):  $v_2 > v_1$  &  $v_3 > v_1$


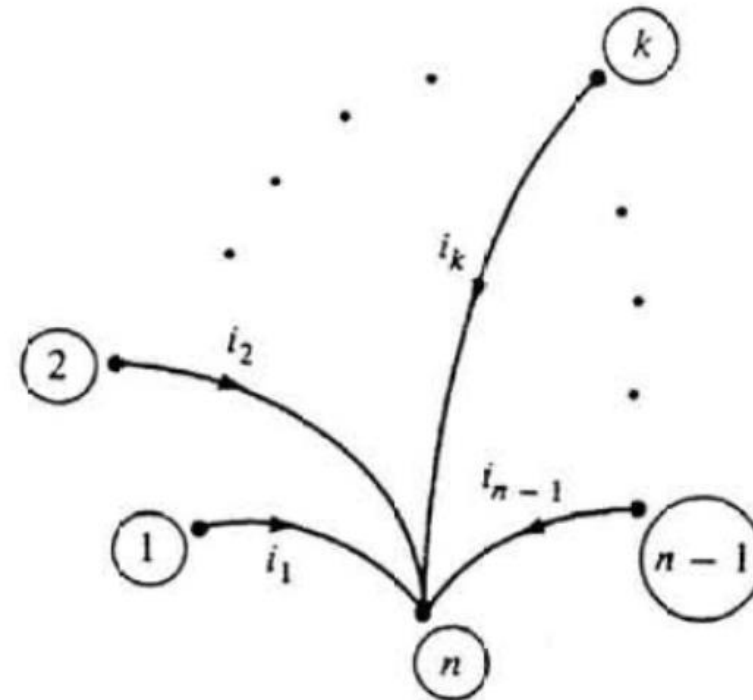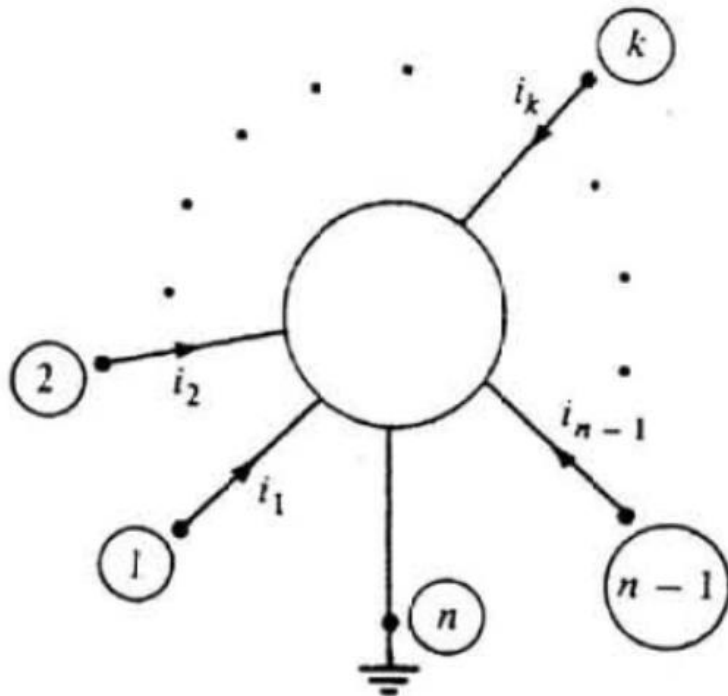
# From Circuits to Graphs

- General form of  $n$ -terminal elements with digraph representation:

$n$ -terminal element:  $n$  nodes and  $n-1$  branches





# Example

Demonstrate the op amp circuit shown below with the corresponding digraph
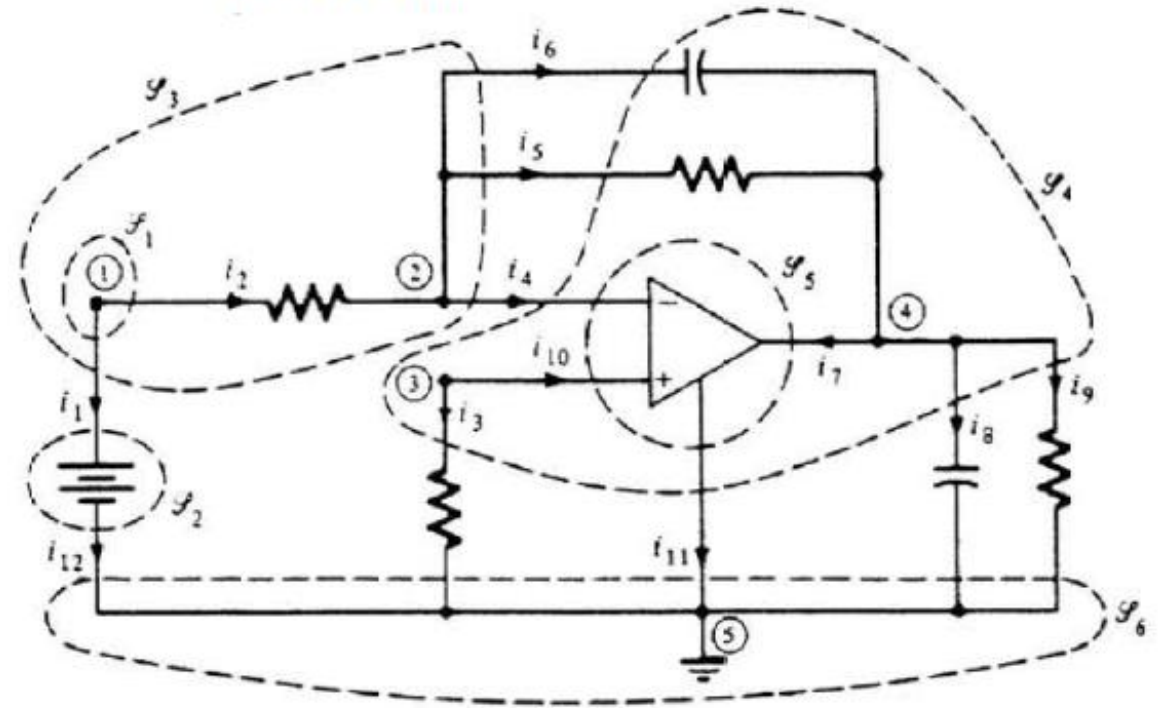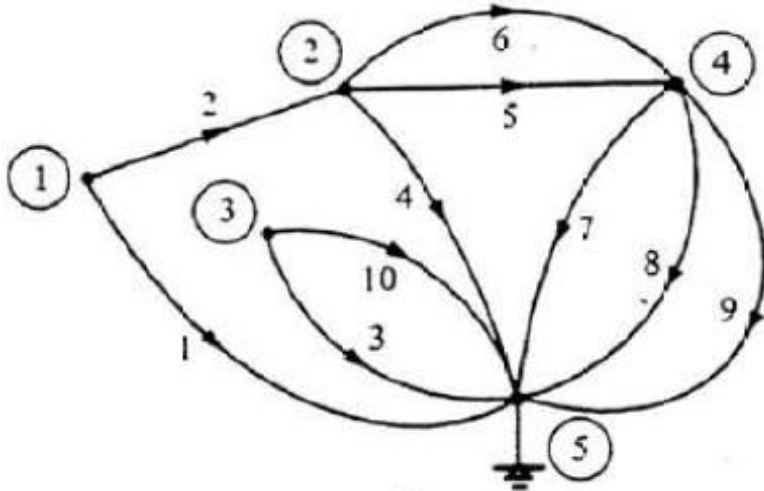
## Solution:

- Seven two-terminal elements and one four-terminal element
- Recall:  $n$ -terminal elements have  $n-1$  branches
- Total number of branches in digraph:  $7+4-1=10$
- Circuit has five nodes. Thus, digraph has five nodes (node 5: datum node)




Suppressed circuit elements  
when drawing the digraph


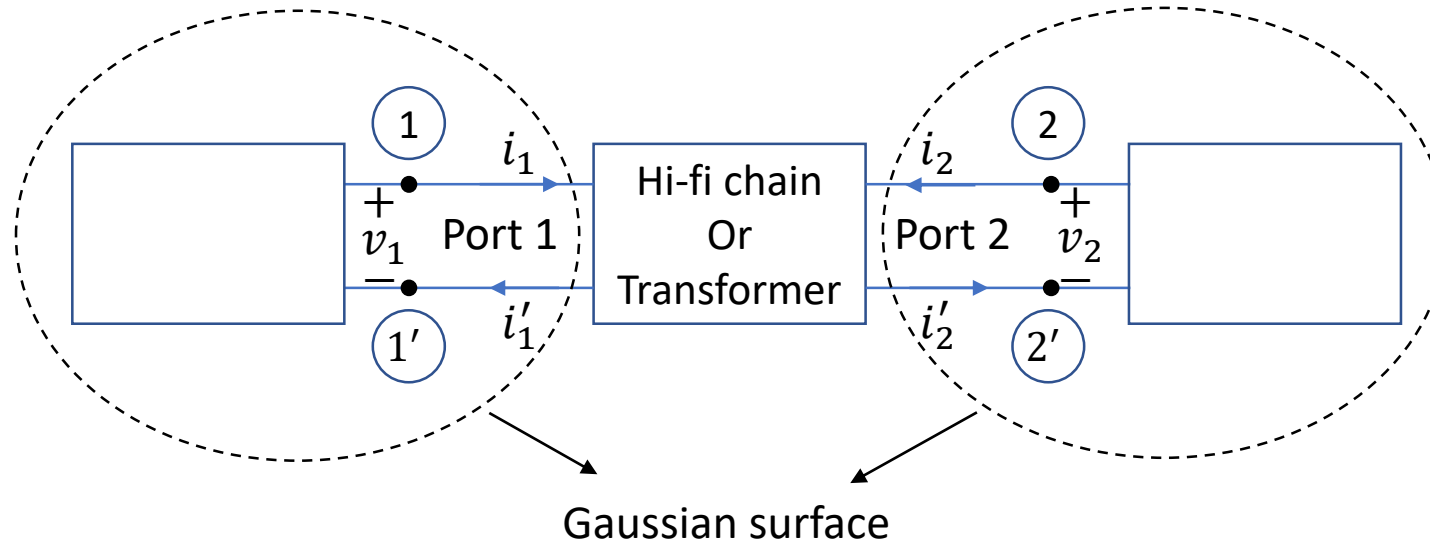
# Two-Ports

- Two-port: circuit element or a circuit with pairs of terminals.
- Example of two-port circuit: Hi-fi chain, two-winding transformer




Apply KCL:  $i_1 = i'_1$  and  $i_2 = i'_2$   
(port condition)

Two-port network reduces  
number of currents from 4 to 2

Power delivered to two-port:  
 $p(t) = v_1(t)i_1(t) + v_2(t)i_2(t)$

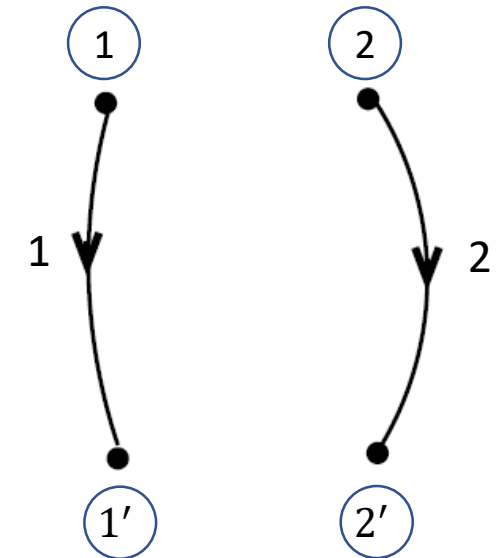Digraph representation  
of two-port circuit




Two-port: 4 nodes and 2 branches


$i_1$  and  $i_2$ : branch currents  
 $v_1$  and  $v_2$ : branch voltages
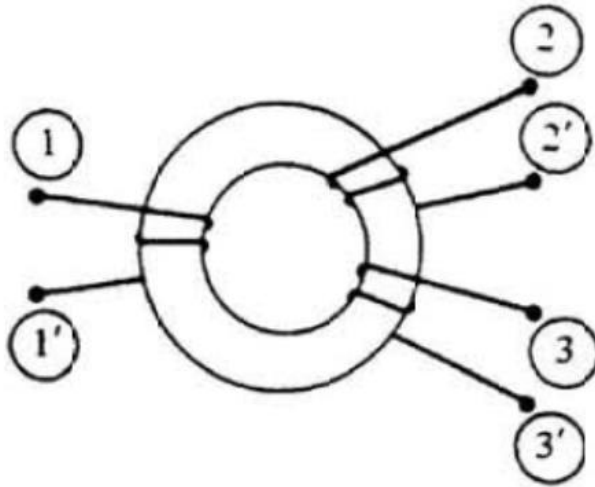
# Multiport


- Generalize the concept of two-port to multiport
- Three-winding transformer: three-port network or circuit.



Three-winding transformer

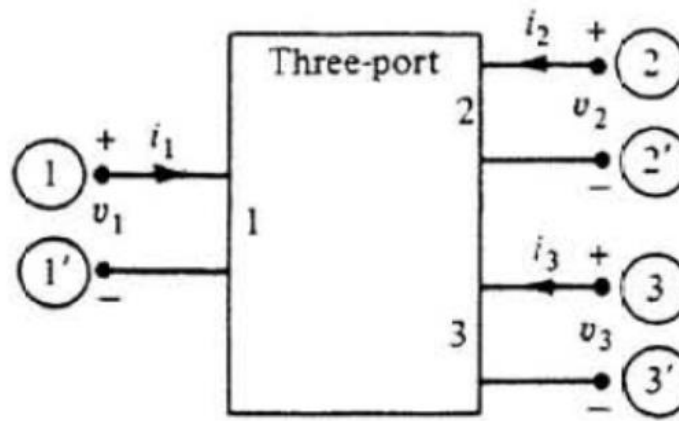

Three-port

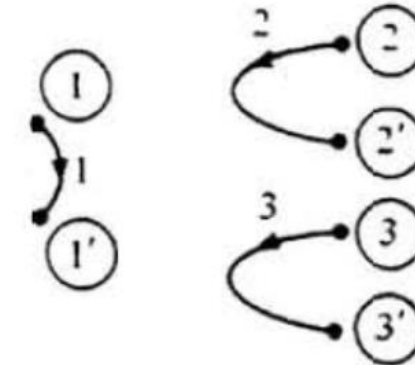

digraph

Three-winding transformer: three-port  
its digraph: 6 nodes and 3 branches


## Recall:

Digraph (directed graph) is a graph that is made up of a set of vertices (nodes) connected by edges (branches)


# Grounded Two-Port

- If a common connection exists between node  $1'$  and  $2'$ , it is called grounded two-port. This is equivalent to three terminal element

Grounded two-port

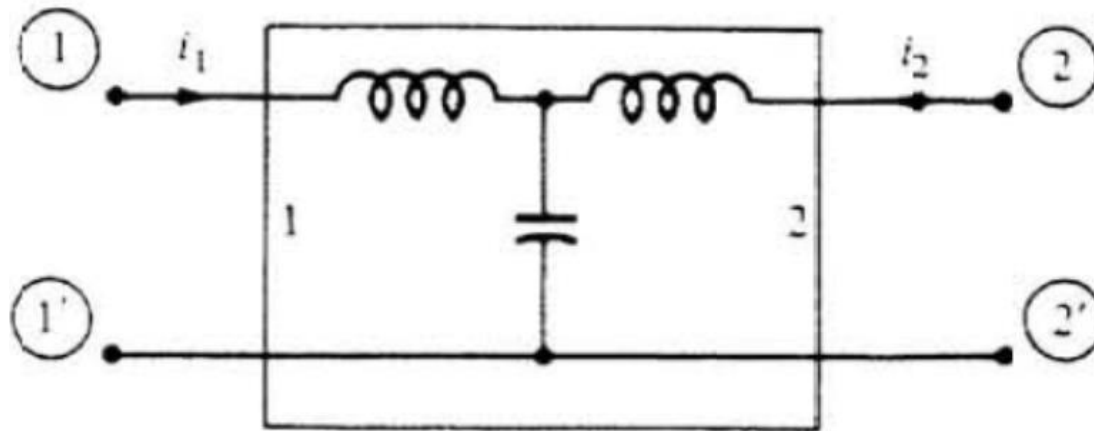


digraph

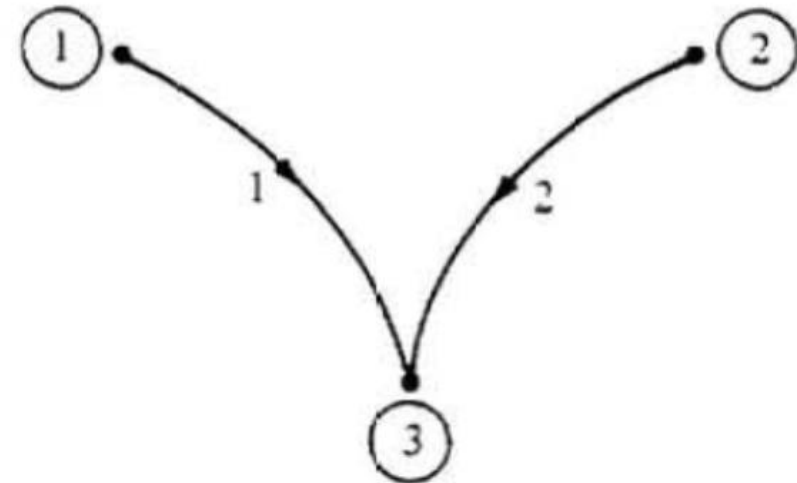

- Digraph of grounded two-port: 3 nodes and 2 branches which are tied together at the common node
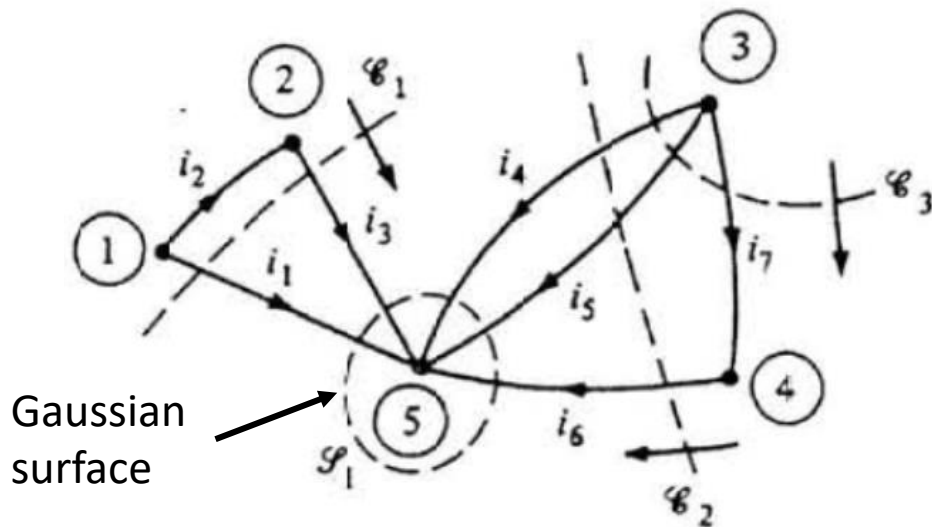
# Cut Sets

- Cut set is very useful concept in graph theory
- Given a connected digraph  $G$ , a set of branches  $b$  of  $G$  is called a cut set if and only if:
  - The removal of all the branches of the cut set results in a unconnected digraph (resulted digraph is no longer connected).
  - The removal of all but any one branch of  $G$  leaves the digraph connected. In other words, if any branch in the set is left intact, the digraph remains connected.



$b_1, b_2, b_3$  represent the cut set line.


Arrows for  $b_1, b_2, b_3$  define a reference direction for each cut set. A reference direction is chosen arbitrary.

Cut set is a way to isolate node or nodes from the circuit

- $b_1 = \{1,3\} \longrightarrow b_1$  intersects with branch  $\{1,3\}$
- $b_2 = \{4,5,6\} \longrightarrow b_2$  intersects with branch  $\{4,5,6\}$
- $b_3 = \{4,5,7\} \longrightarrow b_3$  intersects with branch  $\{4,5,7\}$
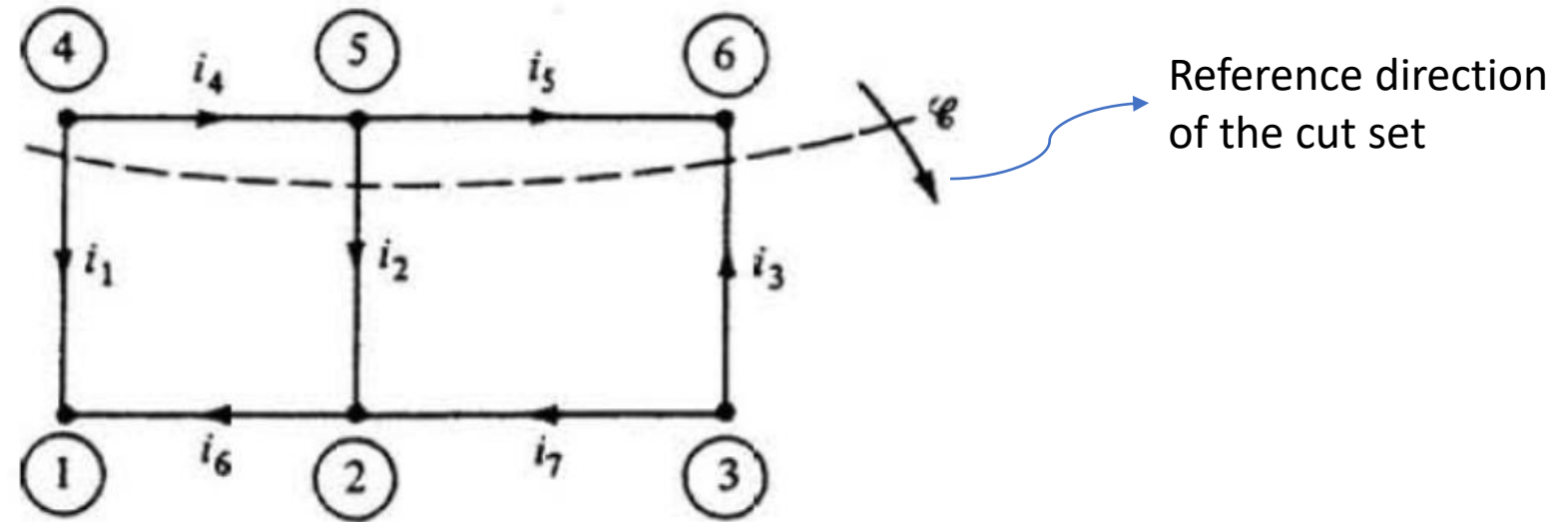
# Cut Sets and KCL

- KCL: algebraic sum of the currents associated with any cut set is equal to zero.




- For the digraph shown in the figure, the cut set  $b = \{1, 2, 3\}$  is indicated by the dashed line cutting through these branches. (it intersects with three branches  $\{1, 2, 3\}$ ).
- Direction of current is positive if it is in the same direction as the reference direction of the cut set.

$$i_1 + i_2 - i_3 = 0$$
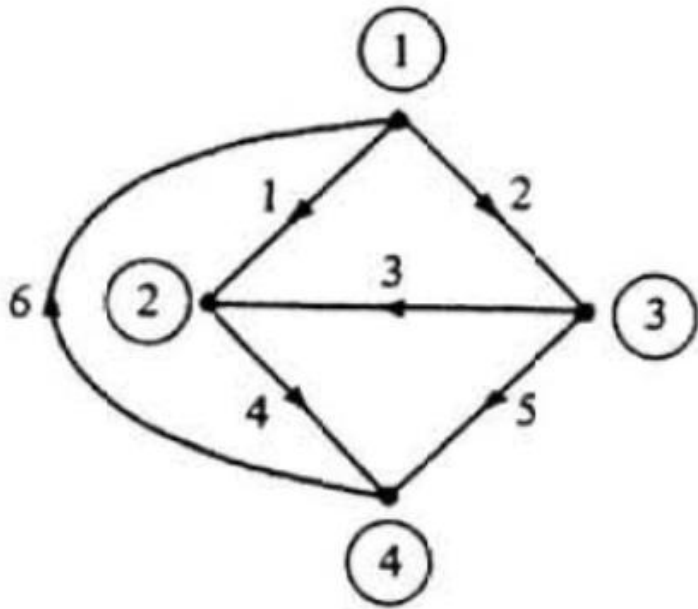
# Matrix Formation—KCL

- Formation of incidence matrix of the digraph.
- The incidence matrix is denoted by  $A_a$
- If digraph  $G$  has  $n$  nodes and  $b$  branches, then  $A_a$  has  $n$  rows (one row for each node) and  $b$  columns (one column for each branch).



- Digraph: 4 nodes and 6 branches
- By definition:  $A_a$  has 4 rows and 6 columns
- Apply KCL
- Before writing KCL equations for each node, assign a reference direction for currents
- The direction of current is positive (+) if branch leaves the node. Otherwise it is negative

# Matrix Formation—KCL

- Write the KCL equation for each node:

Branches: 1    2    3    4    5    6

Node 1:  $i_1 + i_2 - i_6 = 0$

Node 2:  $-i_1 - i_3 + i_4 = 0$

Node 3:  $-i_2 + i_3 + i_5 = 0$

Node 4:  $-i_4 - i_5 + i_6 = 0$


- KCL equations in matrix form as:

$$\begin{array}{l}
 \textcircled{1} \rightarrow \\
 \textcircled{2} \rightarrow \\
 \textcircled{3} \rightarrow \\
 \textcircled{4} \rightarrow
 \end{array}
 \begin{bmatrix}
 1 & 1 & 0 & 0 & 0 & -1 \\
 -1 & 0 & -1 & 1 & 0 & 0 \\
 0 & -1 & 1 & 0 & 1 & 0 \\
 0 & 0 & 0 & -1 & -1 & 1
 \end{bmatrix}
 \begin{bmatrix}
 i_1 \\
 i_2 \\
 i_3 \\
 i_4 \\
 i_5 \\
 i_6
 \end{bmatrix}
 =
 \begin{bmatrix}
 0 \\
 0 \\
 0 \\
 0
 \end{bmatrix}$$

↙
↗

branch 1
branch 6

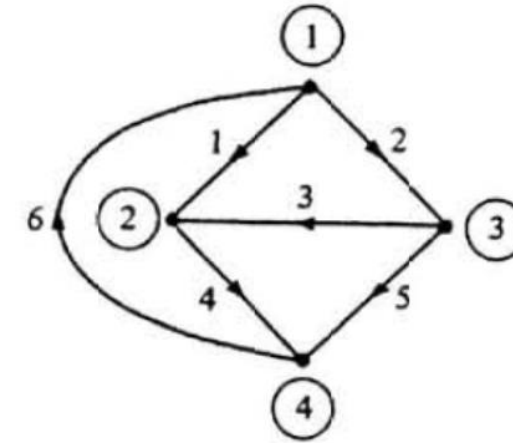$4 \times 6$  matrix called incidence matrix  $A_a$



- Node equation of digraph can be written as:

$A_a$ : incidence matrix

$$A_a i = 0$$

$i$ : branch current vector  
(magnitude and direction)

- Rank: number of linear independent equations in a digraph, denoted by  $r$ .

$$r = n - 1 \quad n \text{ is number of nodes}$$


- For any connected digraph  $G$  with  $n$  nodes, if we choose a datum node and throw away the corresponding KCL equation, the remaining  $n-1$  KCL equations are linearly independent

# Matrix Formation—KCL

- Assume node 4 is a datum (reference) node
- Delete the last equation (row corresponding datum node).

$$\begin{array}{l}
 \textcircled{1} \rightarrow \\
 \textcircled{2} \rightarrow \\
 \textcircled{3} \rightarrow
 \end{array}
 \begin{bmatrix}
 1 & 1 & 0 & 0 & 0 & -1 \\
 -1 & 0 & -1 & 1 & 0 & 0 \\
 0 & -1 & 1 & 0 & 1 & 0
 \end{bmatrix}
 \begin{bmatrix}
 i_1 \\
 i_2 \\
 i_3 \\
 i_4 \\
 i_5 \\
 i_6
 \end{bmatrix}
 =
 \begin{bmatrix}
 0 \\
 0 \\
 0
 \end{bmatrix}
 \Rightarrow Ai = 0$$

Reduced incidence matrix  $A$

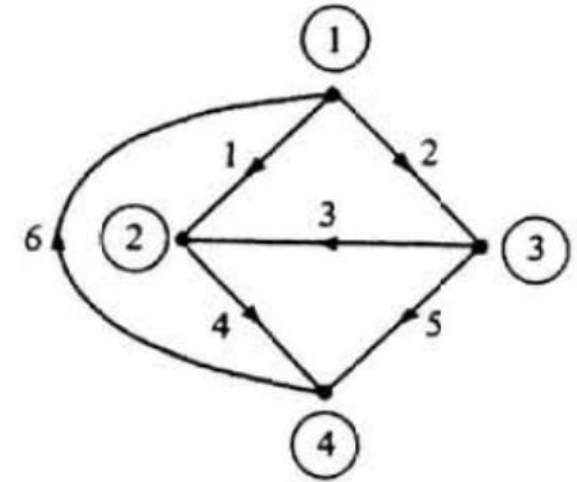

- $A$  (reduced incidence matrix) is obtained from  $A_a$  (incidence matrix) by deleting the row which corresponds to the chosen datum node
- Addition of all the KCL equation in above matrix will not cancel out each other. Three KCL equations are linearly independent.
- For connected digraph with  $n$  nodes, dimension of reduced incidence matrix is  $(n - 1) \times b$



# Matrix Formation—KCL

- Write KCL equations in a matrix form using cut sets
- First, write all distinct cut sets for the given digraph

$$b_1 = \{1,2,6\} \quad b_4 = \{4,5,6\}$$

$$b_2 = \{1,3,4\} \quad b_5 = \{2,3,4,6\}$$

$$b_3 = \{2,3,5\} \quad b_6 = \{1,3,5,6\}$$


- Based on the cut sets, the matrix is as follows:

$$\begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 \\ 0 & 1 & -1 & 1 & 0 & -1 \\ 1 & 0 & 1 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \Rightarrow Q_a i = 0$$

Cut-set matrix,  $Q_a$

Rank of cut set matrix:  $r = n - 1$

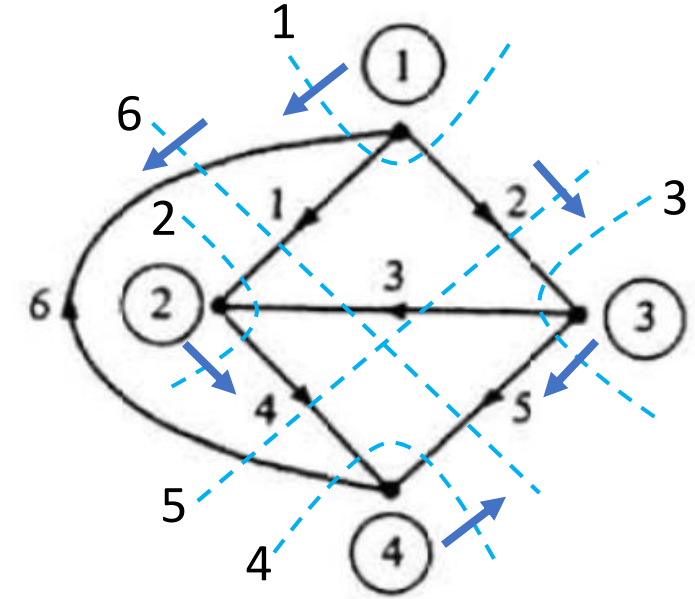$Q_R i = 0$  ( $Q_R$  is called reduced cut-set matrix obtained by deleting redundant equations)



## Recall:

Cut set is a partition of the nodes (vertices) of a graph into two disjoint subsets


## Recall:

Direction of current is positive if it is in the same direction as the reference direction of the cut set.
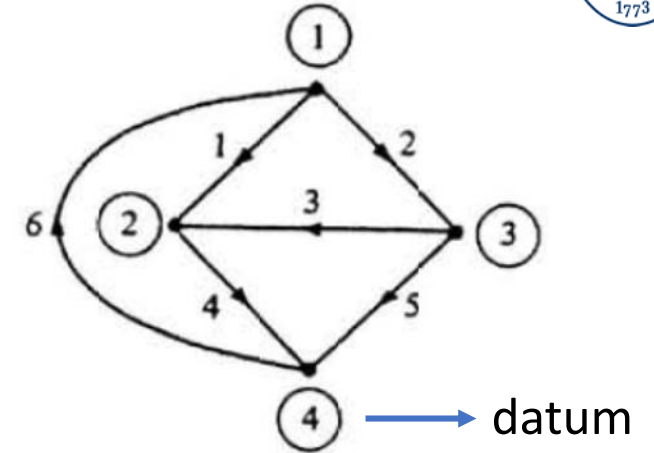
# Matrix Formation—KVL

- KVL: another way of obtaining matrix form of the digraph
- Using the associated reference direction, the branch voltages:

$$\begin{aligned}
 v_1 &= e_1 - e_2 \\
 v_2 &= e_1 - e_3 \\
 v_3 &= -e_2 + e_3 \\
 v_4 &= e_2 - e_4 \\
 v_5 &= e_2 - e_3 \\
 v_6 &= -e_1
 \end{aligned}
 \Rightarrow
 \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \underbrace{\begin{bmatrix} 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & -1 & 1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & 0 & 0 \end{bmatrix}}_M \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} \Rightarrow v = Me$$



$v = [v_1, v_2, v_3, \dots, v_n]^T$  is the branch voltage vector  
 $e = [e_1, e_2, e_3, \dots, e_n]^T$  is the node-to-datum voltage vector  
 $M: b \times (n - 1)$  matrix

- Comparing KCL & KVL equations:  $M = A^T \longrightarrow$   $M$  matrix equals to transformation of reduced incidence matrix  $A$

$$v = A^T e$$

# Graph Theory—Subgraph


- digraph  $G$  is define as a set of vertices (nodes) connected by edges (branches) where the direction of all edges (branches) is specified.

$$G = (v, b)$$

- Let  $G_1$  is a subgraph of  $G$  if and only if  $G_1$  itself is a graph.

$$G_1 = (v_1, b_1) \text{ where } v_1 \text{ is subset of } v \text{ and } b_1 \text{ is subset of } b$$




- Example of subgraphs of digraph  $G$ :

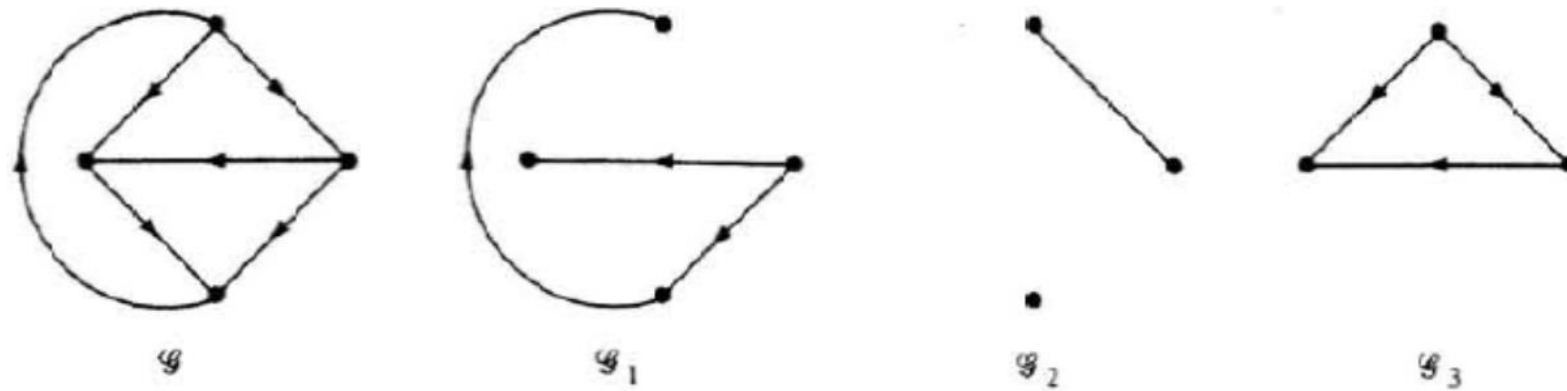

- Graph is connected if there is a path from any point to any other point in the graph.
- Graph  $G$  is connected but subgraph does not have to be connected.
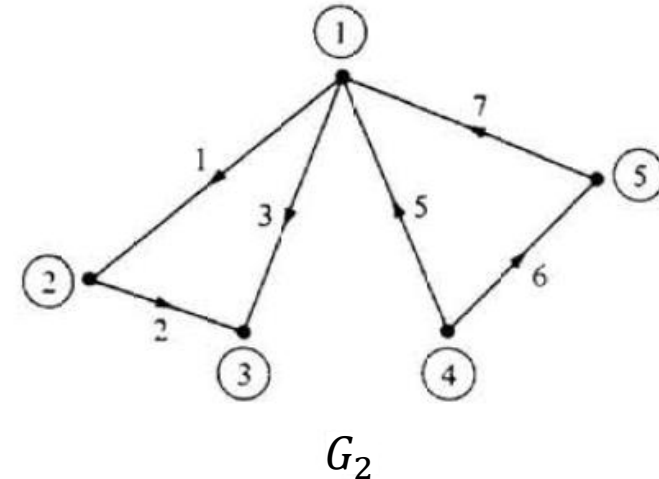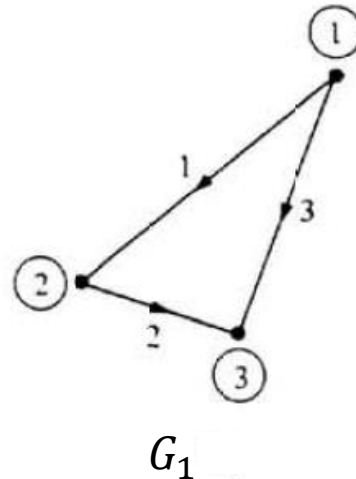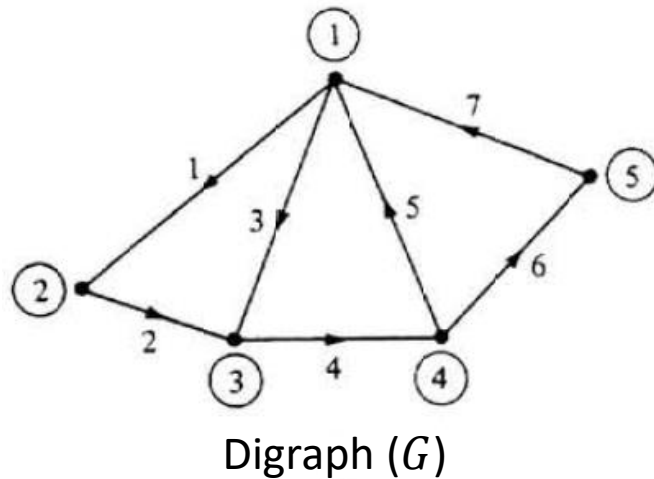
# Graph Theory—Loop


- Loop: connected subgraph of digraph  $G$  in which precisely two branches are incident with each other.
- For the loop concept, consider the following digraph  $G$ :




- $G$ : digraph
- $G_1$ : loop
- $G_2$ : not a loop as it violates the definition of loop at node 1.
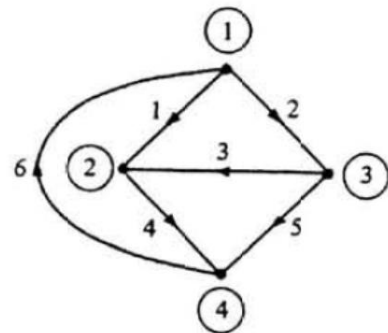
# Graph Theory—KVL Based on Loops


- KVL equations based on loops
- First, identify all possible distinct loops from the digraph
- Following are all distinct loops:




Digraph ( $G$ )

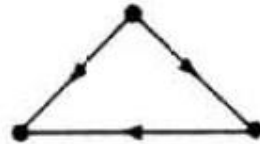

$L_1$

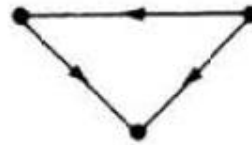


$L_2$

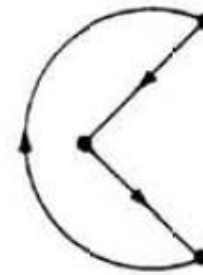


$L_3$




$L_4$

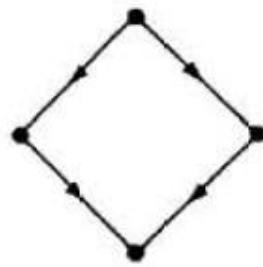

$L_5$

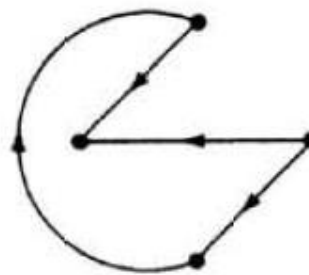

$L_6$

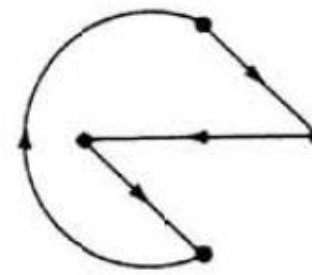

$L_7$

- Every node has exactly two branches
- 7 distinct loops of digraph  $G$

# Graph Theory—KVL Based on Loops

- Apply KVL to each loop:

$$L_1: v_1 - v_2 - v_3 = 0$$

$$L_2: v_3 + v_4 - v_5 = 0$$









$$L_3: v_1 + v_4 + v_6 = 0$$

$$L_4: v_2 + v_5 + v_6 = 0$$

$$L_5: v_1 - v_2 + v_4 - v_5 = 0$$

$$L_6: v_1 - v_3 + v_5 + v_6 = 0$$

$$L_7: v_2 + v_3 + v_4 + v_6 = 0$$

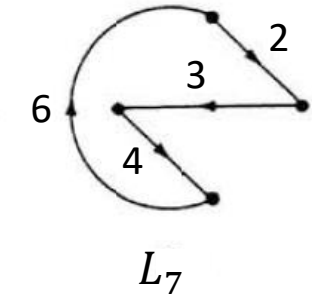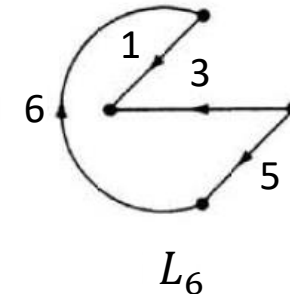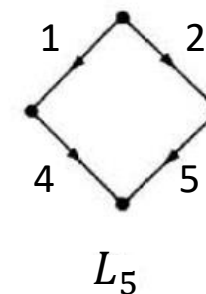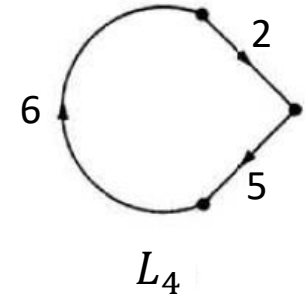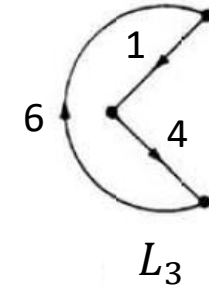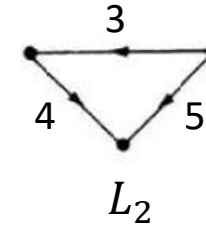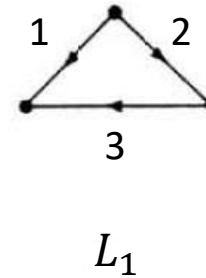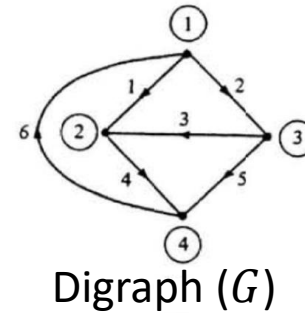

$$\underbrace{\begin{bmatrix} 1 & -1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 & -1 & 0 \\ 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & 1 \\ 1 & -1 & 0 & 1 & -1 & 0 \\ 1 & 0 & -1 & 0 & 1 & 1 \\ 0 & 1 & 1 & 1 & 0 & 1 \end{bmatrix}}_{\text{Loop matrix, } B_a} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \Rightarrow B_a v = 0$$

Set of equations in the loop matrix is linearly dependent.

Linear dependency: set of equations are linearly dependent if a linear combination of them is zero.

# Graph Theory—KVL Based on Loops

- Minimum set of loops that contains all the information related to KVL equations:

$$l = b - (n - 1)$$

$l$ : minimum number of loops for linearly independent KVL equations  
 $b$ : number of branches in digraph  
 $n$ : number of nodes in digraph

- For the digraph, minimum number of linearly independent equations:

$$l = 6 - (4 - 1) = 3 \longrightarrow \text{3 linearly independent equations contained all the information on the digraph} \longrightarrow \text{Choose only 3 loops (or KVL equations)}$$



$$\underbrace{\begin{bmatrix} 1 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 & -1 & 0 \\ 1 & 0 & 0 & 1 & 0 & 1 \end{bmatrix}}_{\text{Reduced Loop matrix, } B_R} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} \longrightarrow \begin{matrix} L_1, L_2, \text{ and } L_3 \text{ are chosen since they contain all} \\ \text{the information. Ignore rest of the loops.} \end{matrix}$$

$$B_R v = 0$$

Reduced loop matrix  $B_R$ :  $b - (n - 1)$  row and  $b$  columns
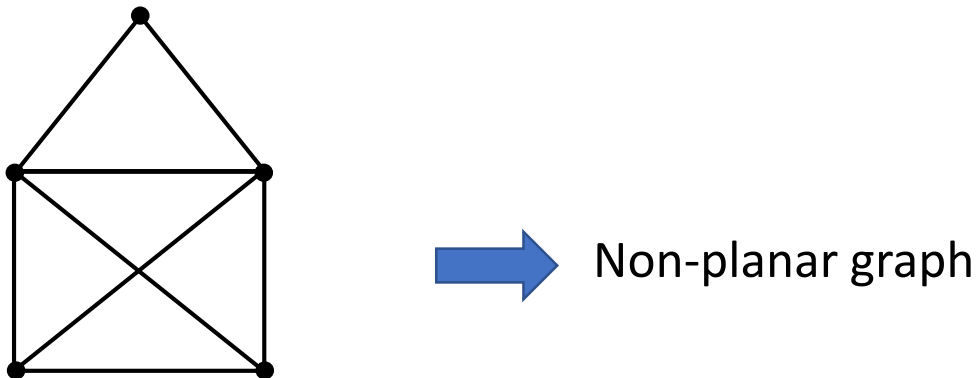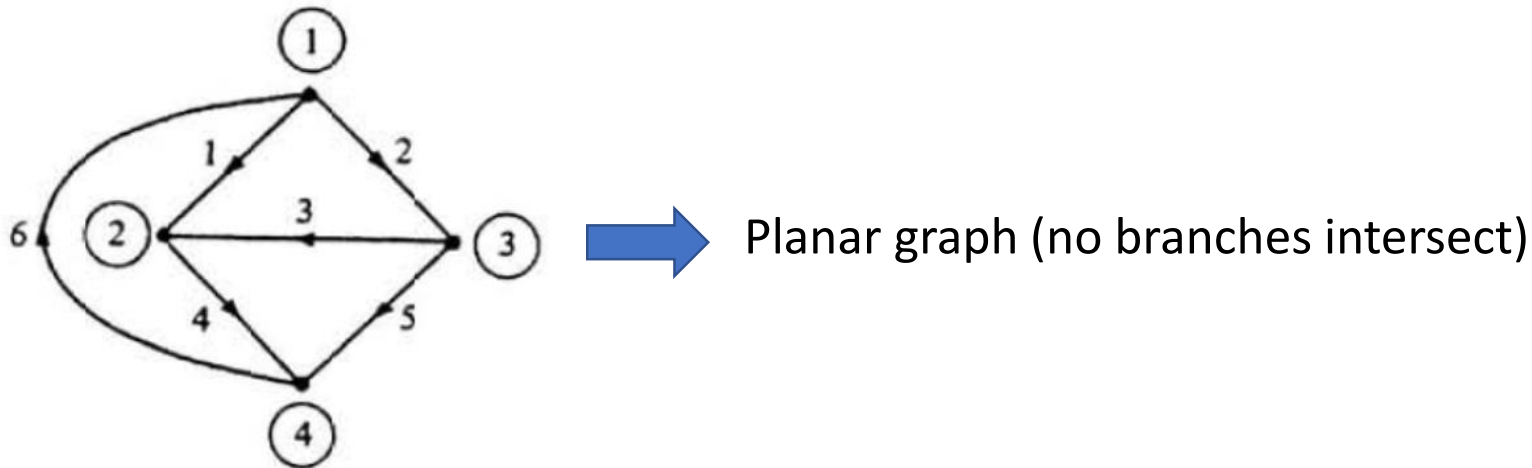
# Graph Theory—Planar Graph


- What is a planar graph?
  - A graph which can be drawn on a plane in such a way that no two branches intersect at a point which is not a node.
- Example of planar and non-planar graph:





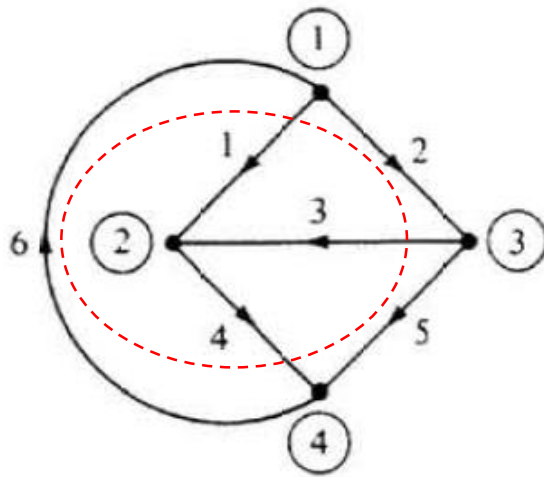
# Graph Theory—Mesh

- Mesh: a loop consisting of branches encircles nothing in its interior
- Outer mesh: a loop consisting of branches has nothing in its exterior



Graph  $G$

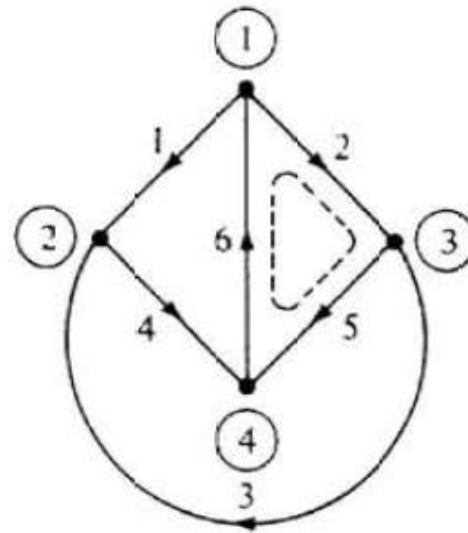


Graph  $G'$

- Graph  $G'$ : mesh (consisting of branches [2,5,6])
- Graph  $G$ : outer mesh (consisting of branches [2,5,6])
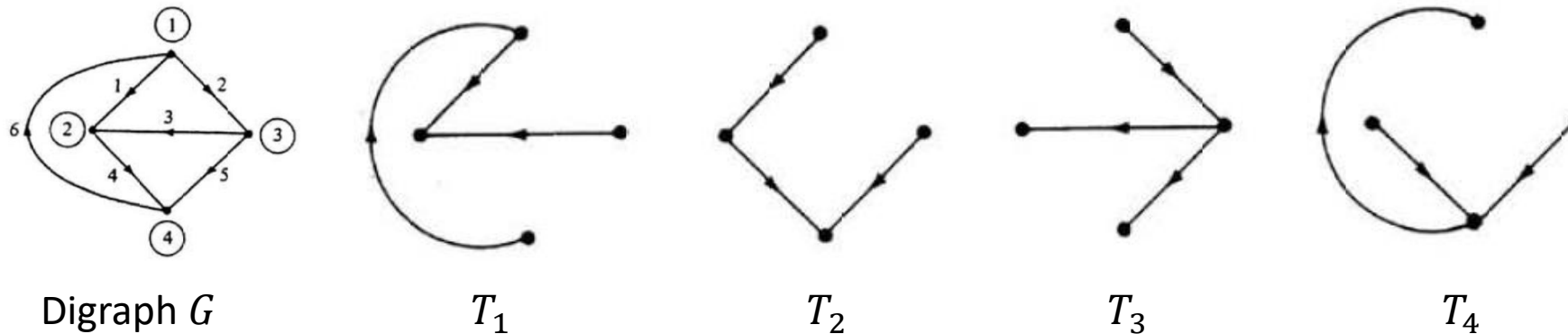
# Graph Theory—Tree

- Tree: one of the most important concept in graph theory
- Tree  $T$  of a connected digraph  $G$  is a subgraph which satisfy the following fundamental properties:
  - It is connected (there is a path from any point to any other point)
  - It contains all the nodes of the digraph
  - It has no loops
- Consider the following situation:



- $T_1, T_2, T_3$ , and  $T_4$  are four distinct trees of the digraph  $G$

$$T_1 = \{1, 3, 6\} \quad T_3 = \{2, 3, 5\}$$

$$T_2 = \{1, 4, 5\} \quad T_4 = \{4, 5, 6\}$$

Each tree consists of three branches

# Fundamental Theorem of Graph



- Basic terminology:
  - ❑ twig: branches belong to the tree. Also known as tree branches
  - ❑ Link: branches that do not belong to the tree. Also known as chord or chord branches
  - ❑ Example:  $T_1 = \{1,3,6\}$ ,  $T_1$  has 3 twigs (1,3,6) and 3 links (2,4,5)
- Given a connected digraph  $G$  with  $n$  nodes,  $b$  branches and a tree  $T$ ;
  - ❑ There is a unique path (disregard the branch orientation) along the tree between any pairs of nodes (tree is connected).
  - ❑ There are  $n - 1$  twigs and  $l = b - (n - 1)$  links.
  - ❑ Every twig of  $T$  along with some links defines a unique cut set, called the fundamental cut set associated with the twig.
  - ❑ Every link of  $T$  and the unique path on the tree between its two nodes constitute a unique loop, called the fundamental loop associated with the link.
- Statements mentioned above simply means how to obtain fundamental cut set associated with twig and fundamental loop associated with link from a given digraph.

# Fundamental Cut Set Associated with a Tree-KCL

- Consider the following digraph with  $b = 9$  and  $n = 6$
- First, pick (draw) a tree: solid dark line is a tree
- Second, determine twigs and links
  - twig:  $n - 1 = 6 - 1 = 5$  twigs (solid dark line)
  - Link:  $l = b - (n - 1) = 9 - 5 = 4$  links (thin solid line)
- Third, determine the fundamental cut set
  - Every twig of tree with some link defines a unique fundamental cut set
- Five fundamental cut sets as:


Cut set 1: {1,6}

Cut set 4: {4,7}

Cut set 2: {2,6,8,9}

Cut set 5: {5,9}

Cut set 3: {3,7,8,9}

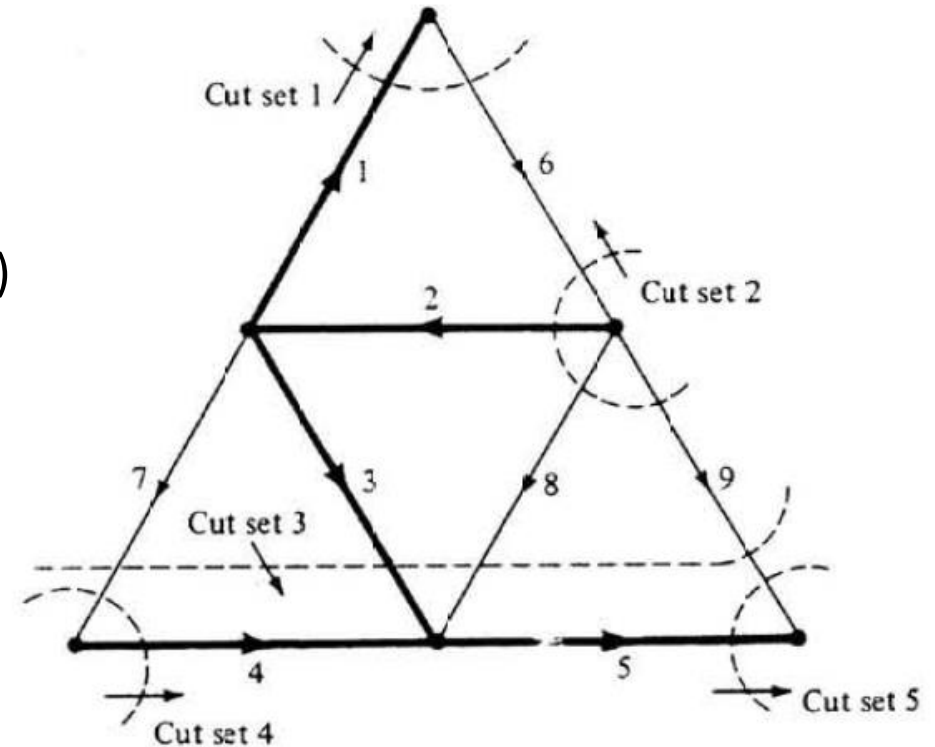

## Recall: Tree

It is connected

It contains all nodes of the digraph

It has no loops

# Fundamental Cut Set Associated with a Tree-KCL on Fundamental Cut Set

- KCL equations for five fundamental cut sets:

Cut set 1: {1,6}      Cut set 2: {2,6,8,9}      Cut set 3: {3,7,8,9}      Cut set 4: {4,7}      Cut set 5: {5,9}

$$\begin{array}{l}
 \text{Cut set 1:} \quad i_1 - i_6 = 0 \\
 \text{Cut set 2:} \quad i_2 - i_6 + i_8 + i_9 = 0 \\
 \text{Cut set 3:} \quad i_3 + i_7 + i_8 + i_9 = 0 \\
 \text{Cut set 4:} \quad i_4 - i_7 = 0 \\
 \text{Cut set 5:} \quad i_5 + i_9 = 0
 \end{array}
 \left. \vphantom{\begin{array}{l} \text{Cut set 1:} \\ \text{Cut set 2:} \\ \text{Cut set 3:} \\ \text{Cut set 4:} \\ \text{Cut set 5:} \end{array}} \right\}$$

$$\begin{array}{l}
 \text{Cut set 1:} \\
 \text{Cut set 2:} \\
 \text{Cut set 3:} \\
 \text{Cut set 4:} \\
 \text{Cut set 5:}
 \end{array}
 \begin{array}{c}
 \overbrace{\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & -1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & -1 & 0 & 1 & 1 \\ 0 & 0 & 1 & 0 & 0 & 0 & 1 & 1 & 1 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 1 \end{bmatrix}}^Q \\
 \underbrace{\hspace{10em}}_{n-1 \text{ twigs}} \quad \underbrace{\hspace{10em}}_{\ell \text{ links}}
 \end{array}
 \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ \cdot \\ \cdot \\ i_9 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$1_{n-1}$  (unit matrix)       $Q_\ell$

$Qi = 0$  where  $Q: (n - 1) \times b$   
fundamental cut set matrix

$$Q = [1_{n-1}, Q_\ell]$$

# KVL Equations Using Twig Voltages

- Let the twig voltages be:

$v_{t1}, v_{t2}, v_{t3}, v_{t4}, v_{t5}$  (5 twigs).

$v_1 = v_{t1}, v_2 = v_{t2}, v_3 = v_{t3}, v_4 = v_{t4}, v_5 = v_{t5}$

- Four fundamental loops defined by each link
  - Fundamental loop contains only one link and some twigs
  - Apply KVL for fundamental loops defined by four links

$$v_6 + v_2 + v_1 = 0 \Rightarrow v_6 = -v_1 - v_2 = -v_{t1} - v_{t2}$$

$$v_7 + v_4 - v_3 = 0 \Rightarrow v_7 = v_3 - v_4 = v_{t3} - v_{t4}$$


$$v_8 - v_3 - v_2 = 0 \Rightarrow v_8 = v_2 + v_3 = v_{t2} + v_{t3}$$

$$v_9 - v_5 - v_3 - v_2 = 0 \Rightarrow v_9 = v_2 + v_3 + v_5 = v_{t2} + v_{t3} + v_{t5}$$

- In general, matrix can be written as:

$$v = Q^T v_t$$

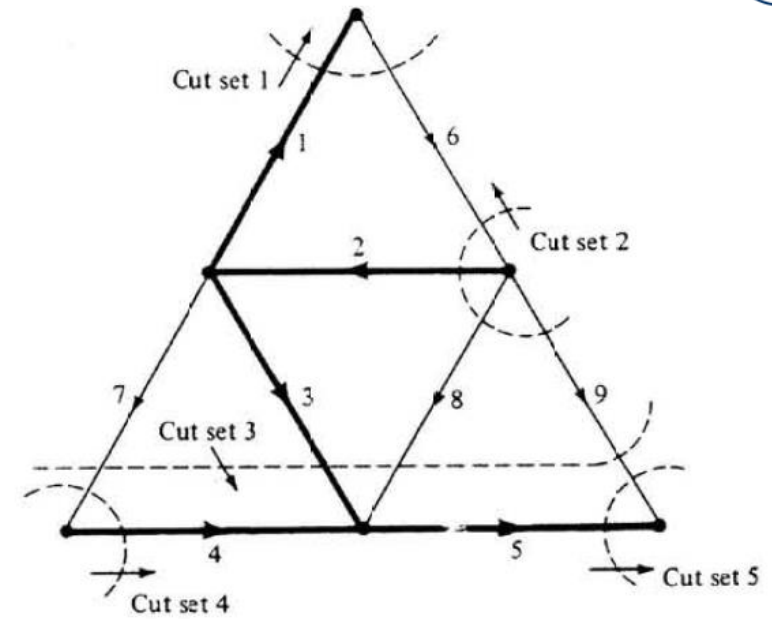$v_t$ : twig voltage vector  
 $Q^T$ : transpose of fundamental cut-set matrix



$$\begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_9 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \\ -1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 \\ 0 & 1 & 1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_{t1} \\ v_{t2} \\ v_{t3} \\ v_{t4} \\ v_{t5} \end{bmatrix}$$

$\underbrace{\hspace{10em}}_{n-1}$

# Fundamental Loop Matrix Associated with Tree


- Determine the KVL equations based on fundamental loops
- Four fundamental loops
- Apply KVL to each fundamental loop:

Loop 1:  $v_6 + v_2 + v_1 = 0$

Loop 2:  $v_7 + v_4 - v_3 = 0$

Loop 3:  $v_8 - v_3 - v_2 = 0$

Loop 4:  $v_9 - v_5 - v_3 - v_2 = 0$

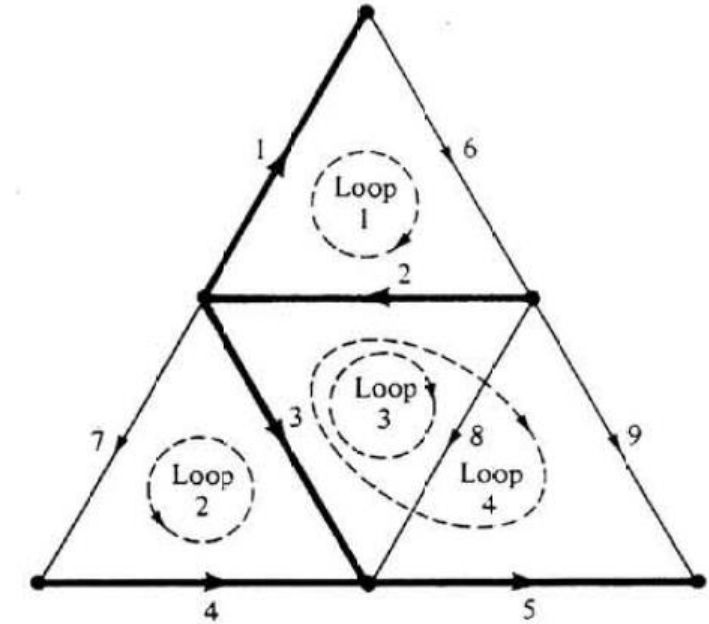

Reference direction of each loop is defined by the direction of its associated link

$$\begin{array}{c} \ell \text{ loops} \end{array} \begin{array}{c} B \\ \left[ \begin{array}{ccccc|cccc} 1 & 1 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & -1 & -1 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & -1 & -1 & 0 & -1 & 0 & 0 & 0 & 1 \end{array} \right] \begin{array}{c} \left[ \begin{array}{c} v_1 \\ v_2 \\ v_3 \\ \cdot \\ \cdot \\ \cdot \\ v_9 \end{array} \right] = \left[ \begin{array}{c} 0 \\ 0 \\ 0 \\ 0 \end{array} \right] \end{array} \Rightarrow Bv = 0$$

$\underbrace{\hspace{10em}}_{n-1 \text{ twigs}} \quad \underbrace{\hspace{10em}}_{\ell \text{ links}}$

$$B = [B_t, 1_\ell]$$

$1_\ell$ : unit matrix

$B_t$ : submatrix of  $\ell$ (loop) rows and  $n-1$  columns

$B$ :  $(\ell \times b)$  fundamental loop matrix associated with the tree  $T$