



BLG 231E - Digital Circuits

Assignment 4


Due Date: Friday, December 16, 2021, 23:59.

- Please **write and draw neatly**.
- Please prepare your homework using the Logisim tool. Points will be taken off for handwritten submissions.
- **Consequences of plagiarism:** Any cheating will be subject to disciplinary action.
- **No late submissions** will be accepted.
- **Submissions:** Submit your **solution as a Logisim .circ file** to Ninova. Please **write your full name** (first name and last name) **and Student ID** into your solution file.

If you have any questions, please e-mail **Mert Sülük** (suluk20@itu.edu.tr).

The combinational circuit shown on the right performs arithmetic operations on three 4-bit integers, A, B, and C based on the values of inputs x and y, as explained in the table given below. We ignore carry, borrow, and overflows for this circuit.

xy	Operation
00	$Z = A + B$
01	$Z = B$
10	$Z = A - C$
11	$Z = C$

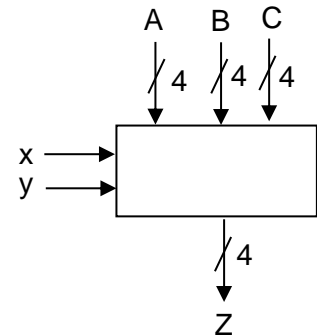

Design this circuit using **only a single** parallel adder and other necessary logic units (i.e., gates and devices that were explained in the lectures). Use the fewest possible number of logic units with smallest possible sizes to make your circuit design as simple as possible.

Implement and test the circuit using the Logisim tool. Do not show the internal structure of the parallel adder; show it only as a block. Fully label all inputs and outputs. Write your name and student ID at the top of the .circ file.