

Experiment 1.1.

We will examine forward active mode of BJT transistor in this experiment. In case of $V_{BE} > 0$ and

$V_{BC} < 0$, collector current will be;

$$I_C \cong I_S e^{V_{BE}/V_T}$$

$$I_C = \beta_F I_B$$

In order to obtain these 2 characteristics, set up the common emitter configuration in Figure 1. V_C will be 5V and R_3 will be short circuit. BJT transistor is BC238 and the model file of this transistor is at end of the Experiment 1.2. Fill the Table 1 by changing R_1 value. Sweep R_1 from 1k ohm to 1M ohm.

Different I_B and/or V_{BE} values can be obtained by changing R_1 resistance in the circuit. Write your measurement result to Table 1. Then draw the graphics in Figure 2 which shows us relationship between $I_C - V_{BE}$ and $I_C - I_B$. You can draw graphs by using Excel.

Note: You can change resistor value in LTspice so you can use resistor instead of potentiometer.

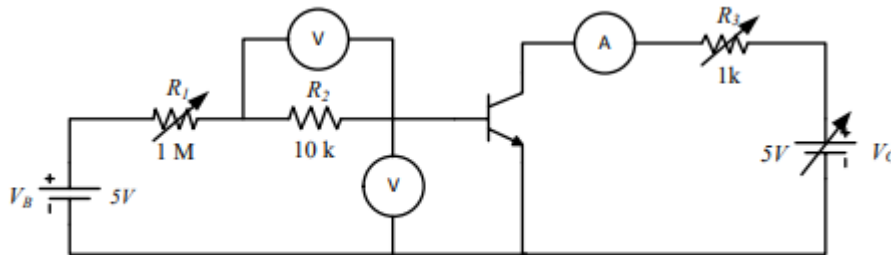


Figure 1: Common emitter configuration

Introduction to Electronics Laboratory
Experiment 2
Extraction of DC Characteristics of BJT and MOSFET



Table 1: Measurement results of experiment 1.1

| R_1 | V_{BE} | I_C | V_{R2} | I_B | β |
|-------|----------|-------|----------|-------|---------|
| | | | | | |
| | | | | | |
| | | | | | |
| | | | | | |
| | | | | | |
| | | | | | |
| | | | | | |
| | | | | | |
| | | | | | |
| | | | | | |
| | | | | | |

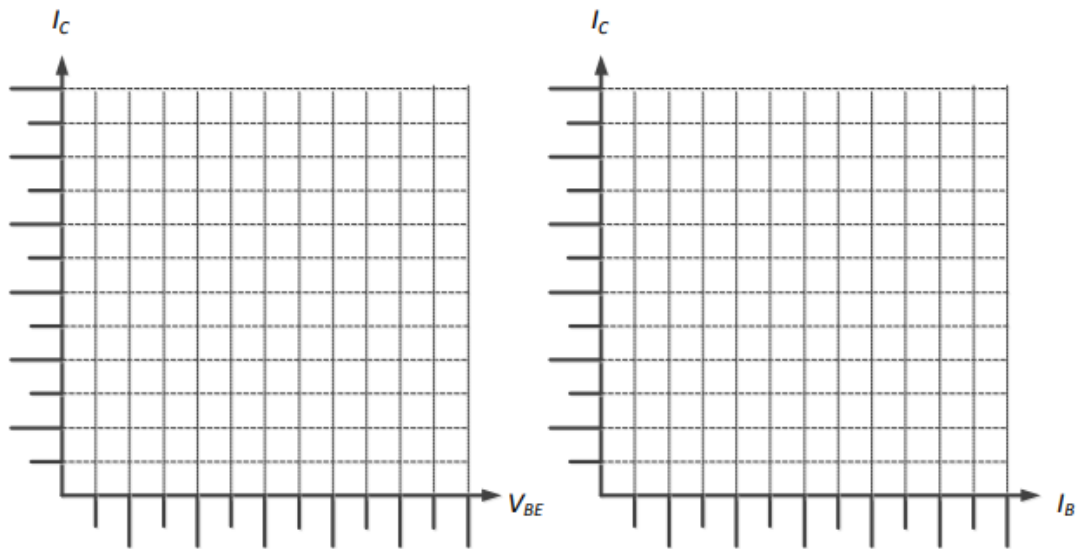


Figure 2: $I_C - V_{BE}$ and $I_C - I_B$ graphs

Experiment 1.2.

In this experiment we will examine the comparison between different operating modes of BJT transistor. For forward active mode you can choose an average value from R_1 values from Table 1 and write measurement results for this R_1 to Table 2.

For reverse active mode, switch connections between collector and emitter nodes and repeat measurements.

For saturation mode, make R_1 short circuit and connect R_3 as 1k ohm. Thus the transistor will enter saturation point ($V_{CE} < 0$). Write your results to Table 2.


Table 2: forward active, reverse active and saturation mode

| | V_{BE} | V_{CE} | I_B | I_C | β |
|---------------------|----------|----------|-------|-------|---------|
| Forward active mode | | | | | |
| Reverse active mode | | | | | |
| Saturation | | | | | |

The Model for BC238

```
.MODEL BC238 NPN (  
+IS =1.8E-14 ISE=5.0E-14 NF =.9955 NE =1.46 BF =400  
+BR =35.5 IKF=.14 IKR=.03 ISC=1.72E-13 NC =1.27 NR =1.005 RB =.56 RE =.6  
+RC =.25 VAF=80 VAR=12.5 CJE=13E-12 TF =.64E-9 CJC=4E-12 TR =50.72E-9  
+VJC=.54 MJC=.33 )
```

Use the MOSFET model at the end of the Experiment 2.5. Set $W = 160\mu$ and $L = 2\mu$.

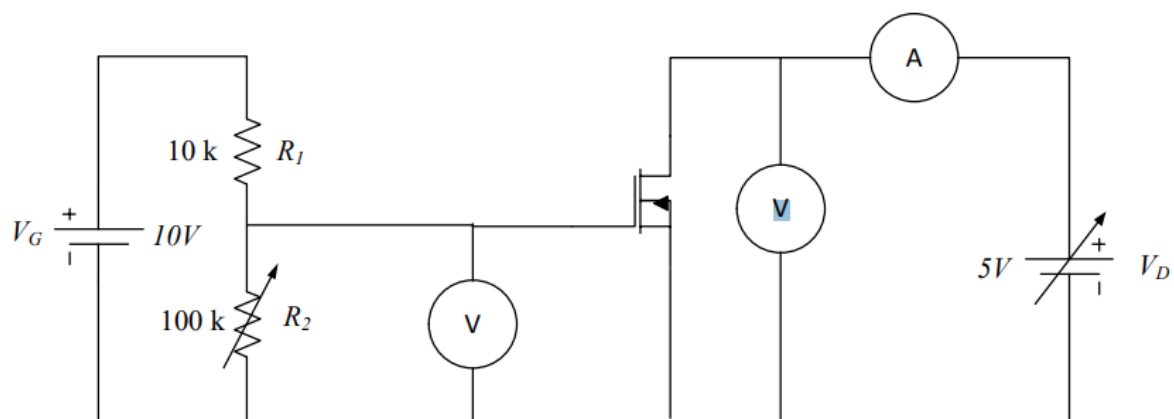Table 3: $V_{GS} - I_D$ values of Experiment 1.3[illegible]

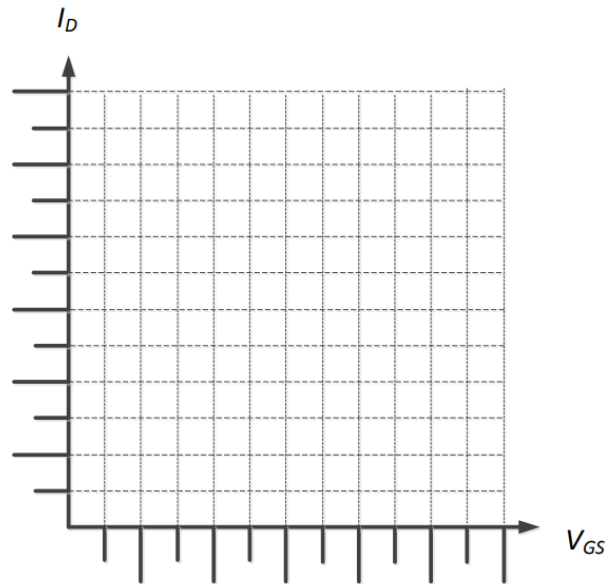


Figure 4: $I_D - V_{GS}$ curve

Experiment 1.4.

Choose V_G as 5V and R_2 as 100k Ω in Figure 3. Since R_2 is constant, V_{GS} remains constant. Sweep V_D value from 0V to 10V and draw $I_D - V_{DS}$ curve in Figure 5. Indicate different operation regions in $I_D - V_{GS}$ curve. Fill in Table 4.

Table 4: $V_{DS} - I_D$ values of Experiment 1.4[illegible]

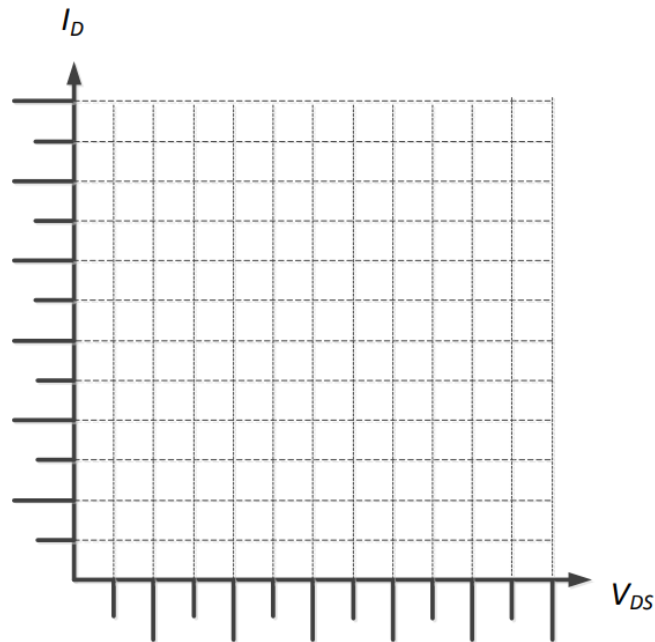


Figure 5: $I_D - V_{DS}$ curve

```
.MODEL cd4007n NMOS (  
+LEVEL = 49 VERSION = 3.3 TNOM = 23  
+TOX = 1e-07 XJ = 1e-06 NCH = 2e+16  
+VTH0 = 1.14098 K1 = 2.12491 K2 = 0.2  
+U0 = 0.0165798 UA = 1e-12 UB = 1.31485e-16  
+UC = 3.45708e-09 VSAT = 189307 A0 = 2  
+AGS = 0.481611 B0 = 5.4717e-06 B1 = 0  
+KETA = 0.034434 A1 = 0.0462264 A2 = 0.926415  
+RDSW = 100 WR = 1 WINT = 1e-06  
+LINT = 1e-07 VOFF = -0.0394991 NFACTOR = 0.320755  
+CIT = 0 CDSC = 0.00024 CDSCD = 0  
+CDSCB = 0 ETA0 = 0 ETAB = 0  
+PCLM = 0.001 PDIBLC1 = 0 PDIBLC2 = 0.0086  
+PDIBLCB = 0 DROUT = 0.56 PVAG = 1.03774  
+DELTA = 0.0915943 IS = 2.15472e-13 MOBMOD = 1  
+CAPMOD = 2 CGDO = 2.3e-10 CGSO = 2.3e-10  
+CGBO = 1.065e-10 CJ = 0.000344 PB = 0.95  
+MJ = 0.5 CJSW = 2.07e-10 PBSW = 0.95  
+MJSW = 0.5 NOFF = 1 ACDE = 1 +MOIN = 15 )
```