

**ISTANBUL TECHNICAL UNIVERSITY**  
**COMPUTER ENGINEERING DEPARTMENT**

**BLG 242E**  
**DIGITAL CIRCUITS LABORATORY**  
**HOMEWORK REPORT**

**HOMEWORK NO** : 1  
**HOMEWORK DATE** : 10.03.2023  
**LAB SESSION** : FRIDAY - 10.30  
**GROUP NO** : G3

**GROUP MEMBERS:**

150200000 : Ahmet Emre Buz  
150200001 : Mustafa Can Çalışkan

**SPRING 2023**

# Contents

<b>1</b>	<b>INTRODUCTION</b>	<b>1</b>
<b>2</b>	<b>PRELIMINARY</b>	<b>1</b>
<b>3</b>	<b>EXPERIMENT</b>	<b>8</b>
3.1	PART 1 . . . . .	8
3.2	PART 2 . . . . .	14
3.3	PART 3 . . . . .	15
3.4	PART 4 . . . . .	16
3.5	PART 5 . . . . .	17
3.6	PART 6 . . . . .	19
3.7	PART 7 . . . . .	20
3.8	PART 8 [7 points] . . . . .	21
3.9	PART 9 . . . . .	21
3.10	PART 10 . . . . .	22
3.11	PART 11 . . . . .	23
<b>4</b>	<b>CONCLUSION</b>	<b>24</b>
	<b>REFERENCES</b>	<b>25</b>

# 1 INTRODUCTION

In this experiment, we implemented and simulated desired designs using Verilog.

## 2 PRELIMINARY

For the given function

$$F(a, b, c, d) = \cup_1(1, 2, 5, 6, 9, 10, 13, 14) + \cup_d(4)$$

- Prime implicants using Karnaugh diagram:

 


Figure 1: Karnaugh Map (created using the tool provided by [boolean-algebra.com](http://boolean-algebra.com))

- Prime implicants using Quine-McCluskey method:

Input		First Comparasion		Second Comparasion	
0	m0 0000	0	(2, 0) 00-0 (8, 0) -000 (4, 0) 0-00	0	(10, 8, 2, 0) -0-0 (6, 4, 2, 0) 0--0
1	m2 0010 m8 1000 d4 0100	1	(6, 2) 0-10 (10, 2) -010 (10, 8) 10-0 (6, 4) 01-0		
2	m6 0110 m10 1010	2	(7, 6) 011- (11, 10) 101-		
3	m7 0111 m11 1011	3	(15, 7) -111 (15, 11) 1-11		
4	m15 1111				
Prime Implicants					
(10, 8, 2, 0) -0-0 (6, 4, 2, 0) 0--0					
(7, 6) 011- (11, 10) 101- (15, 7) -111 (15, 11) 1-11					

Figure 2: Quine-McCluskey Tables (created using the tool provided by quinemccluskey.com)

- Prime implicant chart and expression with the minimum cost:

	-0-0	0--0	011-	101-	-111	1-11
0	X	X				
2	X	X				
6		X	X			
7			X		X	
8	X					
10	X			X		
11				X		X
15					X	X
<b>COST</b>	<b>6</b>	<b>6</b>	<b>7</b>	<b>7</b>	<b>6</b>	<b>6</b>

Figure 3: Prime implicant chart (created using the tool provided by quinemccluskey.com)

	0--0	011-	101-	-111	1-11
6	X	X			
7		X		X	
11			X		X
15				X	X
COST	6	7	7	6	6

Figure 4: Prime implicant chart (created using the tool provided by [quinemcccluskey.com](http://quinemcccluskey.com))

Expression with the minimum cost:

$$F(a, b, c, d) = acd + a'bc + b'd'$$

- Lowest cost expression using NOT, AND, and OR gates:

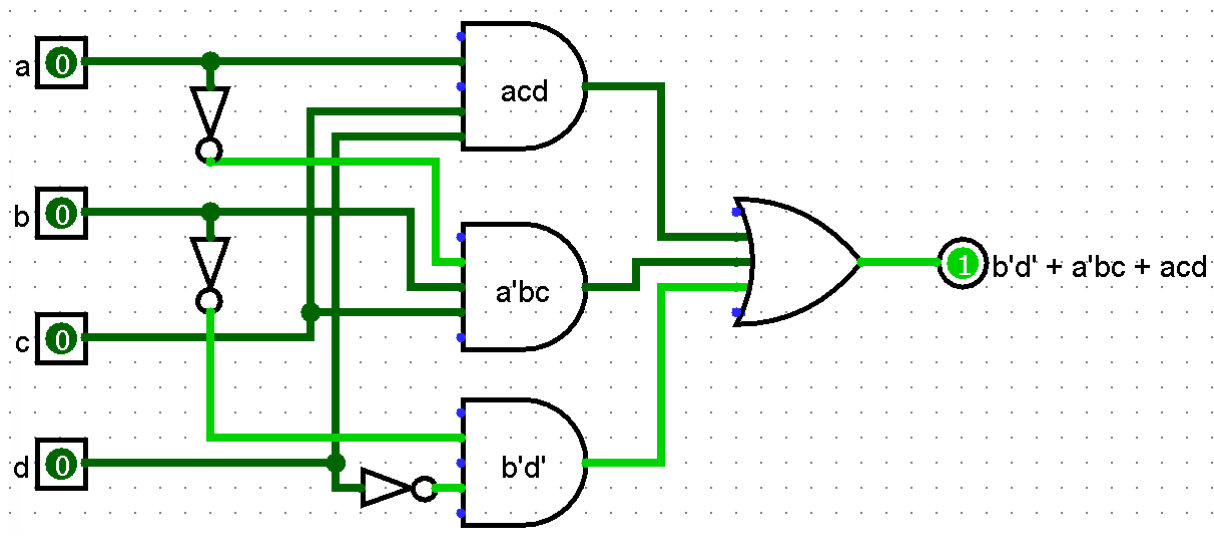


Figure 5: Design

<b>a</b>	<b>b</b>	<b>c</b>	<b>d</b>	<b>bdAbcAc d</b>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Figure 6: Truth Table of Design

- Lowest cost expression using only NAND gates:

 


Figure 7: Design

a	b	c	d	bdAbcAc d
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Figure 8: Truth Table

- Lowest cost expression using a single 8:1 Multiplexer, AND, OR and NOT gates:

 


Figure 9: Design

<i>b</i>	<i>d</i>	<i>a</i>	<i>c</i>	$((\neg b \wedge \neg d) \vee ((\neg a \wedge b) \wedge c)) \vee ((a \wedge c) \wedge d)$	
1	1	1	1	1	
1	1	1	0	0	<b>C</b>
1	1	0	1	1	
1	1	0	0	0	<b>C</b>
1	0	1	1	0	
1	0	1	0	0	<b>0</b>
1	0	0	1	1	
1	0	0	0	0	<b>C</b>
0	1	1	1	1	
0	1	1	0	0	<b>C</b>
0	1	0	1	0	
0	1	0	0	0	<b>0</b>
0	0	1	1	1	
0	0	1	0	1	<b>1</b>
0	0	0	1	1	
0	0	0	0	1	<b>1</b>

Figure 10: Truth Table (created using the tool provided by emathhelp.net)

For the given function

$$F(a, b, c) = a'bc + ab'c$$

- Expression using ONE single 3:8 decoder, 2-input OR gates:

 


Figure 11: Design



<i>a</i>	<i>b</i>	<i>c</i>	$((\neg a \wedge b) \wedge c) \vee ((a \wedge \neg b) \wedge c)$
1	1	1	0
1	1	0	0
1	0	1	1
1	0	0	0
0	1	1	1
0	1	0	0
0	0	1	0
0	0	0	0

Figure 12: Truth Table (created using the tool provided by emathhelp.net)

For the given function

$$F(a, b, c) = abc' + ab$$

- Expression using ONE single 3:8 decoder, 2-input OR gates:

 


Figure 13: Design

$a$	$b$	$c$	$((a \wedge b) \wedge \neg c) \vee (a \wedge b)$
1	1	1	1
1	1	0	1
1	0	1	0
1	0	0	0
0	1	1	0
0	1	0	0
0	0	1	0
0	0	0	0

Figure 14: Truth Table (created using the tool provided by emathhelp.net)

### 3 EXPERIMENT

#### 3.1 PART 1

 


Figure 15: AND Gate Simulation Output

 


Figure 16: AND Gate Circuit

 


Figure 17: OR Gate Simulation Output

 


Figure 18: OR Gate Circuit

 


Figure 19: NOT Gate Simulation Output

 


Figure 20: NOT Gate Circuit

 


Figure 21: XOR Gate Simulation Output

 


Figure 22: XOR Gate Circuit

 


Figure 23: NAND Gate Simulation Output



Figure 24: NAND Gate Circuit

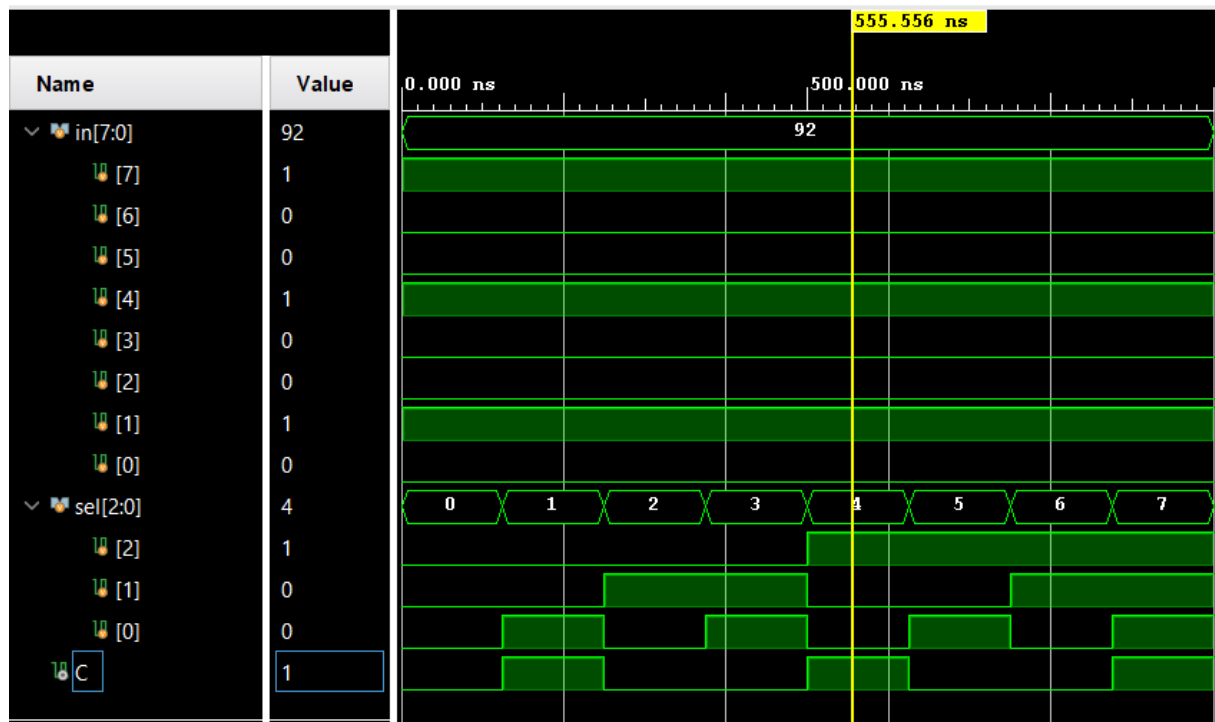


Figure 25: 8:1 Multiplexer Simulation Output

 


Figure 26: 8:1 Multiplexer Circuit

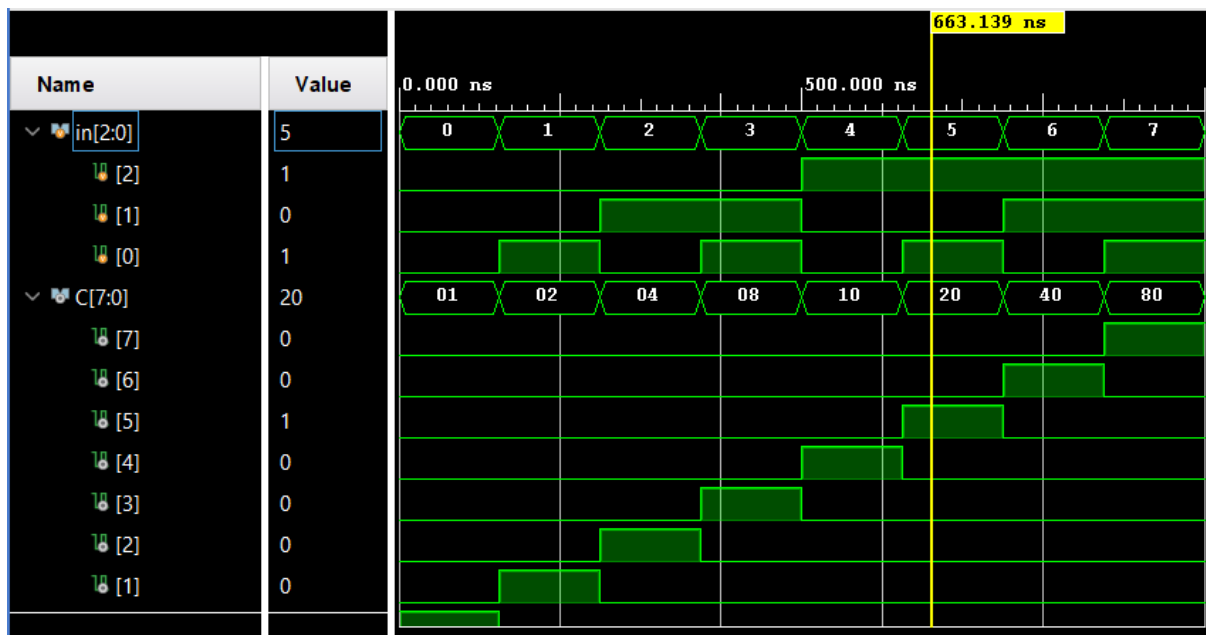


Figure 27: 3:8 Decoder Simulation Output



Figure 28: 3:8 Decoder Circuit

## 3.2 PART 2

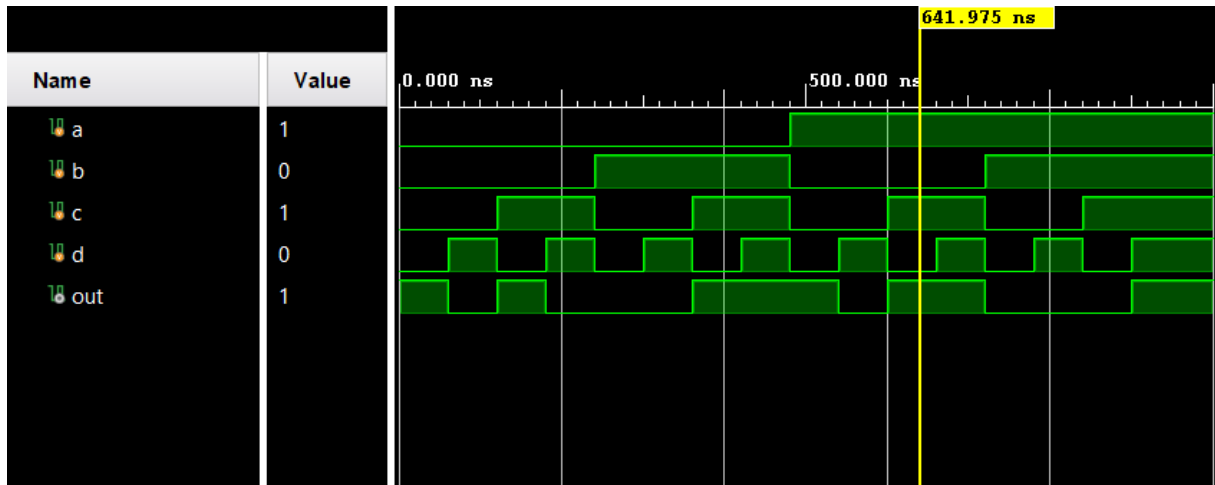


Figure 29: Part 2 Simulation Output

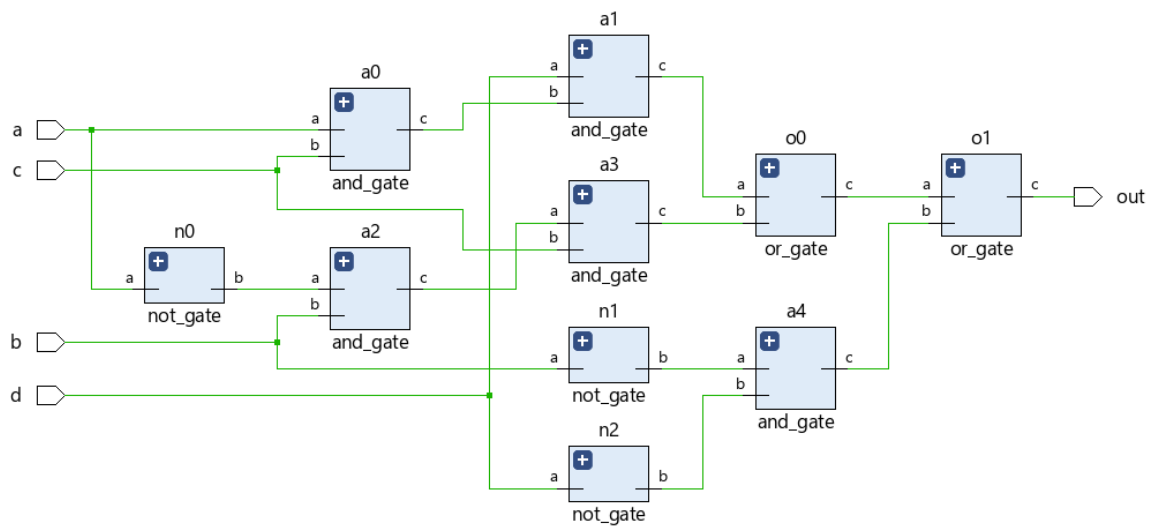


Figure 30: Circuit of Part 2



### 3.3 PART 3

 


Figure 31: Part 3 Simulation Output

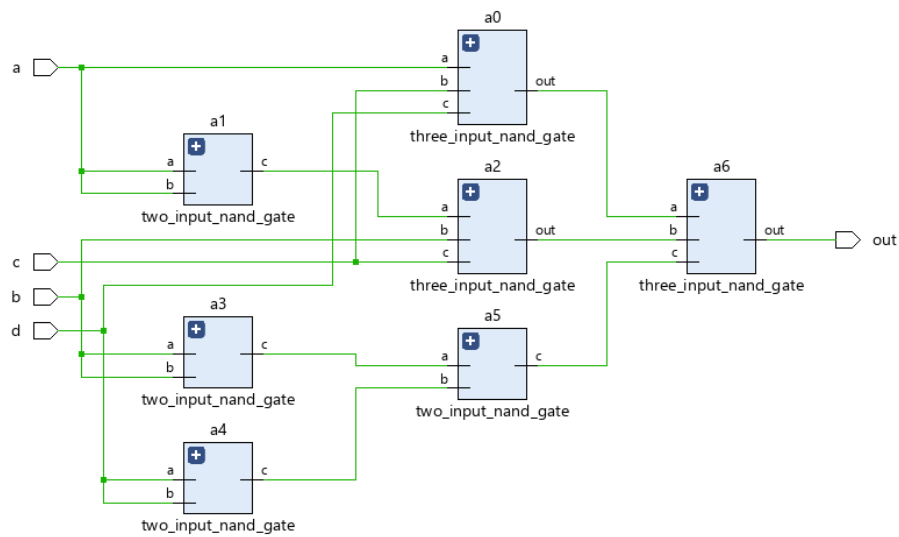


Figure 32: Circuit of Part 3

### 3.4 PART 4

 


Figure 33: Part 4 Simulation Output

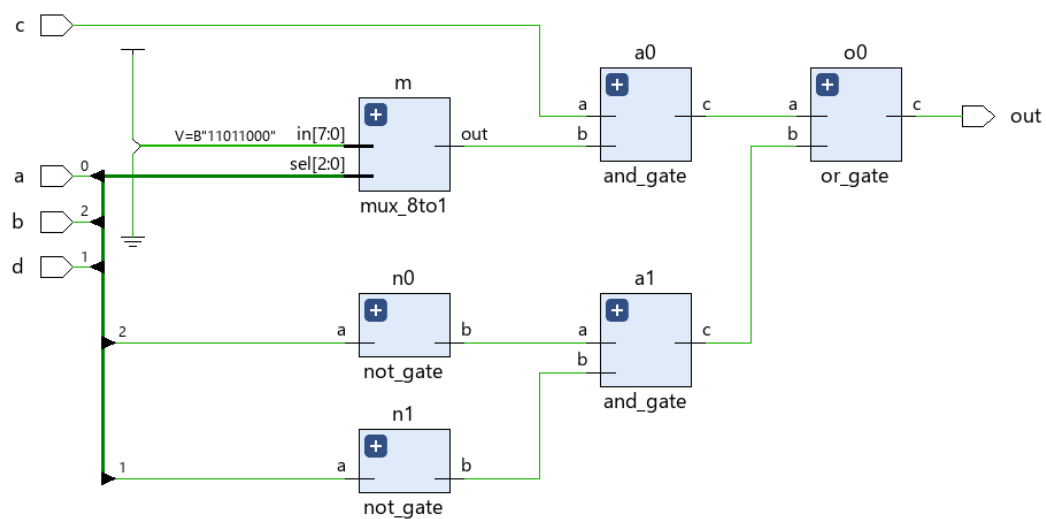


Figure 34: Circuit of Part 4

### 3.5 PART 5

- Equation 2

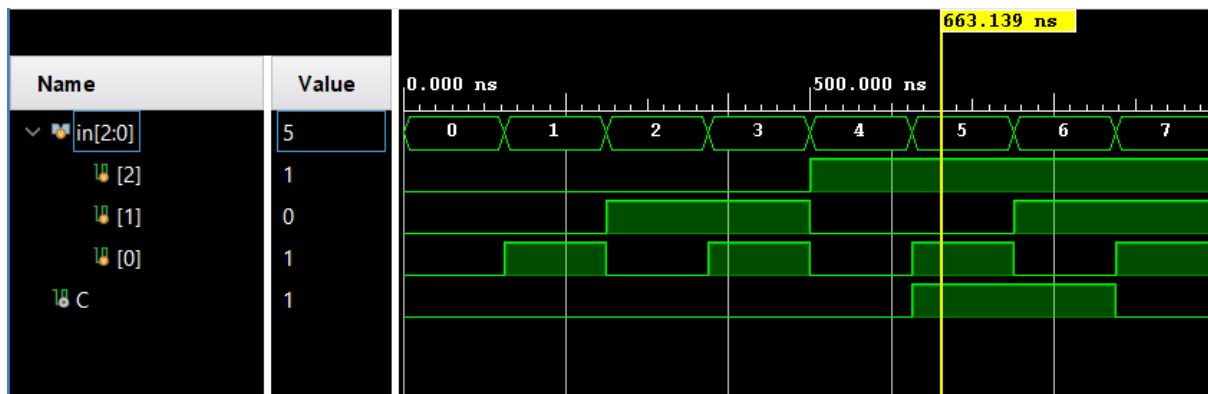


Figure 35: Simulation Output

 


Figure 36: Circuit

- Equation 3

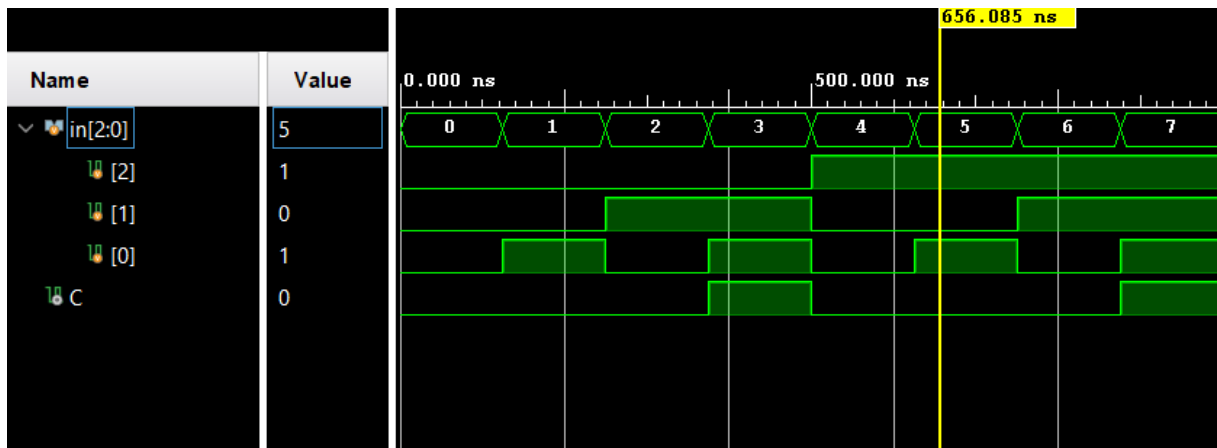


Figure 37: Simulation Output

 


Figure 38: Circuit

### 3.6 PART 6

 


Figure 39: Simulation Output of Half Adder

 


Figure 40: Circuit of Half Adder

### 3.7 PART 7

 


Figure 41: Simulation Output of 1-bit Full Adder

 


Figure 42: Circuit of 1-bit Full Adder

### 3.8 PART 8 [7 points]

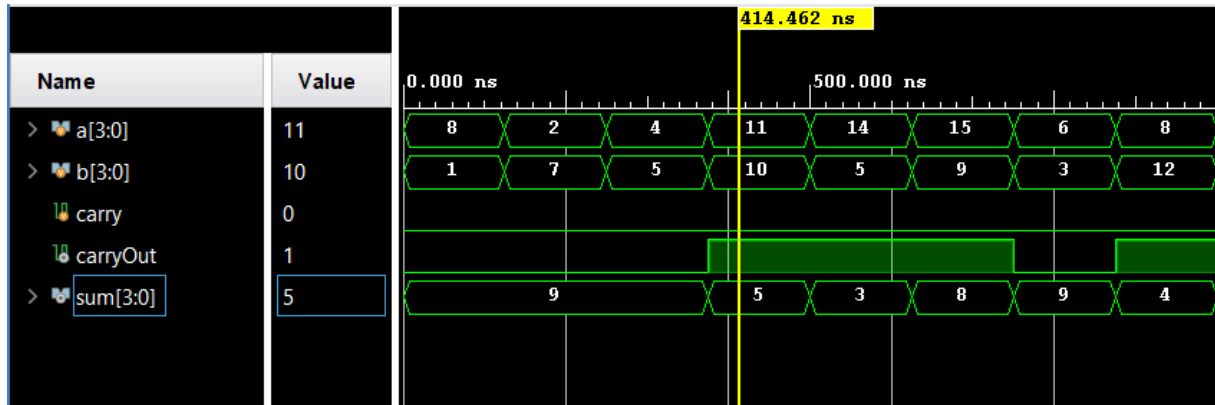


Figure 43: Simulation Output of 4-bit Full Adder

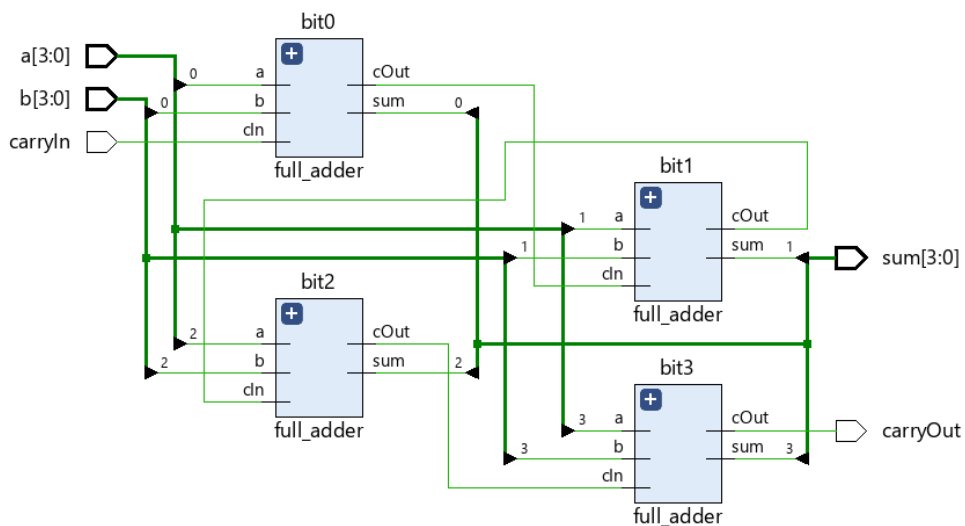


Figure 44: Circuit of 4-bit Full Adder

### 3.9 PART 9

 


Figure 45: Simulation Output of 8-bit Full Adder

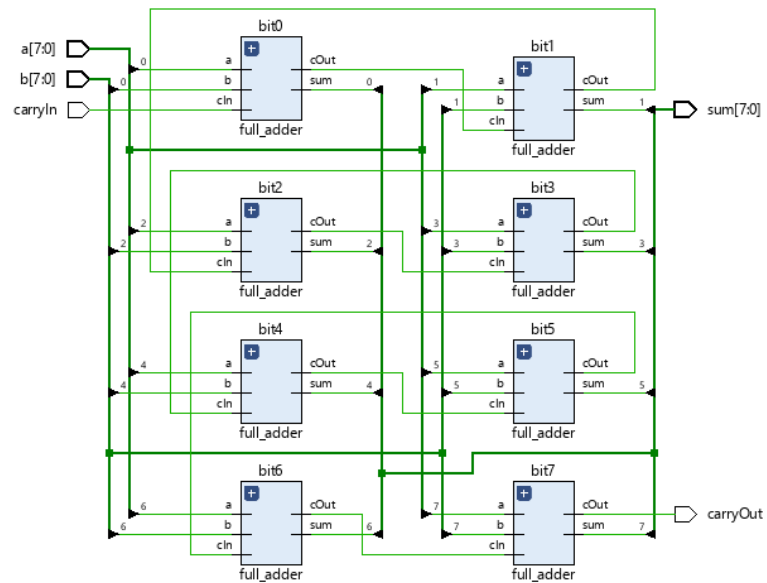


Figure 46: Circuit of 8-bit Full Adder

### 3.10 PART 10

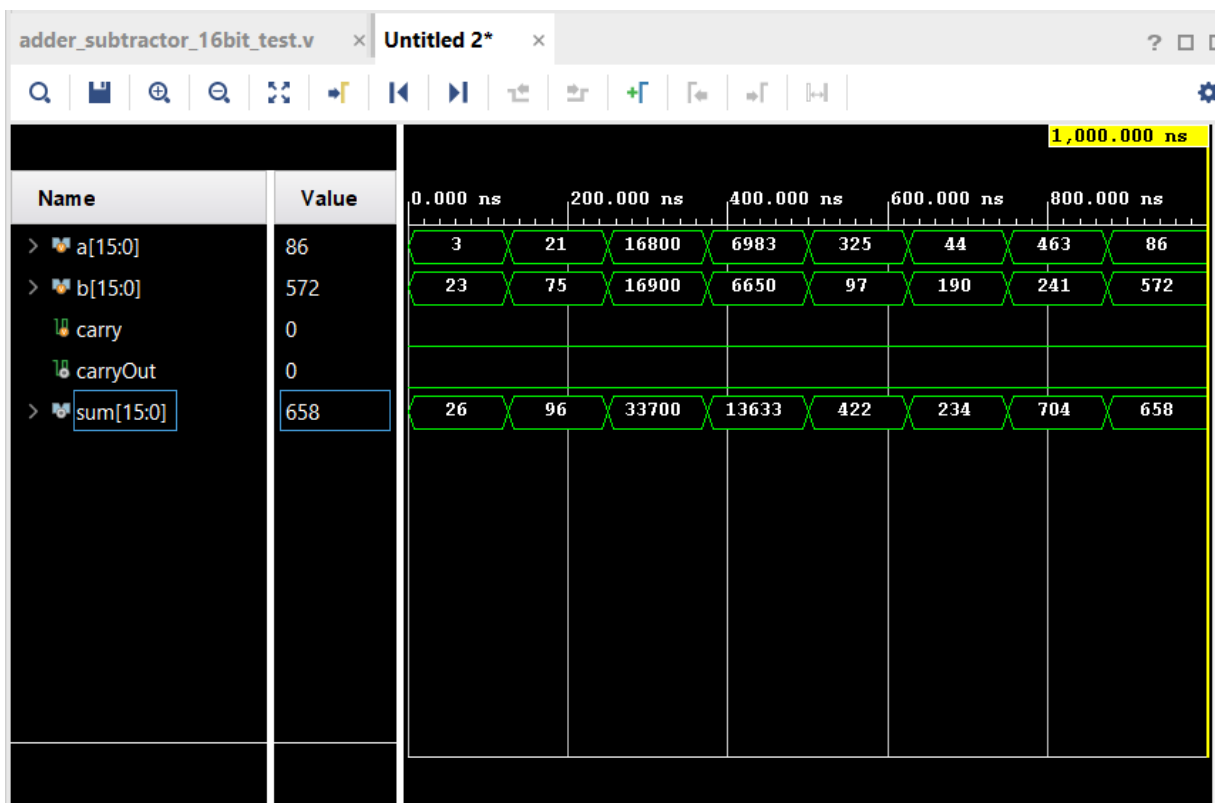


Figure 47: Simulation Output of 16-bit Adder-Subtractor



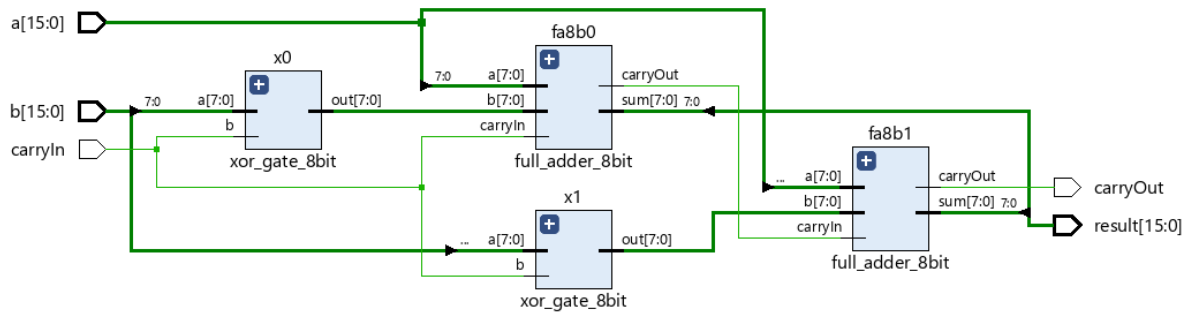


Figure 48: Circuit of 16-bit Adder-Subtractor

### 3.11 PART 11

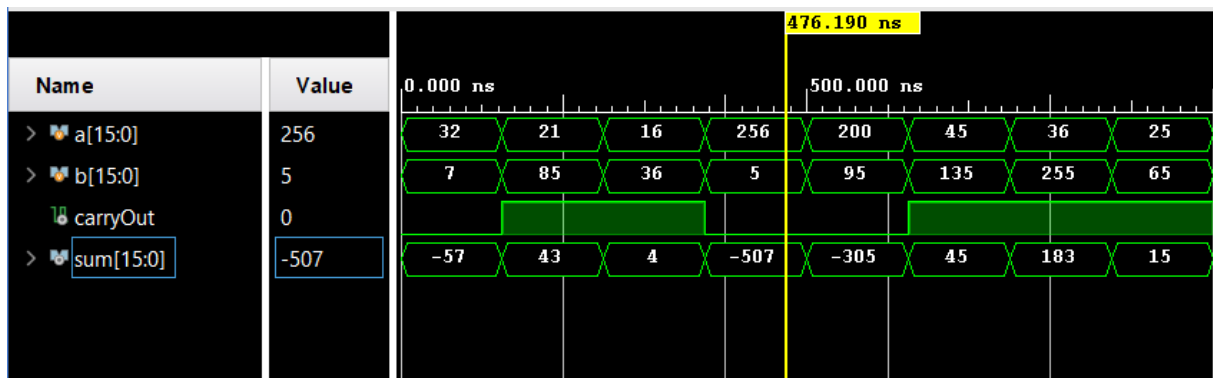


Figure 49: Simulation Output of B - 2A Expression

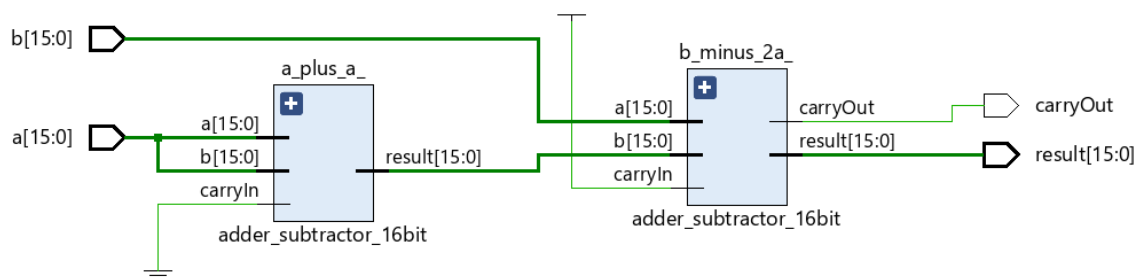


Figure 50: Circuit of B - 2A Expression

## 4 CONCLUSION

In this experiment, we implemented and simulated desired designs using Verilog.

## REFERENCES