

EHB 211E

Basics of Electrical Circuits

Asst. Prof. Onur Kurt

State-Space Representation and Nonlinear Circuit Elements



- **What is state-space representation?**
 - ❑ Mathematical model of a physical system as a set of input, output, and state variable related by 1st order differential equations.
 - ❑ In other words, a system by a series of 1st order differential equations. Highest order of derivative is 1st derivative.
 - ❑ It is also known as state-space model.
- **Why do we use state-space representation?**
 - ❑ State-space representation allows us to understand complex systems.
 - ❑ As systems become more complex, representing them with transfer function becomes harder.
 - ❑ More useful way to solve complex systems as it can handle multiple inputs and outputs as opposed to transfer function.
- **State-space representation of a system is given by**

$$\dot{\mathbf{x}}(t) = \mathbf{A}\mathbf{x}(t) + \mathbf{B}\mathbf{u}(t)$$

$$\mathbf{y}(t) = \mathbf{C}\mathbf{x}(t) + \mathbf{D}\mathbf{u}(t)$$

\mathbf{x} : state vector

$\dot{\mathbf{x}}$: derivative of state vector


\mathbf{u} : input vector

\mathbf{y} : output vector

$\mathbf{A}, \mathbf{B}, \mathbf{C}, \mathbf{D}$: matrixes

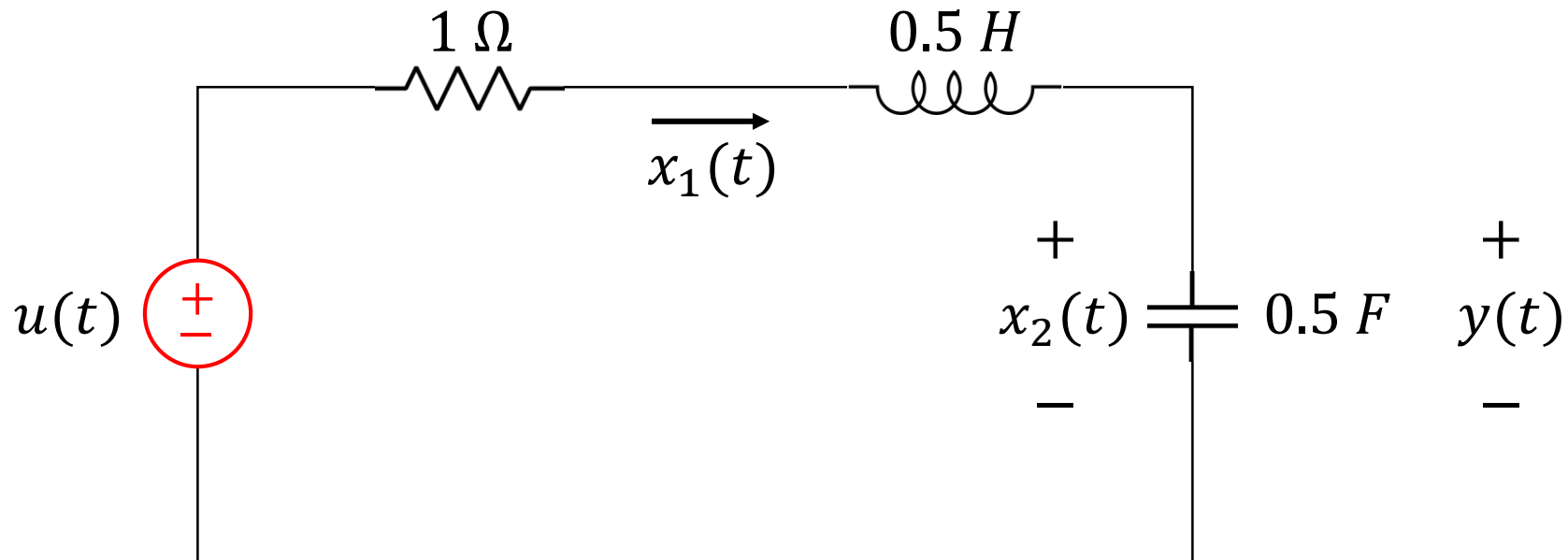Example 1

Consider the circuit shown below. Represent the system in a state-space form (adapted from Assoc. Prof. Onur Ferhanoğlu).



Solution:

Apply KVL: $-u + V_R + V_L + V_C = 0 \longrightarrow$ Input, state variable, and output as function of time. Drop (t) for simplicity.

By definition, inductor: $V_L = L \frac{di}{dt}$

By definition, capacitor: $i_C = C \frac{dv}{dt}$

$x_1(t)$: current and $x_2(t)$: voltage across capacitor.

Solution

$$V_R = x_1 \times 1 = x_1$$

$$V_L = L \frac{di}{dt} \Rightarrow V_L = 0.5 \frac{di}{dt} \Rightarrow \frac{di}{dt} = \frac{d}{dt}(x_1) \Rightarrow \frac{di}{dt} = \dot{x}_1 \Rightarrow V_L = 0.5 \dot{x}_1$$


$$i_C = C \frac{dv}{dt} \Rightarrow i_C = 0.5 \frac{dv}{dt} \Rightarrow \frac{dv}{dt} = \frac{d}{dt}(x_2) = \dot{x}_2 \quad \begin{array}{l} i_C = x_1 \\ V_C = x_2 \end{array}$$

$$x_1 = 0.5 \dot{x}_2 \Rightarrow \dot{x}_2 = 2 x_1$$

$$-u + x_1 + 0.5 \dot{x}_1 + x_2 = 0 \Rightarrow \dot{x}_1 = -2x_2 - 2x_1 + 2u \quad y = x_2$$

$$\left. \begin{array}{l} \dot{x}_1 = -2x_1 - 2x_2 + 2u \\ \dot{x}_2 = 2x_1 \end{array} \right\} \text{State equations}$$
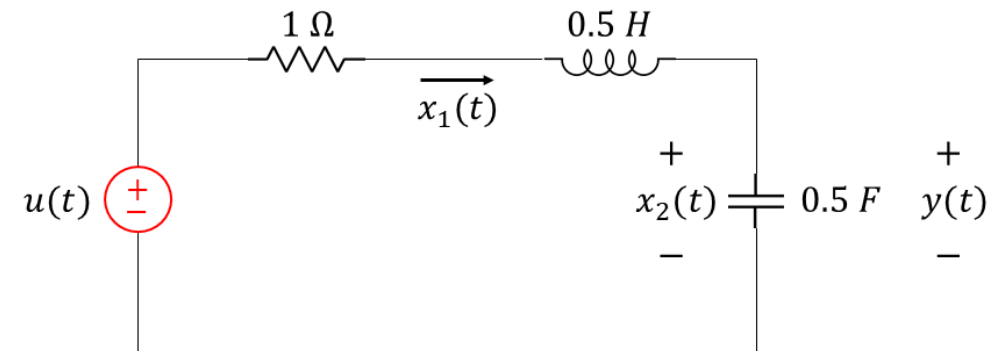
$$y = x_2 \quad \left. \right\} \text{Output equations}$$



Solution

$$\left. \begin{aligned} \dot{x}_1 &= -2x_1 - 2x_2 + 2u \\ \dot{x}_2 &= 2x_1 \end{aligned} \right\} \text{State equations}$$

$$y = x_2 \} \text{Output equations}$$

Equations can be written as:

$$\underbrace{\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix}}_{\dot{x}} = \underbrace{\begin{bmatrix} -2 & -2 \\ 2 & 0 \end{bmatrix}}_A \underbrace{\begin{bmatrix} x_1 \\ x_2 \end{bmatrix}}_x + \underbrace{\begin{bmatrix} 2 \\ 0 \end{bmatrix}}_B \underbrace{u(t)}_u \leftarrow \text{Single output}$$

State-space form of the output equation:

$$\underbrace{[y]}_y = \underbrace{[0 \ 1]}_C \underbrace{\begin{bmatrix} x_1 \\ x_2 \end{bmatrix}}_x + \underbrace{[0]}_D \underbrace{u(t)}_u$$


General equations

$$\vec{\dot{x}} = A\vec{x} + B\vec{u}$$

$$\vec{y} = C\vec{x} + D\vec{u}$$

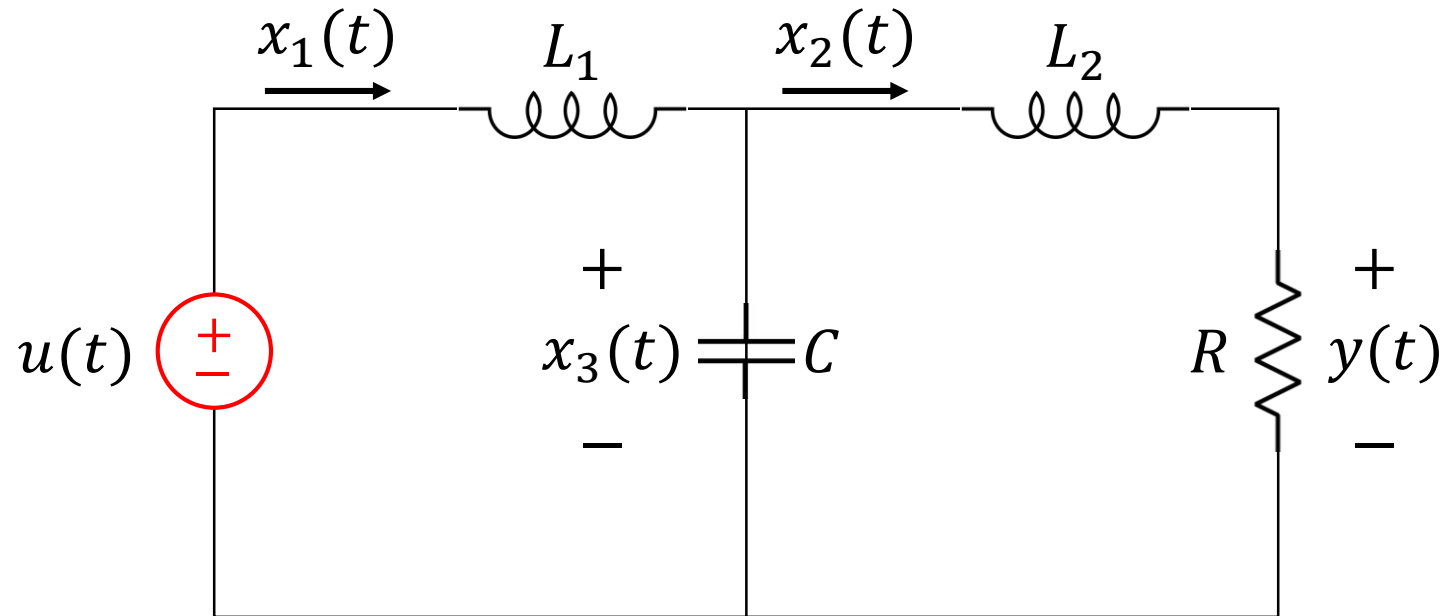Example 2

Determine the state-space equations for the circuit shown below (adapted from Assoc. Prof. Onur Ferhanoğlu).



Solution:

Apply KVL to the left loop: $-u(t) + V_{L1} + V_C = 0$

$$V_L = L \frac{di}{dt} \Rightarrow \frac{di}{dt} = \frac{d}{dt}(x_1) \Rightarrow \frac{di}{dt} = \dot{x}_1 \Rightarrow V_{L1} = L_1 \dot{x}_1(t) \quad V_C = x_3(t)$$

$$-u(t) + L_1 \dot{x}_1(t) + x_3(t) = 0 \Rightarrow \dot{x}_1(t) = -\frac{1}{L_1} x_3(t) + \frac{1}{L_1} u(t)$$

Solution

Apply KVL to the right loop: $-V_C + V_{L2} + V_R = 0$

$$V_C = x_3(t)$$

$$V_L = L \frac{di}{dt} \Rightarrow \frac{di}{dt} = \frac{d}{dt}(x_2) \Rightarrow \frac{di}{dt} = \dot{x}_2 \Rightarrow V_{L2} = L_2 \dot{x}_2(t) \quad V_R = x_2(t)R$$


$$-x_3(t) + L_2 \dot{x}_2(t) + x_2(t)R = 0 \Rightarrow \dot{x}_2(t) = -\frac{R}{L_2}x_2(t) + \frac{1}{L_2}x_3(t)$$

$$\text{KCL: } x_1(t) = x_2(t) + i_C$$

$$i_C = C \frac{dv}{dt} \Rightarrow \frac{dv}{dt} = \frac{d}{dt}(x_3) = \dot{x}_3 \Rightarrow i_C = C \dot{x}_3(t)$$

$$x_1(t) = x_2(t) + C \dot{x}_3(t) \Rightarrow \dot{x}_3(t) = \frac{1}{C}x_1(t) - \frac{1}{C}x_2(t)$$

Equation for output: $y(t) = x_2(t)R$

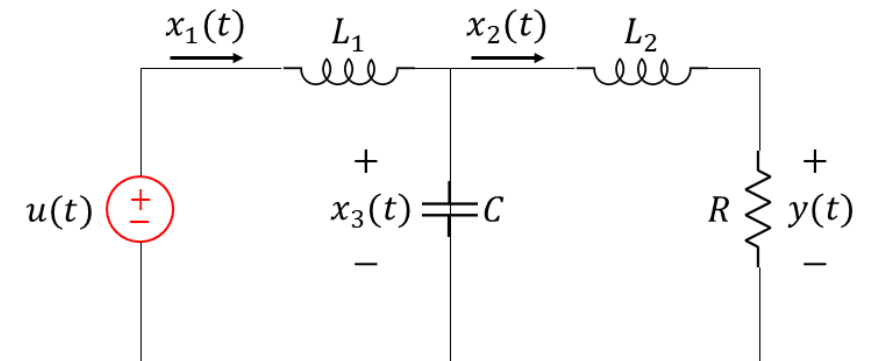

Solution

All equations:

$$\left. \begin{aligned} \dot{x}_1(t) &= -\frac{1}{L_1}x_3(t) + \frac{1}{L_1}u(t) \\ \dot{x}_2(t) &= -\frac{R}{L_2}x_2(t) + \frac{1}{L_2}x_3(t) \\ \dot{x}_3(t) &= \frac{1}{C}x_1(t) - \frac{1}{C}x_2(t) \end{aligned} \right\} \text{State equations}$$

$$y(t) = x_2(t)R \quad \} \text{Output equations}$$


Matrix form:

$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \\ \dot{x}_3(t) \end{bmatrix} = \begin{bmatrix} 0 & 0 & -\frac{1}{L_1} \\ 0 & -\frac{R}{L_2} & \frac{1}{L_2} \\ \frac{1}{C} & -\frac{1}{C} & 0 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \\ x_3(t) \end{bmatrix} + \begin{bmatrix} \frac{1}{L_1} \\ 0 \\ 0 \end{bmatrix} u(t)$$

$$y(t) = [0 \quad R \quad 0] \begin{bmatrix} x_1(t) \\ x_2(t) \\ x_3(t) \end{bmatrix} + [0]u(t)$$

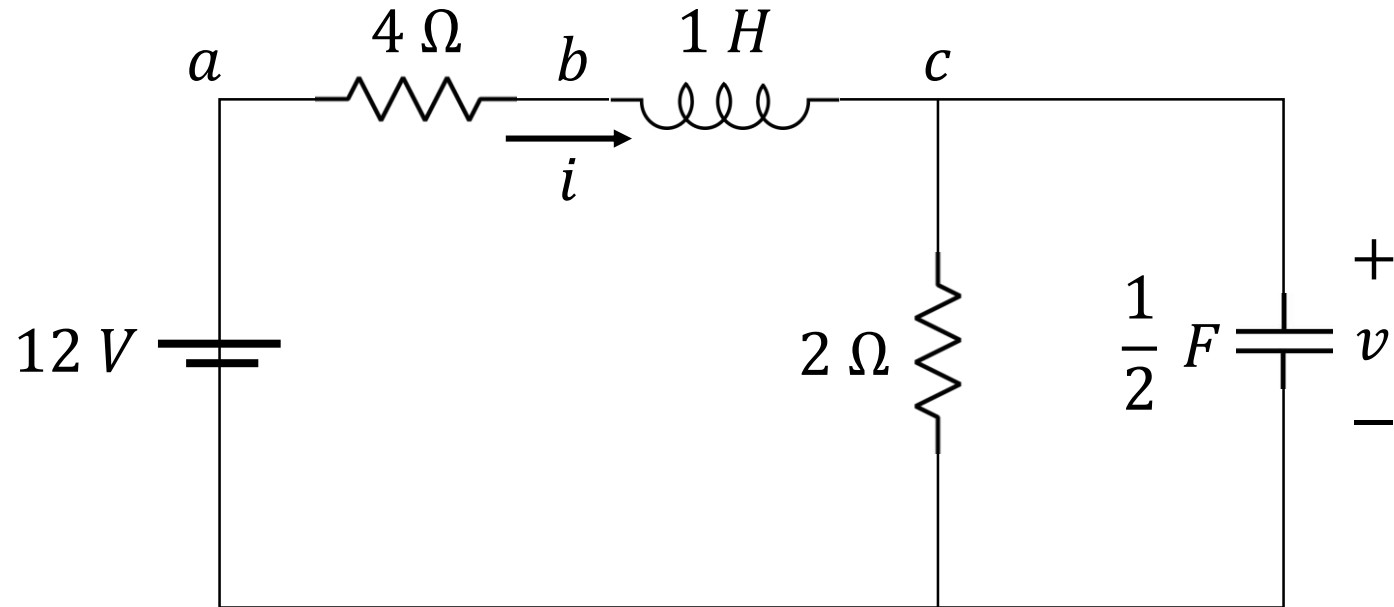Example 3

Determine the state equations of the system shown below (adapted from C.T. Pan's note).



Solution:

Represent the system in terms of voltage v and current i since these are the state variables.

Apply KCL at node c: $i = \frac{v}{2} + C \frac{dv}{dt} \Rightarrow C \frac{dv}{dt} = i - \frac{v}{2} \Rightarrow \underbrace{\frac{dv}{dt} = -\frac{1}{2C}v + \frac{1}{C}i}_{\text{State equation}}$

Solution

Apply KVL to the left loop: $-12 + 4i + V_L + v = 0$

$$V_L = L \frac{di}{dt} \Rightarrow \frac{di}{dt} = \frac{d}{dt}(i) \Rightarrow \frac{di}{dt} = \dot{i}$$

$$-12 + 4i + L\dot{i} + v = 0 \quad \text{Represent current as } \frac{d}{dt}$$

$$-12 + 4i + L \frac{di}{dt} + v = 0 \Rightarrow \frac{di}{dt} = -\frac{1}{L}v - \frac{4}{L}i + \frac{1}{L}12$$


State equation

Note that no output equation since it is not stated in the circuit

$$\frac{d}{dt} \begin{bmatrix} v \\ i \end{bmatrix} = \begin{bmatrix} -1/2C & 1/C \\ -1/L & -4/L \end{bmatrix} \begin{bmatrix} v \\ i \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \end{bmatrix} 12$$


or

$$\begin{bmatrix} \frac{dv}{dt} \\ \frac{di}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{1}{2C} & \frac{1}{C} \\ -\frac{1}{L} & -\frac{4}{L} \end{bmatrix} \begin{bmatrix} v \\ i \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{L} \end{bmatrix} 12$$

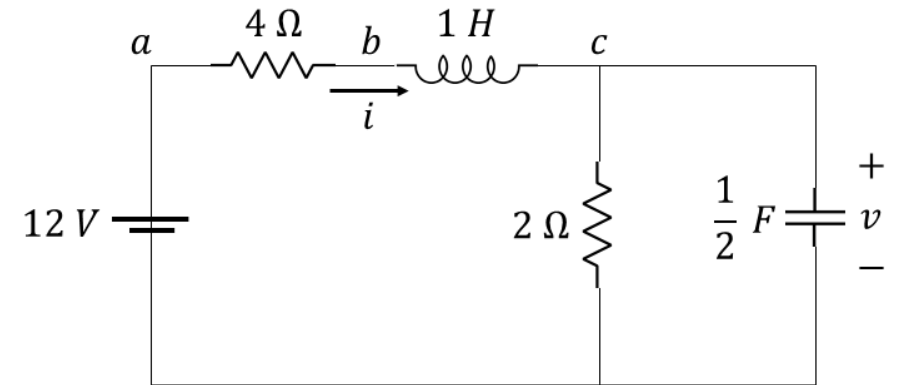

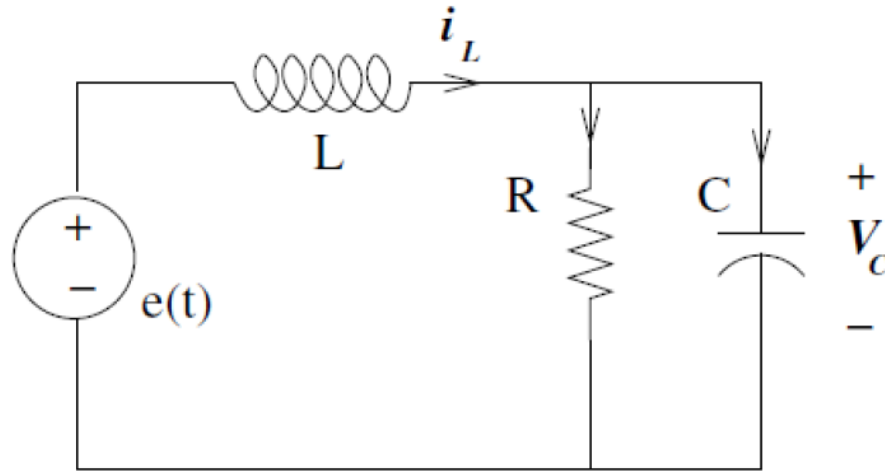Example 4

Write the state variable equations in the circuit shown below (adapted from Müştak E. Yalçın's note).



Solution:

Apply KCL: $i_L = i_R + i_C$ $i_R = V_C/R$ $G = \frac{1}{R}$ $i_R = GV_C$


$$i_L = GV_C + C \frac{dV_C}{dt} \quad \Rightarrow \quad C \frac{dV_C}{dt} = -GV_C + i_L \quad \Rightarrow \quad \underbrace{\frac{dV_C}{dt} = -\frac{G}{C} V_C + \frac{1}{C} i_L}_{\text{State equation}}$$

Solution

Apply KVL to the left loop: $-e + V_L + V_R = 0$

$$V_R = V_C \text{ (since } R||C) \quad V_L = L \frac{di_L}{dt}$$
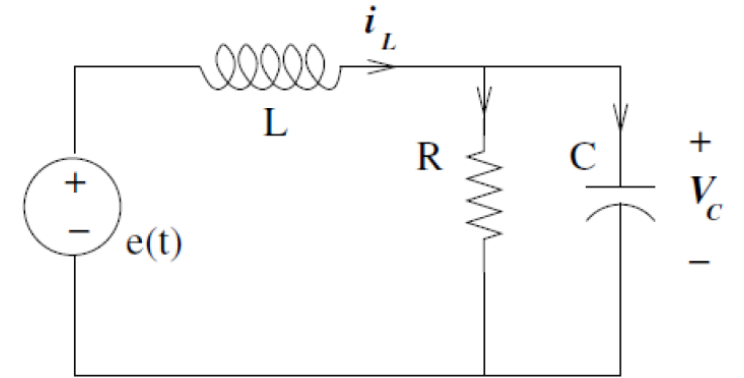
$$-e + L \frac{di_L}{dt} + V_C = 0 \Rightarrow \underbrace{\frac{di_L}{dt} = -\frac{1}{L}V_C + \frac{1}{L}e}_{\text{State equation}}$$



Output is not specified in the circuit

$$\begin{bmatrix} \frac{dV_C}{dt} \\ \frac{di_L}{dt} \end{bmatrix} = \begin{bmatrix} -G/C & 1/C \\ -1/L & 0 \end{bmatrix} \begin{bmatrix} V_C \\ i_L \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \end{bmatrix} e$$

Example 5

Represent the system shown below using state-space model. $R_1 = R_2 = R_3 = 1 \Omega$ and $C_1 = C_2 = 1 F$ (adapted from Eytan Modiano's note-MIT).

Solution:

Apply KCL (each node):


$$e_1: i_1 = \frac{e_3 - e_1}{R_1} = \frac{e_3 - e_1}{1}$$

$$e_2: i_2 = \frac{e_3 - e_2}{R_2} = \frac{e_3 - e_2}{1}$$

$$e_3: \frac{e_3}{R_3} = \frac{e_3}{1} \quad i_1 + i_2 + i_3 = 0$$

$$\frac{e_3 - e_1}{1} + \frac{e_3 - e_2}{1} + \frac{e_3}{1} = 0 \Rightarrow 3e_3 - e_1 - e_2 = 0 \Rightarrow e_3 = \frac{e_1 + e_2}{3}$$

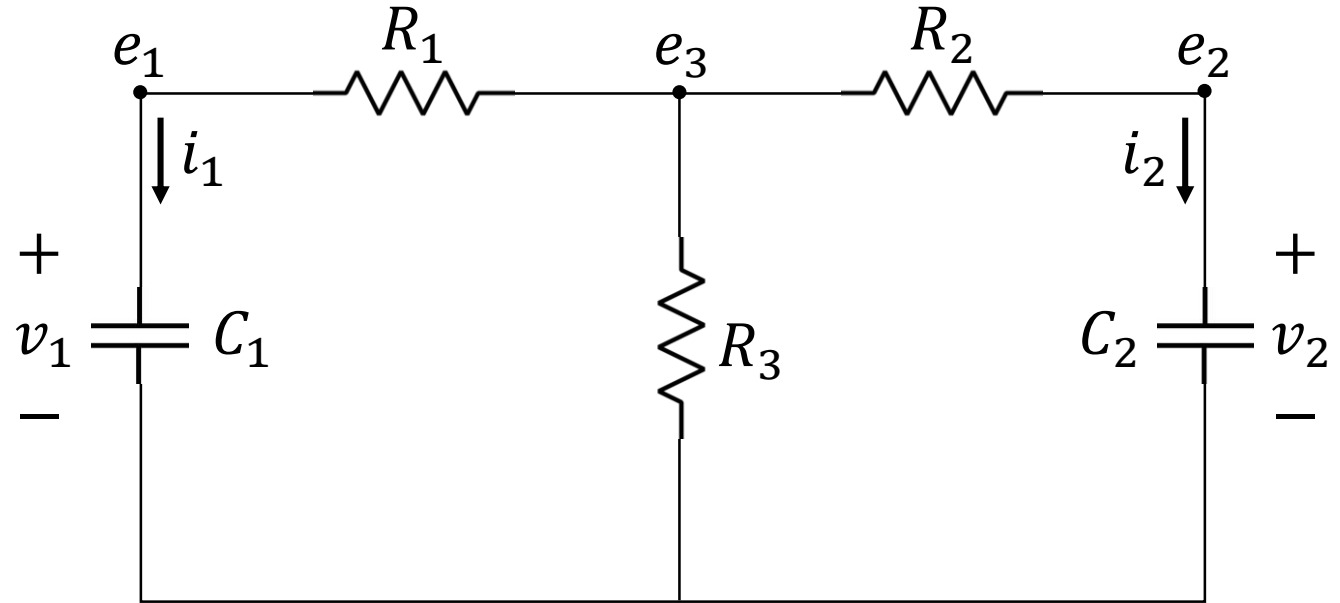e_1 , e_2 , and e_3 are node voltages and can be replaced by V_1 , V_2 , and V_3 , respectively.



Solution

Substitute e_3 into i_1 and i_2 equations

$$i_1 = \frac{e_3 - e_1}{1} = \frac{\frac{e_1 + e_2}{3} - e_1}{1} \Rightarrow i_1 = \frac{-2V_1 + V_2}{3}$$

$$i_2 = \frac{e_3 - e_2}{1} = \frac{\frac{e_1 + e_2}{3} - e_2}{1} \Rightarrow i_2 = \frac{V_1 - 2V_2}{3}$$

$$i_1 = C \frac{dV_1}{dt} = 1 \frac{dV_1}{dt} = \frac{dV_1}{dt}$$

$$i_2 = C \frac{dV_2}{dt} = 1 \frac{dV_2}{dt} = \frac{dV_2}{dt}$$

Solution


$$\left. \begin{aligned} \frac{dV_1}{dt} &= -\frac{2}{3}V_1 + \frac{1}{3}V_2 \\ \frac{dV_2}{dt} &= \frac{1}{3}V_1 - \frac{2}{3}V_2 \end{aligned} \right\} \text{State equations}$$

$$\begin{bmatrix} \frac{dV_1}{dt} \\ \frac{dV_2}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{2}{3} & \frac{1}{3} \\ \frac{1}{3} & -\frac{2}{3} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} u(t) \quad \text{or} \quad \begin{bmatrix} \dot{V}_1 \\ \dot{V}_2 \end{bmatrix} = \begin{bmatrix} -\frac{2}{3} & \frac{1}{3} \\ \frac{1}{3} & -\frac{2}{3} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \text{or}$$

$$\frac{d}{dt} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -\frac{2}{3} & \frac{1}{3} \\ \frac{1}{3} & -\frac{2}{3} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

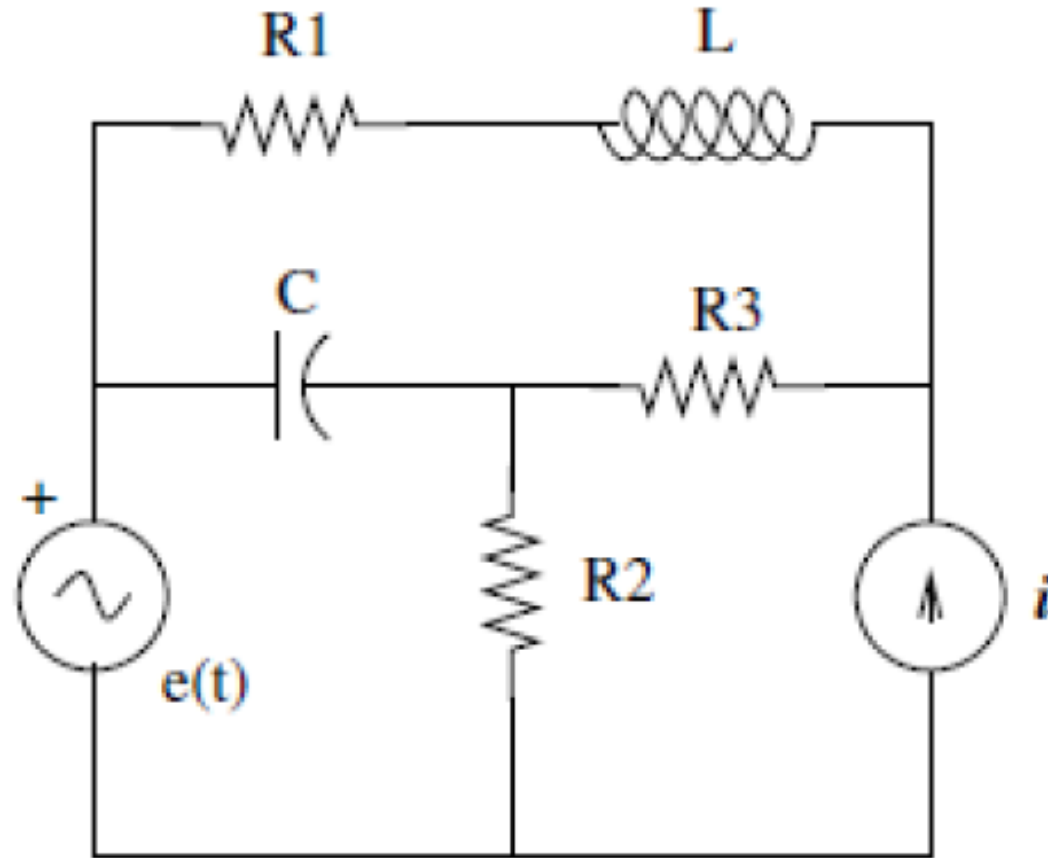Example 6

Write the state equations for the circuit given below (adapted from Müştak E. Yalçın's note).



Solution

Apply KCL

$$\text{at node a: } i + i_L + i_3 = 0$$

$$i_c = i_3 + i_2 \Rightarrow i_3 = i_c - i_2$$

$$i + i_L + i_c - i_2 = 0$$


Apply KVL to the upper loop:

$$-V_C + V_1 + V_L - V_3 = 0$$

$$i_c = C \frac{dV_C}{dt} \quad V_L = L \frac{di_L}{dt}$$

$$i + i_L + C \frac{dV_C}{dt} - i_2 = 0 \Rightarrow C \frac{dV_C}{dt} = -i_L + i_2 - i$$
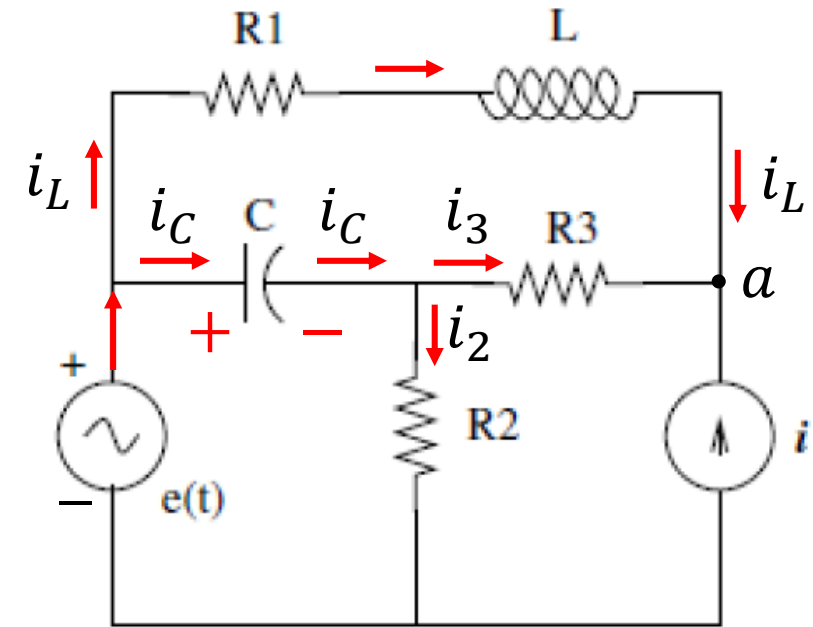
$$-V_C + V_1 + L \frac{di_L}{dt} - V_3 = 0 \Rightarrow L \frac{di_L}{dt} = V_3 + V_C - V_1$$



Circuit has two inputs, voltage and current source.

Since variable are V_C and i_L , write equations in terms of V_C and i_L .

Solution

$$i_2 = \frac{-V_C - (-e)}{R_2} = \frac{e - V_C}{R_2}$$

$$V_1 = i_L R_1$$


$$V_3 = R_3 i_3 \text{ where } i_3 = i_c - i_2$$

$$V_3 = R_3(i_c - i_2) \quad \text{where } i_c = -i_L + i_2 - i$$

$$V_3 = R_3(-i_L + i_2 - i - i_2) \Rightarrow V_3 = R_3(-i_L - i)$$

$$C \frac{dV_C}{dt} = -i_L + i_2 - i \Rightarrow \frac{dV_C}{dt} = -\frac{1}{C} i_L + \frac{e - V_C}{R_2 C} - \frac{1}{C} i \quad \text{or}$$
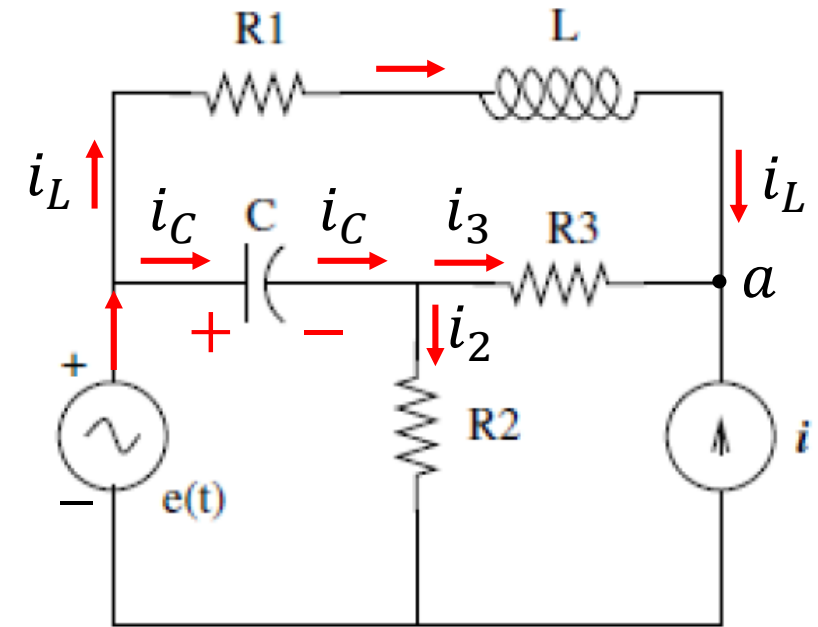
$$\left. \frac{dV_C}{dt} = -\frac{1}{R_2 C} V_C - \frac{1}{C} i_L + \frac{1}{R_2 C} e - \frac{1}{C} i \right\} \text{ State equations}$$



Solution

$$L \frac{di_L}{dt} = V_3 + V_C - V_1 \Rightarrow L \frac{di_L}{dt} = R_3(-i_L - i) + V_C - i_L R_1$$


$$\frac{di_L}{dt} = -\frac{R_3}{L} i_L - \frac{R_3}{L} i + \frac{1}{L} V_C - \frac{R_1}{L} i_L \quad \text{or}$$

$$\frac{di_L}{dt} = \frac{1}{L} V_C + \left(-\left(\frac{R_1 + R_3}{L} \right) \right) i_L - \frac{R_3}{L} i \quad \left. \vphantom{\frac{di_L}{dt}} \right\} \text{State equations}$$

$$\frac{d}{dt} \begin{bmatrix} V_C \\ i_L \end{bmatrix} = \begin{bmatrix} \frac{-1}{R_2 C} & \frac{-1}{C} \\ \frac{1}{L} & \frac{-(R_3 + R_1)}{L} \end{bmatrix} \begin{bmatrix} V_C \\ i_L \end{bmatrix} + \begin{bmatrix} \frac{1}{R_2 C} \\ 0 \end{bmatrix} e(t) + \begin{bmatrix} \frac{-1}{C} \\ -\frac{R_3}{L} \end{bmatrix} i$$

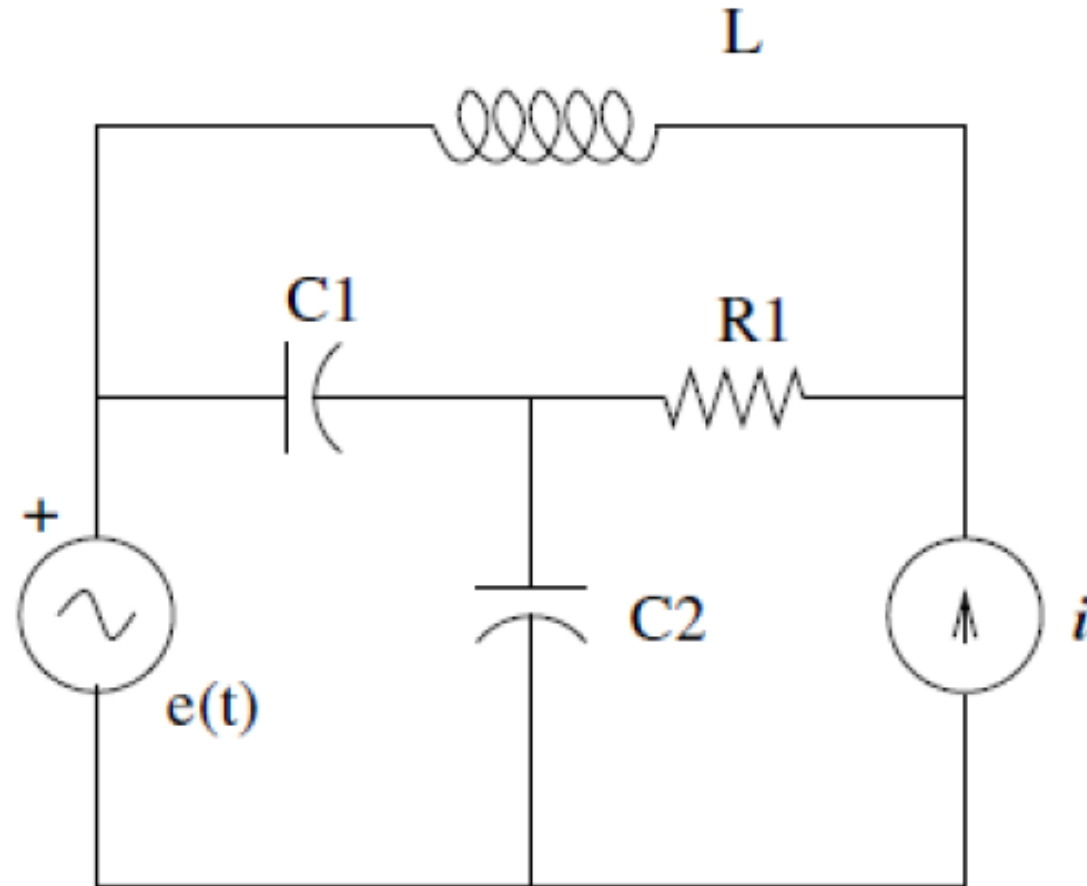Example 7

Write the state equations for the circuit shown below (adapted from Müştak E. Yalçın's note).



Solution

Apply KCL at node a: $i_1 + i_L + i = 0$

$$i_{C1} = i_1 + i_{C2} \Rightarrow i_1 = i_{C1} - i_{C2}$$

$$i_{C1} - i_{C2} + i_L + i = 0$$


Apply KVL to the upper loop:

$$-V_{C1} + V_L - V_1 = 0$$

$$i_{C1} = C_1 \frac{dV_{C1}}{dt} \quad V_L = L \frac{di_L}{dt}$$

$$C_1 \frac{dV_{C1}}{dt} - i_{C2} + i_L + i = 0 \quad \Rightarrow \quad C_1 \frac{dV_{C1}}{dt} = -i_L - i + i_{C2} \quad \rightarrow \text{1st equation}$$
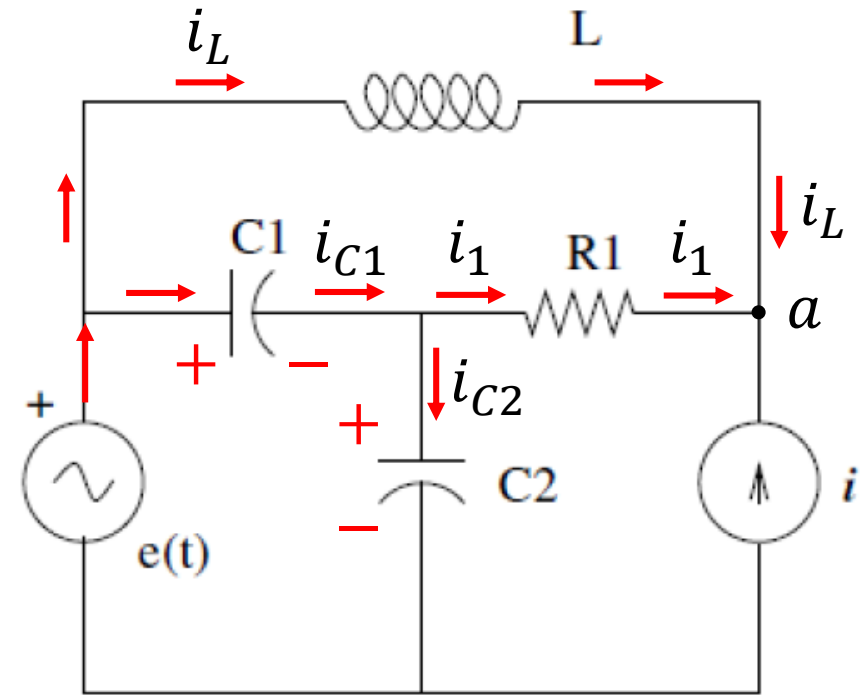
$$-V_{C1} + L \frac{di_L}{dt} - V_1 = 0 \quad \Rightarrow \quad L \frac{di_L}{dt} = V_1 + V_{C1} \quad \rightarrow \text{2nd equation}$$



Solution

$$i_{C2} = C_2 \frac{dV_{C2}}{dt}$$


Apply KVL to the lower left loop:

$$V_{C2} = e - V_{C1} \quad \Rightarrow \quad \text{Take the derivative of both sides}$$

$$\frac{dV_{C2}}{dt} = \frac{de}{dt} - \frac{dV_{C1}}{dt} \quad \Rightarrow \quad \text{Multiply both sides with } C_2$$

$$\underbrace{C_2 \frac{dV_{C2}}{dt}}_{i_{C2}} = C_2 \frac{de}{dt} - C_2 \frac{dV_{C1}}{dt} \quad \Rightarrow \quad \text{Substitute into equation 1}$$
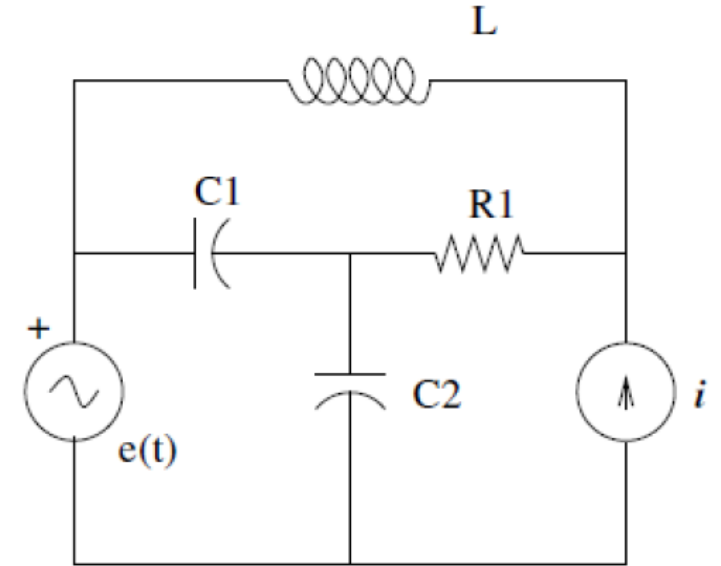
$$C_1 \frac{dV_{C1}}{dt} = -i_L - i + C_2 \frac{de}{dt} - C_2 \frac{dV_{C1}}{dt} \quad \Rightarrow \quad C_1 \frac{dV_{C1}}{dt} + C_2 \frac{dV_{C1}}{dt} = -i_L - i + C_2 \frac{de}{dt}$$



Solution

$$C_1 \frac{dV_{C1}}{dt} + C_2 \frac{dV_{C1}}{dt} = -i_L - i + C_2 \frac{de}{dt} \rightarrow \frac{dV_{C1}}{dt} (C_1 + C_2) = -i_L - i + C_2 \frac{de}{dt}$$

$$\frac{dV_{C1}}{dt} = -\frac{1}{C_1 + C_2} i_L - \frac{1}{C_1 + C_2} i + \frac{C_2}{C_1 + C_2} \frac{de}{dt} \rightarrow \text{1st state equ.}$$

$$L \frac{di_L}{dt} = V_1 + V_{C1} \quad V_1 = i_1 R_1 \quad i_1 + i_L + i = 0 \Rightarrow i_1 = -(i_L + i)$$

$$V_1 = -R_1(i_L + i)$$

$$L \frac{di_L}{dt} = -R_1(i_L + i) + V_{C1} \rightarrow \frac{di_L}{dt} = -\frac{R_1}{L} i_L - \frac{R_1}{L} i + \frac{1}{L} V_{C1} \rightarrow \text{2nd state equ.}$$

Solution

$$\left. \begin{aligned} \frac{dV_{C1}}{dt} &= -\frac{1}{C_1 + C_2} i_L + \frac{C_2}{C_1 + C_2} \frac{de}{dt} - \frac{1}{C_1 + C_2} i \\ \frac{di_L}{dt} &= \frac{1}{L} V_{C1} - \frac{R_1}{L} i_L - \frac{R_1}{L} i \end{aligned} \right\} \text{State equations}$$

- In matrix form:

$$\frac{d}{dt} \begin{bmatrix} V_{C1} \\ i_L \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{C_1 + C_2} \\ \frac{1}{L} & -\frac{R_1}{L} \end{bmatrix} \begin{bmatrix} V_{C1} \\ i_L \end{bmatrix} + \begin{bmatrix} \frac{C_2}{C_1 + C_2} \\ 0 \end{bmatrix} \frac{de}{dt} + \begin{bmatrix} -\frac{1}{C_1 + C_2} \\ -\frac{R_1}{L} \end{bmatrix} i$$

Example 8

For the circuit given below, write state equations (adapted from Müştak E. Yalçın's note).

Solution:

Apply KCL at node 2: $i_1 = i_2 + i_3 + i_{C1}$

Let voltages at each node as follows:

Node 1: V_{d1}
 Node 2: V_{d2}


$$i_1 = \frac{V_{d1} - V_{d2}}{R_1} \quad i_2 = \frac{V_{d2} - V_{d4}}{R_2}$$

Node 3: V_{d3}
 Node 4: V_{d4}

$$i_3 = \frac{V_{d2} - V_{d3}}{R_3} \quad i_{C1} = C1 \frac{dV_{C1}}{dt}$$

$$\frac{V_{d1} - V_{d2}}{R_1} = \frac{V_{d2} - V_{d4}}{R_2} + \frac{V_{d2} - V_{d3}}{R_3} + C1 \frac{dV_{C1}}{dt}$$
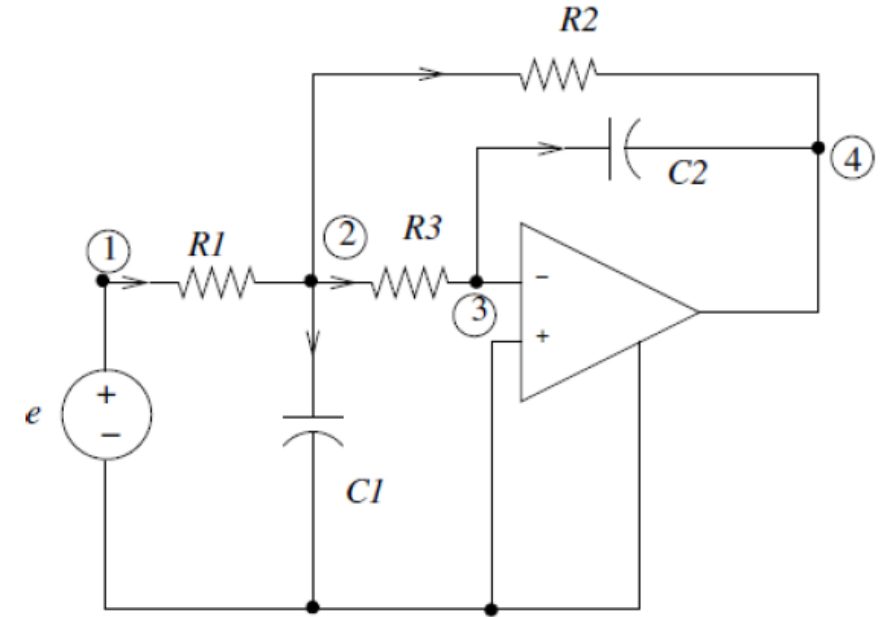
$$C1 \frac{dV_{C1}}{dt} = \frac{V_{d1} - V_{d2}}{R_1} - \frac{V_{d2} - V_{d4}}{R_2} - \frac{V_{d2} - V_{d3}}{R_3}$$



Solution

Apply KCL at node 3: $i_3 = i_{C2}$ $i_3 = \frac{V_{d2} - V_{d3}}{R_3}$ $i_{C2} = C2 \frac{dV_{C2}}{dt}$

$$C2 \frac{dV_{C2}}{dt} = \frac{V_{d2} - V_{d3}}{R_3}$$


Redefine node voltages as: $V_{d1} = e$, $V_{d2} = V_{C1}$, $V_{d3} = 0$, and $V_{d4} = -V_{C2}$

Recall: $G = \frac{1}{R}$

$$C1 \frac{dV_{C1}}{dt} = G_1(e - V_{C1}) - G_2(V_{C1} - V_{C2}) - G_3(V_{C1} - 0)$$

$$\frac{dV_{C1}}{dt} = \frac{G_1}{C1} (e - V_{C1}) - \frac{G_2}{C1} (V_{C1} - V_{C2}) - \frac{G_3}{C1} V_{C1}$$
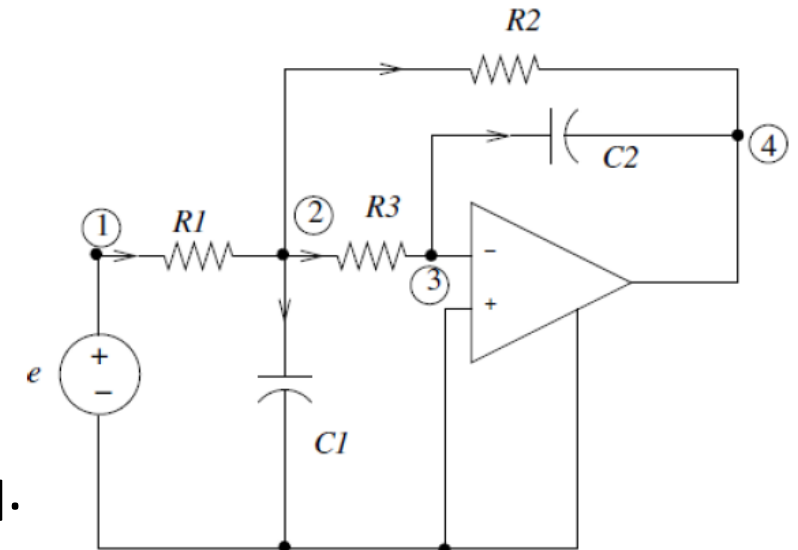
$$\frac{dV_{C1}}{dt} = - \left(\frac{G_1 + G_2 + G_3}{C1} \right) V_{C1} - \frac{G_2}{C1} V_{C2} - \frac{G_1}{C1} e \rightarrow 1^{\text{st}} \text{ eq.}$$



Solution


$$C_2 \frac{dV_{C2}}{dt} = G_3 (V_{C1} - 0) \rightarrow \frac{dV_{C2}}{dt} = \frac{G_3}{C_2} V_{C1} \rightarrow 2^{\text{nd}} \text{ eq.}$$

$$\left. \begin{aligned} \frac{dV_{C1}}{dt} &= - \left(\frac{G_1 + G_2 + G_3}{C_1} \right) V_{C1} - \frac{G_2}{C_1} V_{C2} - \frac{G_1}{C_1} e \\ \frac{dV_{C2}}{dt} &= \frac{G_3}{C_2} V_{C1} \end{aligned} \right\} \text{State equations}$$

$$\frac{d}{dt} \begin{bmatrix} V_{C1} \\ V_{C2} \end{bmatrix} = \begin{bmatrix} -\frac{G_1 + G_2 + G_3}{C_1} & -\frac{G_2}{C_1} \\ -\frac{G_3}{C_2} & 0 \end{bmatrix} \begin{bmatrix} V_{C1} \\ V_{C2} \end{bmatrix} + \begin{bmatrix} \frac{G_1}{C_1} \\ 0 \end{bmatrix} e$$

Two terminal Linear and Nonlinear Circuit Elements

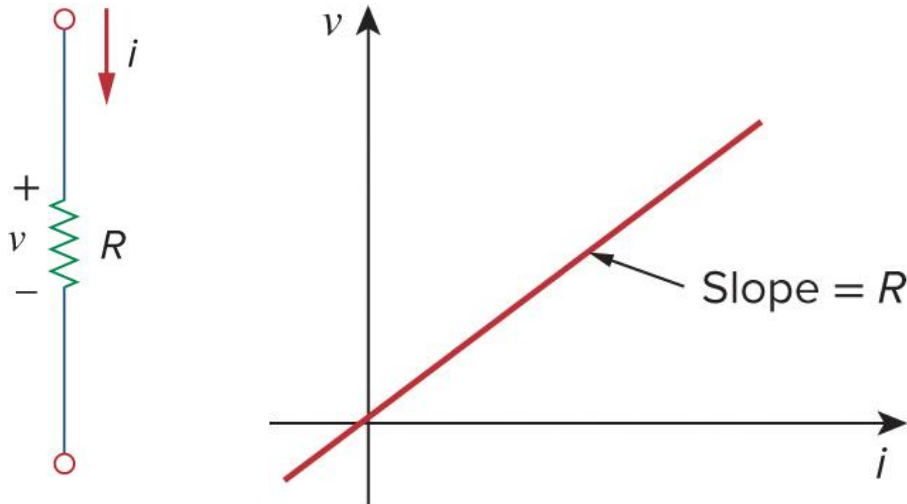- Two types of resistors:
 - Linear resistor
 - Nonlinear resistor
- **Linear resistor:**
 - Two terminal circuit element whose resistance value does not change or vary with the flow of current through it.
 - Current through the resistance is always proportional to the voltage applied across it.



- Linear resistance: Obey Ohm's law

$$v(t) = i(t)R \text{ or } i(t) = Gv(t)$$


- It has a constant resistance (slope)
- Linearity: Its i - v graph is a straight line passing through the origin

Linear Resistor

- Resistance value for open and short circuit:


$$v = iR \text{ or } i = Gv$$

- When $R = \infty$, $i = 0$

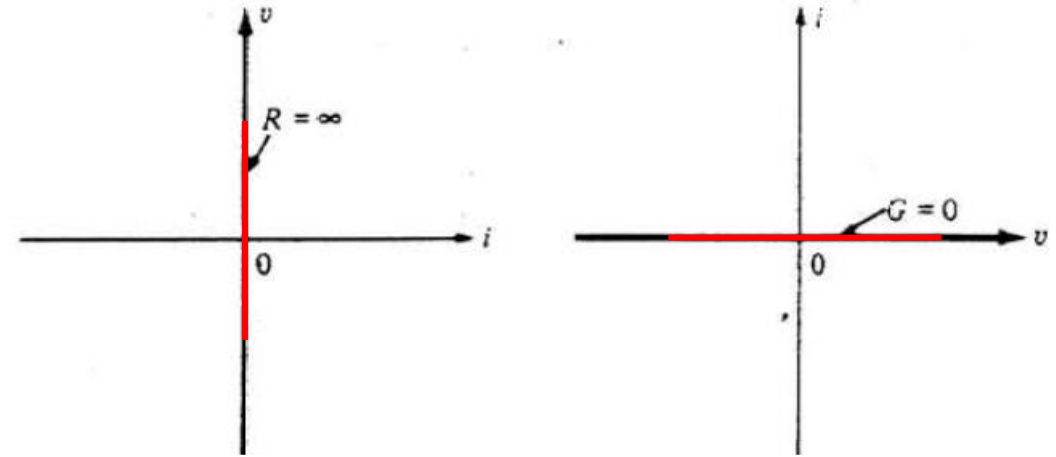

Characteristics of open circuit

- When $R = 0$, $v = 0$

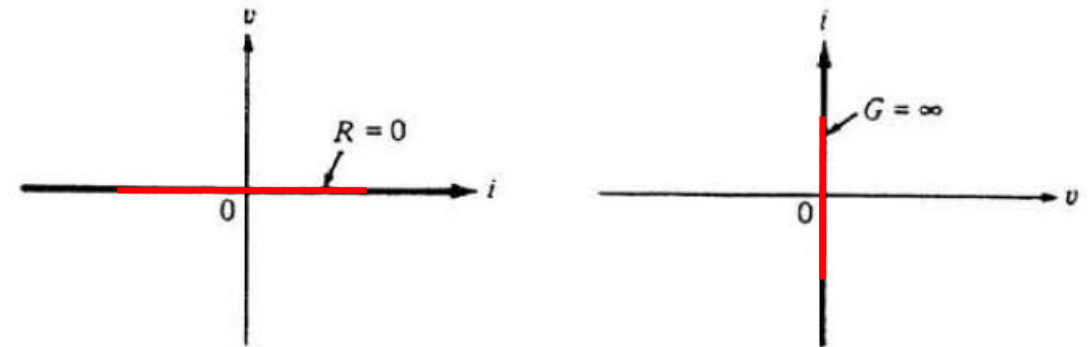


Characteristics of short circuit

Nonlinear Resistor

- What is nonlinear resistor?
 - Circuit element whose voltage and current relation vary nonlinearly as opposed to linear resistor.
 - Current through nonlinear resistor is not proportional to the voltage applied across it.
- Diode: nonlinear resistor.


Circuit symbol of diode

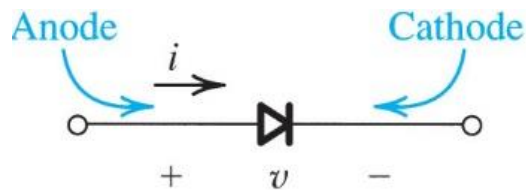

Two terminals:
Anode (+) and Cathode (-)

Current flows in the
direction of arrowhead

$i - v$ characteristics of ideal diode

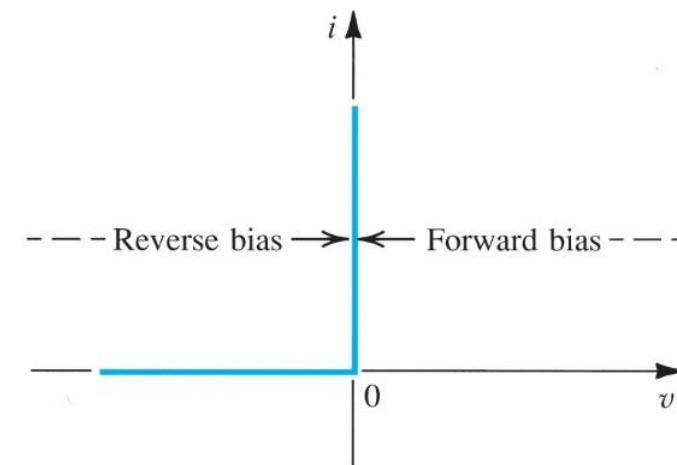


Highly nonlinear

Nonlinear Resistor: pn-Junction Diode

- pn-junction diode is a two terminal semiconductor devices
- Current increases exponentially in the forward bias region.
- pn-Junction diode: nonlinear elements as $i - v$ relationship is not linear.

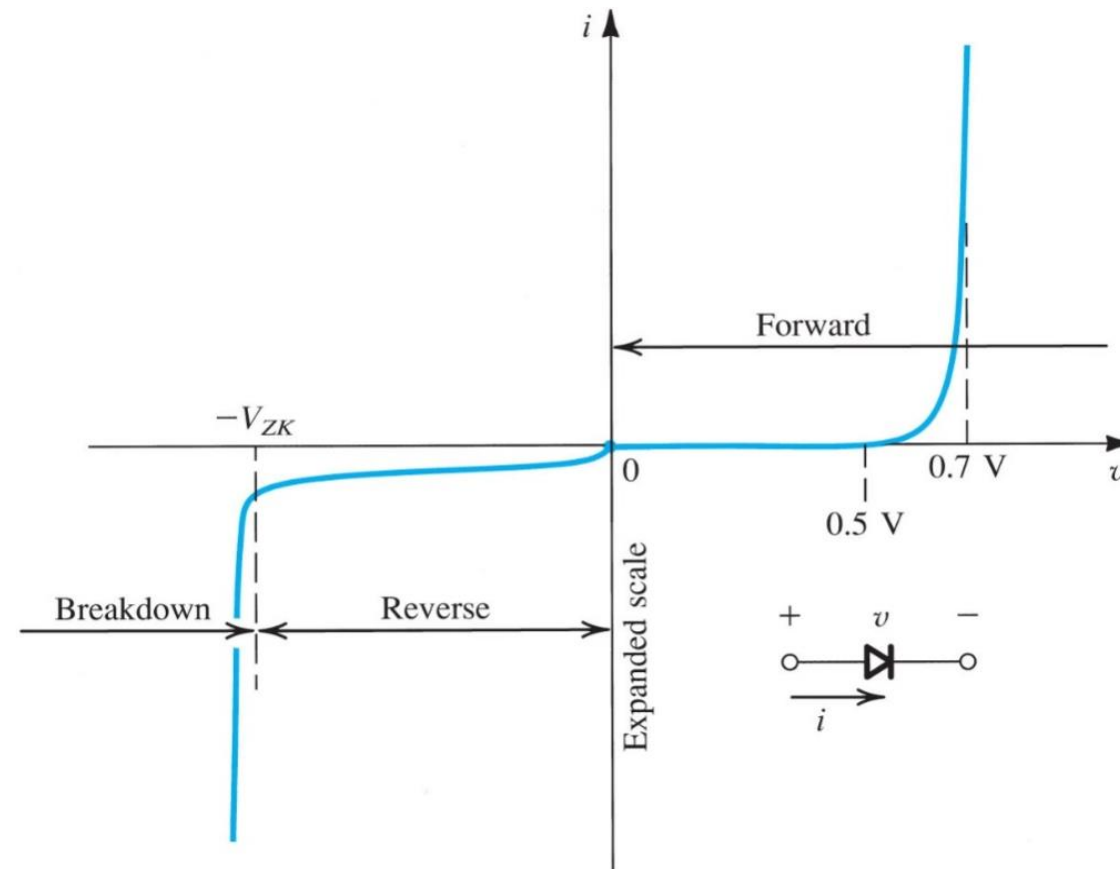
$$i = I_S \left(e^{\frac{v}{V_T}} - 1 \right)$$



Analysis of Nonlinear Resistive Circuit

- Reason to analyze nonlinear circuits:
 - ❑ Electrical devices such as computer or amplifier are constructed based upon mostly nonlinear circuit.
 - ❑ Understanding nonlinear circuit: design superior devices.

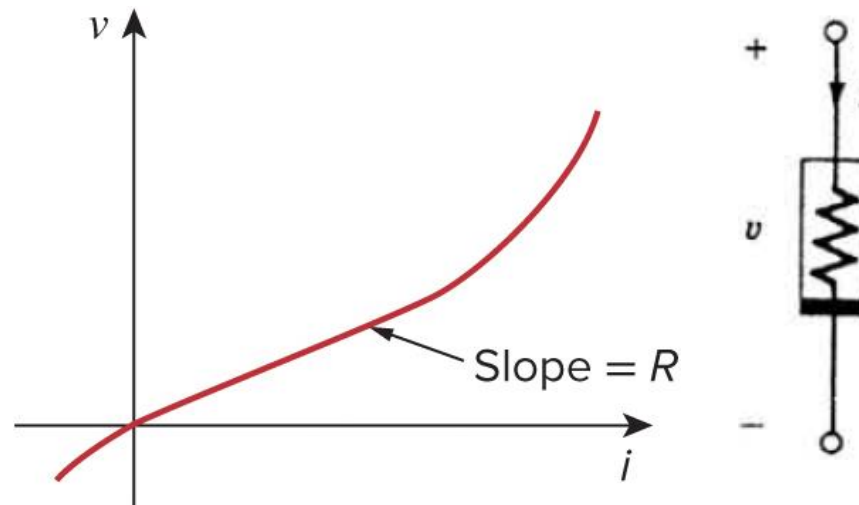Nonlinear resistance: Does not Obey Ohm's law



- Its resistance (slope) varies with current


Analysis of Nonlinear Resistive Circuit

- Nonlinear resistor in a circuit can be analyzed using linear approximation.
- Linear approximation is called linearization.
- Nonlinear graph: i and v are not directly proportional
- Point Q: operation point
- Linearized based on the slope at the operation point Q. Resistance is obtained from slope.

$$R_Q = \left. \frac{dv_Q}{dI_Q} \right|_Q$$

- DC operating point is obtained from the dc component of the input signal when ac components are set to zero.
- For ac analysis, determine the slope (R_Q) at operating point Q when dc components are set to zero.

$$R_Q = \left. \frac{df(i)}{di_N} \right|_Q$$

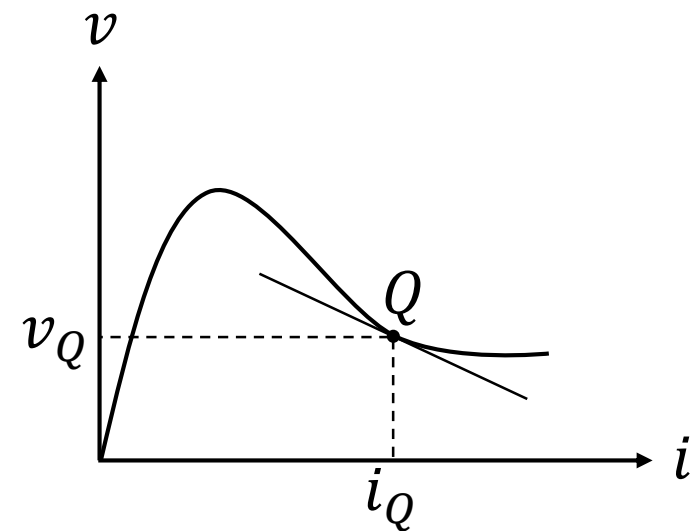

Example 9

For the circuit shown below, $R = 3.5 \Omega$, $e_s = 9 V$, $e_t(t) = 0.1\sin(10t)$. The nonlinear resistance is characterized by

$$v_R = i_R^3 - 6i_R^2 + 9i_R$$

Determine the solution for v_R (adapted from Müştak E. Yalçın's note).


Solution:

Circuit has both ac and dc components:

$$e_s = 9 V \longrightarrow \text{dc}$$

$$e_t(t) = 0.1\sin(10t) \longrightarrow \text{ac}$$

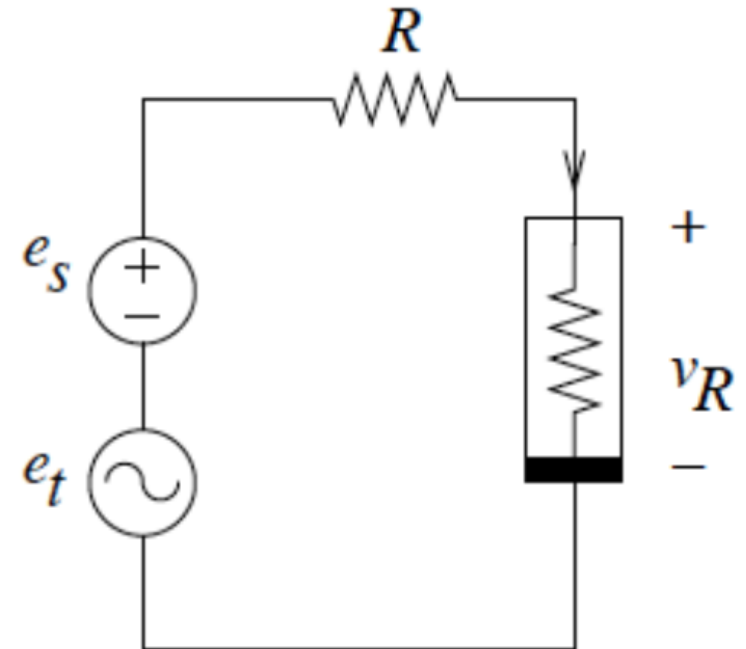In order to find complete solution for v_R , determine both ac & dc components of v_R .



Solution

DC analysis: Ignore ac component and find dc operating point based on dc component of the input signal.

Apply KVL: $-e_S + i_R R + V_R = 0 \Rightarrow e_S = i_R R + V_R$

$$v_R = i_R^3 - 6i_R^2 + 9i_R \quad e_S = 9 \text{ V} \quad R = 3.5 \Omega$$


$$9 = 3.5i_R + i_R^3 - 6i_R^2 + 9i_R$$

$$3.5i_R + i_R^3 - 6i_R^2 + 9i_R - 9 = 0 \Rightarrow i_R^3 - 6i_R^2 + 12.5i_R - 9 = 0$$

Solving the cubic equation: $i_R = 2 \text{ A}$

$$v_R = i_R^3 - 6i_R^2 + 9i_R \Rightarrow v_R = 2^3 - 6(2)^2 + 9(2) \Rightarrow v_R = 2 \text{ V}$$
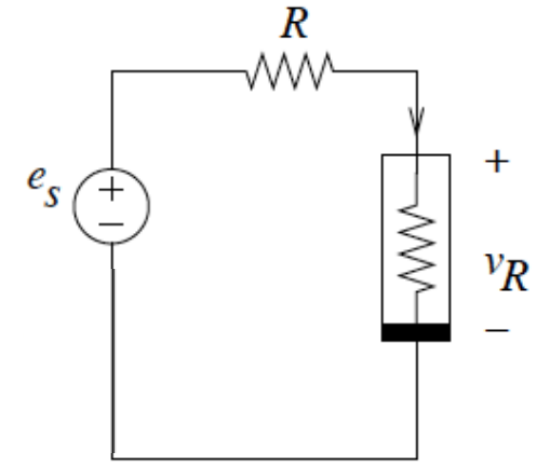
$$\left. \begin{array}{l} I_R = 2 \text{ A} \\ V_R = 2 \text{ V} \end{array} \right\} \text{DC operating point}$$



Solution

AC analysis: Ignore dc component and determine R_Q at operating point Q.

$$R_Q = \left. \frac{dv_Q}{dI_Q} \right|_Q \rightarrow \text{Linearizing the nonlinear resistor around } i_R = 2 \text{ A}$$

$$R_Q = \left. \frac{d}{dI_Q} (i_R^3 - 6i_R^2 + 9i_R) \right|_{i_R = 2 \text{ A}} \rightarrow R_Q = 3i_R^2 - 12i_R + 9 \Big|_{i_R = 2 \text{ A}}$$


$$R_Q = 3(2)^2 - 12(2) + 9 \Rightarrow R_Q = -3 \Omega$$

Find the ac component of v_R

$$\text{Voltage division: } v_R = \frac{R_Q}{R_Q + R} e_t(t)$$


$$v_R = \frac{-3}{-3 + 3.5} 0.1 \sin(10t) \Rightarrow v_R = -0.6 \sin(10t)$$

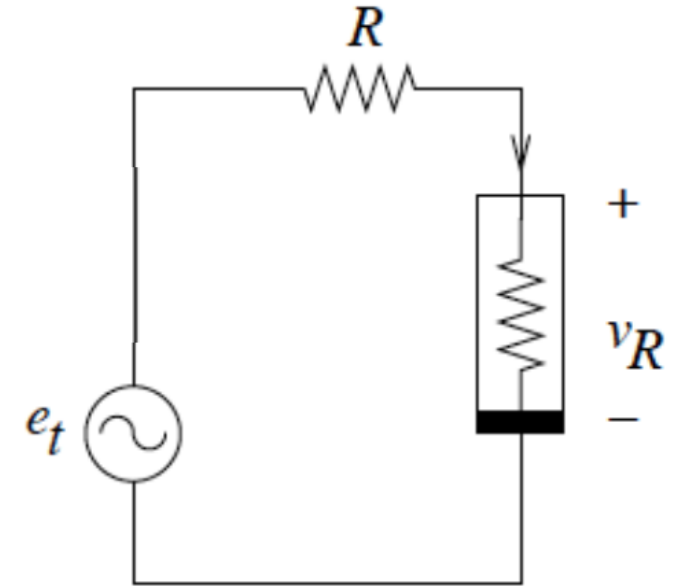Complete solution (superposition): $v_R = 2 - 0.6 \sin(10t)$



Resistive One-Port Network

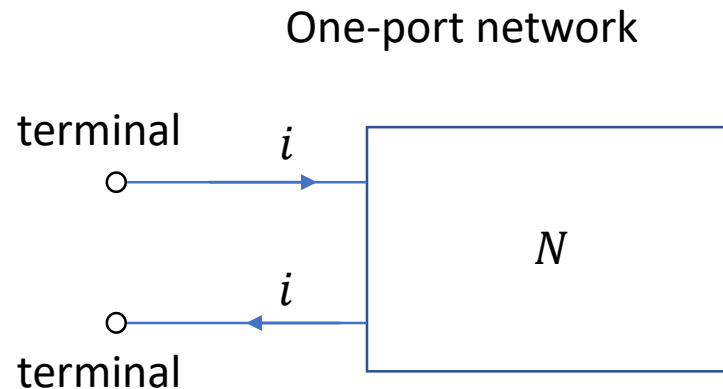- What is port?
 - A pair of terminals connecting an electrical network or circuit to an external circuit.
- Port network: useful to analyze large and complex circuit.
- Port condition:
 - Current enters through one terminal of the port is equal to the current leaving through second terminal of the port
- Example of one-port network: Resistor, capacitor, inductor.




Resistive Two-Port Network

- Electrical circuit or network has two pairs of terminals called two port network.
- Example of two-port network: transformer, filter, transmission line
- Two port network has four variables: V_1, V_2, i_1, i_2
- Port voltages and port currents can be represented as:

$$V = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad i = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

- Note that more than two-port network is called multiport network.

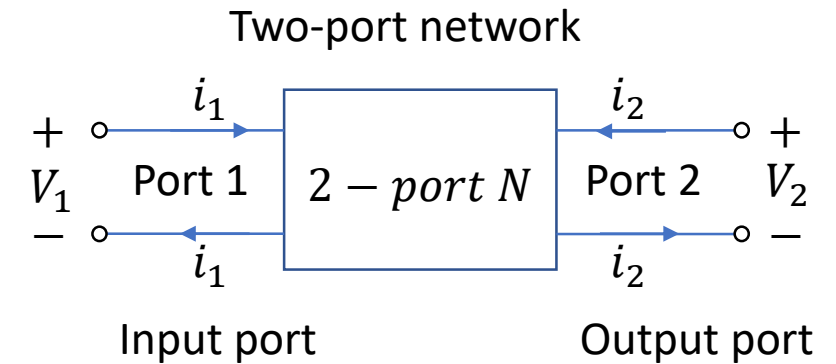

Example 10

Figure below shows a T-circuit which is placed into a black box to create a network. Two independent current sources are connected to the input and output ports. Represent input and output voltages in matrix form. Network variables are V_1, i_1, V_2, i_2

Solution:

Apply KCL:


$$i_{S1} = i_1 \quad i_{S2} = i_2 \quad i_3 = i_1 + i_2$$

Apply KVL: $-V_1 + R_1 i_1 + R_3 i_3 = 0$

Write i_3 in terms of i_1 and i_2 as they are circuit variables.

$$-V_1 + R_1 i_1 + R_3 (i_1 + i_2) = 0 \quad \Rightarrow \quad V_1 = R_1 i_1 + R_3 i_1 + R_3 i_2$$
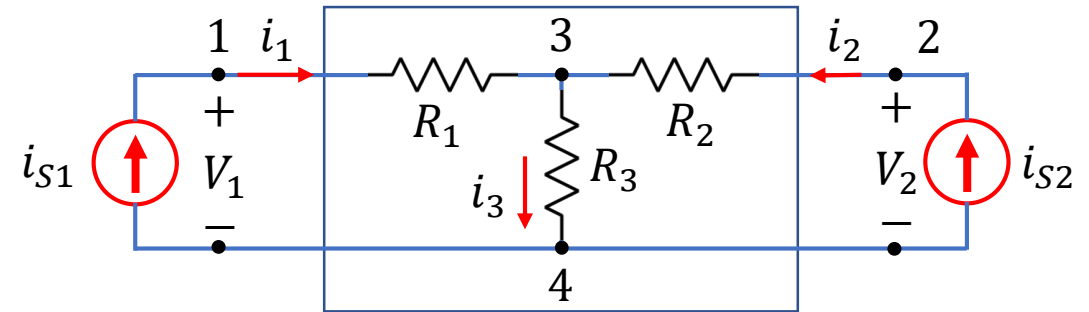
$$V_1 = (R_1 + R_3) i_1 + R_3 i_2 \quad \longrightarrow \quad 1^{\text{st}} \text{ equation}$$



Solution


Apply KVL: $-V_2 + R_2 i_2 + R_3 i_3 = 0$

$$V_2 = R_2 i_2 + R_3 (i_1 + i_2) = 0$$

$$V_2 = R_3 i_1 + (R_2 + R_3) i_2 = 0 \longrightarrow 2^{\text{nd}} \text{ equ.}$$

$$V = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = Ri = \begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \quad \text{Current controlled representation}$$
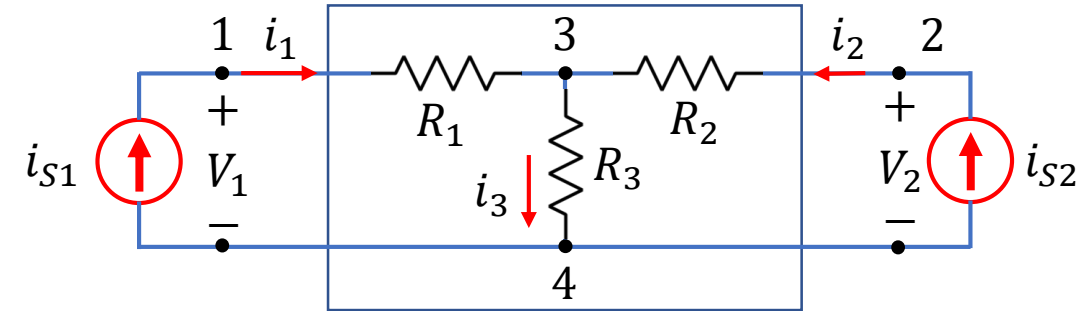
$$R = \begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 & R_2 + R_3 \end{bmatrix} \longrightarrow \text{Resistance matrix of the linear resistive two port}$$



Two currents are sources and two voltages are responses. Thus, i_1 and i_2 are independent variables and V_1 and V_2 are dependent variables (voltages are function of currents).

Solution

- i_1 and i_2 can be solved in terms of V_1 and V_2

$$G = \frac{1}{R} \quad i = GV$$

- G is conductance which is inverse of resistance matrix R

$$G = R^{-1} = \frac{1}{R_1 R_2 + R_1 R_3 + R_2 R_3} \begin{bmatrix} R_2 + R_3 & -R_3 \\ -R_3 & R_1 + R_3 \end{bmatrix} \longrightarrow \text{Conductance matrix of the linear resistive two port}$$

- Current equations:

$$i_1 = \frac{R_2 + R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} V_1 - \frac{R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} V_2$$

$$i_2 = \frac{-R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} V_1 + \frac{R_1 + R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3} V_2$$

$$i = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = GV = [G] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Voltage controlled
representation

Six Representations

- For a resistive two-port network, there exists six different representations
- All possible representations are shown in the table below:

Representations	Independent variables	Dependent variables
Current-controlled	i_1, i_2	v_1, v_2
Voltage-controlled	v_1, v_2	i_1, i_2
Hybrid 1	i_1, v_2	v_1, i_2
Hybrid 2	v_1, i_2	i_1, v_2
Transmission 1	v_2, i_2	v_1, i_1
Transmission 2	v_1, i_1	v_2, i_2

Six Representations

- Equations for six different representations of a resistive two-port:


Representations	Scalar equations	Vector equations
Current-controlled	$v_1 = r_{11}i_1 + r_{12}i_2$ $v_2 = r_{21}i_1 + r_{22}i_2$	$\mathbf{v} = \mathbf{R}\mathbf{i}$
Voltage-controlled	$i_1 = g_{11}v_1 + g_{12}v_2$ $i_2 = g_{21}v_1 + g_{22}v_2$	$\mathbf{i} = \mathbf{G}\mathbf{v}$
Hybrid 1	$v_1 = h_{11}i_1 + h_{12}v_2$ $i_2 = h_{21}i_1 + h_{22}v_2$	$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \mathbf{H} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$
Hybrid 2	$i_1 = h'_{11}v_1 + h'_{12}i_2$ $v_2 = h'_{21}v_1 + h'_{22}i_2$	$\begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = \mathbf{H}' \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$
Transmission 1†	$v_1 = t_{11}v_2 - t_{12}i_2$ $i_1 = t_{21}v_2 - t_{22}i_2$	$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \mathbf{T} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$
Transmission 2†	$v_2 = t'_{11}v_1 + t'_{12}i_1$ $-i_2 = t'_{21}v_1 + t'_{22}i_1$	$\begin{bmatrix} v_2 \\ -i_2 \end{bmatrix} = \mathbf{T}' \begin{bmatrix} v_1 \\ i_1 \end{bmatrix}$

Linear Controlled Sources

- Controlled sources are resistive two-port elements consisting of two branches:
 - Primary branch: open circuit or short circuit
 - Secondary branch: voltage source or current source

Constant:

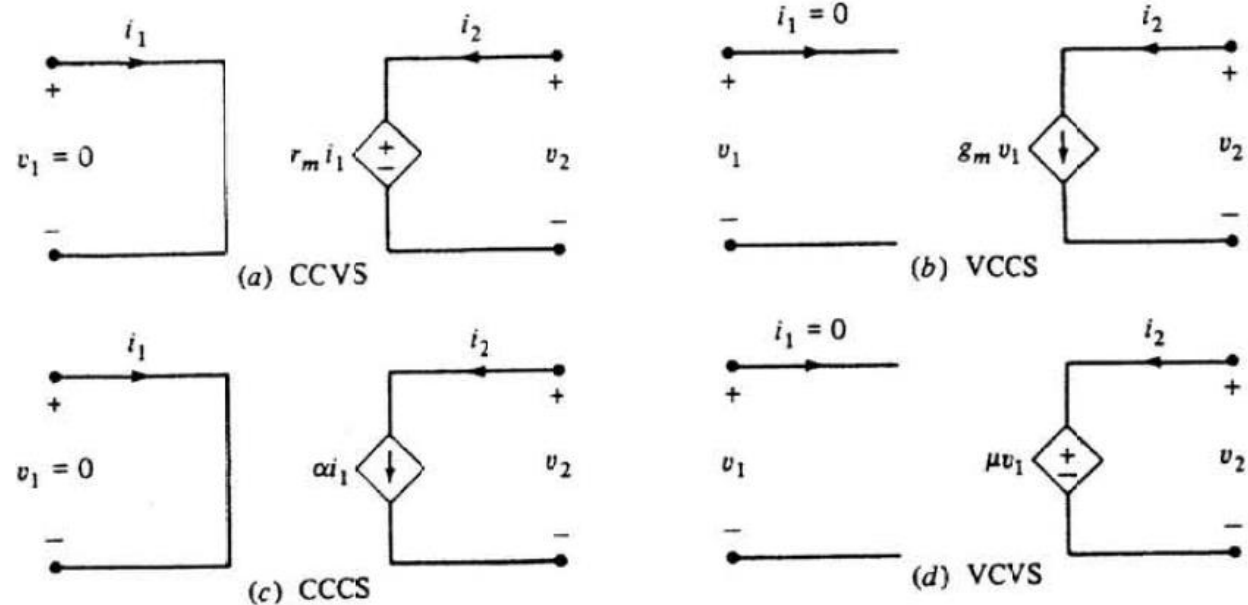- r_m : transresistance
- g_m : transconductance
- α : current transfer ratio
- μ : voltage transfer ratio



- Each linear controlled source is characterized by two linear equations



CCVS:

$$v_1 = 0$$

$$v_2 = r_m i_1$$

VCCS:

$$i_1 = 0$$

$$i_2 = g_m v_1$$

CCCS:

$$v_1 = 0$$

$$i_2 = \alpha i_1$$

VCVS:

$$i_1 = 0$$

$$v_2 = \mu v_1$$

Linear Controlled Sources

- Linear equation for four controlled sources can also be represented in matrix form as:


CCVS:	$v_1 = 0$	$v_2 = r_m i_1$	→	CCVS:	$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ r_m & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$
VCCS:	$i_1 = 0$	$i_2 = g_m v_1$		VCCS:	$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$
CCCS:	$v_1 = 0$	$i_2 = \alpha i_1$		CCCS:	$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ \alpha & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$
VCVS:	$i_1 = 0$	$v_2 = \mu v_1$		VCVS:	$\begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ \mu & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$

Linear Controlled Sources

- Ideal transformer: ideal two-port resistive circuit element characterizing by

$$v_1 = n v_2 \quad i_2 = -n i_1 \quad n: \text{real number called turn ratio}$$

Symbol of transformer

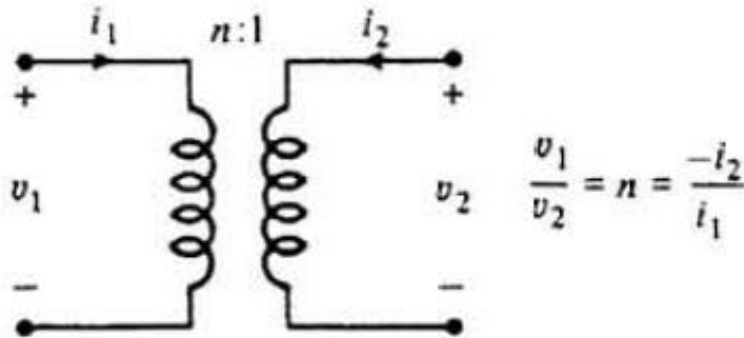

$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = H \begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & n \\ -n & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$

- Ideal transformer neither dissipate nor stores energy (non-energetic elements)

$$p = v_1 i_1 + v_2 i_2 = 0$$

Gyrator

- Gyrator: an ideal two-port element defined by the following equations:


$$i_1 = Gv_2 \quad i_2 = -Gv_1$$

Constant G is called the gyration conductance

- In vector form, the voltage controlled representation:

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & G \\ -G & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \quad i = \begin{bmatrix} 0 & G \\ -G & 0 \end{bmatrix} v$$

Symbol of gyrator

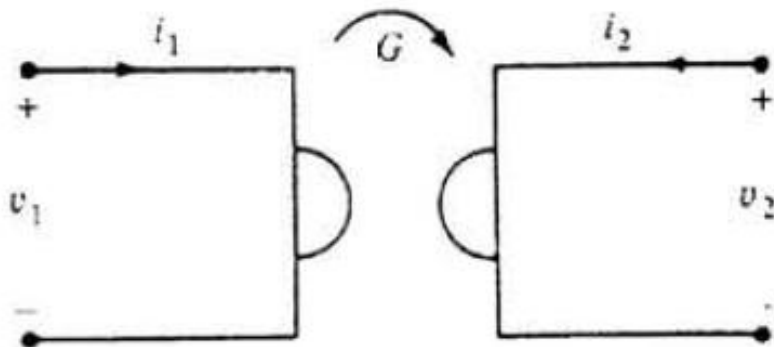

- Just like Ideal transformer, gyrator is non-energetic elements (power delivered to the two-port is zero).