



**Quiz #1**

1. The following questions are according to the memory map given on the side.
- a) Draw the chip select input of *BIOS*, *Main Memory*, and *Graphics Card* separately using the NAND circuit.
- b) Fill the following table according to the address input in which the chip selection area will be enabled or disabled.

| Address Input | $\overline{CS}_{BIOS}$ | $\overline{CS}_{Memory}$ | $\overline{CS}_{Graphics}$ |
|---------------|------------------------|--------------------------|----------------------------|
| 0x23FF        | 1                      | 1                        | 1                          |
| 0xE4B7        | 1                      | 1                        | 0                          |
| 0xC800        | 1                      | 1                        | 1                          |
| 0x6B20        | 0                      | 1                        | 1                          |

|        |                          |
|--------|--------------------------|
| 0x0000 |                          |
| 0x4000 | <b>BIOS</b>              |
| 0x7FFF |                          |
| 0xA400 | <b>Main<br/>Memory</b>   |
| 0xA3FF |                          |
| 0xE000 | <b>Graphics<br/>Card</b> |
| 0xFFFF |                          |


2. Build a memory that spans between \$3000 and \$6FFF with 4Kx8 memory chips for a CPU with 8-bit data bus and 16-bit address bus.
- a) Calculate the memory address range for all chips.
- b) How many 4K chips are needed?
- c) Draw the memory design by showing all necessary connections. (Address bus, Data bus, Chip select signals). Use an address decoder (determine its type) and logic gates (determine their types). Assume the decoder select signal and the memory chip select signals are active high.

Duration: 40 minutes

①

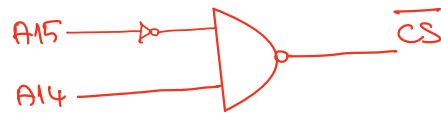
a) BIOS

$0x4000 \Rightarrow 0100000000000000$   
 $0x7FFF \Rightarrow 0111111111111111$




MAIN MEMORY

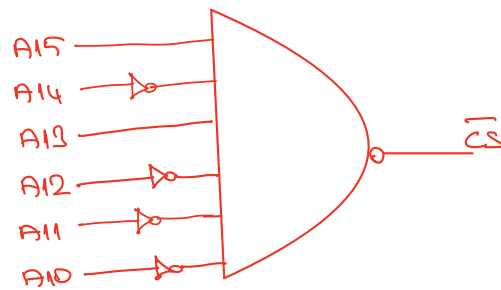$0xA000 \Rightarrow 1010000000000000$   
 $0xA3FF \Rightarrow 1010001111111111$



GRAPHICS CARD

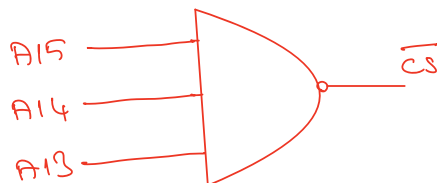$0xE000 \Rightarrow 1110000000000000$   
 $0xFFFF \Rightarrow 1111111111111111$



②

a)

|        |   |      |      |      |      |
|--------|---|------|------|------|------|
| \$3000 | ⇒ | 0011 | 0000 | 0000 | 0000 |
| \$3FFF |   | 0011 | 1111 | 1111 | 1111 |
| <hr/>  |   |      |      |      |      |
| \$4000 | ⇒ | 0100 | 0000 | 0000 | 0000 |
| \$4FFF |   | 0100 | 1111 | 1111 | 1111 |
| <hr/>  |   |      |      |      |      |
| \$5000 | ⇒ | 0101 | 0000 | 0000 | 0000 |
| \$5FFF |   | 0101 | 1111 | 1111 | 1111 |
| <hr/>  |   |      |      |      |      |
| \$6000 | ⇒ | 0110 | 0000 | 0000 | 0000 |
| \$6FFF |   | 0110 | 1111 | 1111 | 1111 |

b) 4

c)

