

Experiment 4.1

An inverting amplifier circuit shown in Figure-1. Apply a sinusoidal signal for V_{in} with 100 mV amplitude and 1 kHz frequency. You are free to choose your resistor values but you have to obtain a gain larger than 10.

- Observe your V_{in} and V_{out} and copy them onto your protocol paper.
- Explain the circuit.
- What is the maximum input voltage amplitude for your amplifier without any clipping at the output?

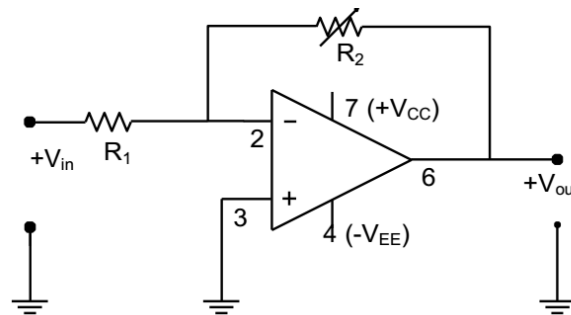


Figure 1: Inverting Amplifier

Experiment 4.2

Repeat the exact same things (for the same input amplitude, frequency etc.) for the non-inverting amplifier which given in Figure-2. Explain the difference between the amplifiers in Figure-1 and Figure-2.

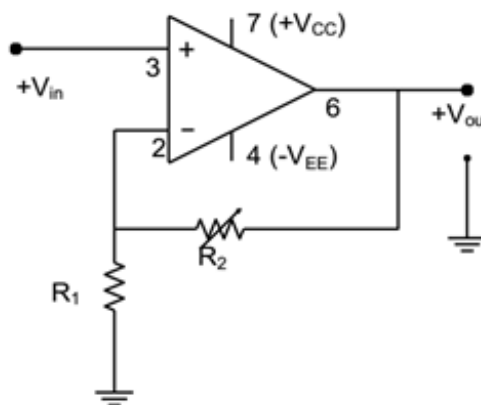


Figure 2: Non-Inverting Amplifier

Experiment 4.3

For the summing amplifier circuit in Figure-3, implement the function $V_{out} = -(aV_1 + bV_2)$. You are free to choose a and b (using appropriate resistor ratios, you can easily set a and b). V_1 and V_2 are the sinusoidal signals and have the amplitudes 100 mV and 200 mV, respectively. Set the both frequency to 1 kHz.

- Observe V_{in1} , V_{in2} and V_{out} with the oscilloscope and copy them onto your protocol paper.
- Explain the circuit.

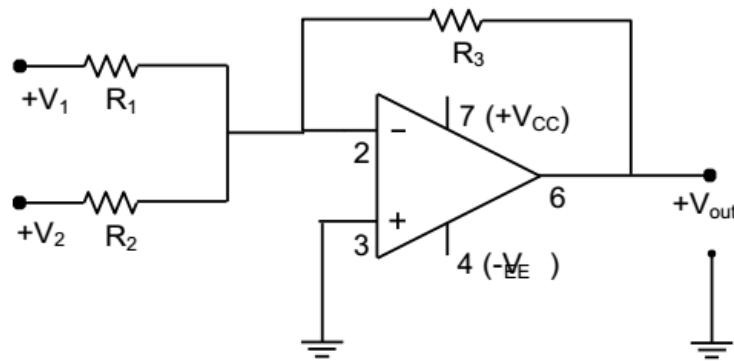


Figure 3: Summing Amplifier

Experiment 4.4

For the difference amplifier circuit in Figure-4, implement the function $V_{out} = (aV_2 - bV_1)$. You are free to choose a and b (using appropriate resistor ratios, you can easily set a and b). V_1 and V_2 are the sinusoidal signals and have the amplitudes 100 mV and 200 mV, respectively. Set the both frequency to 1 kHz.

- Observe V_{in1} , V_{in2} and V_{out} with the oscilloscope and copy them onto your protocol paper.
- Explain the circuit.

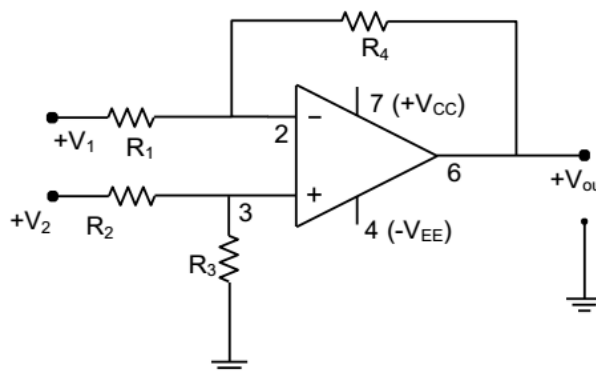


Figure 4: Difference Amplifier

Experiment 4.5

For the integrator circuit in Figure 5, $C = 10 \text{ nF}$, $R_1 = R_{eq} = 10\text{k}$, $R_2 = 100\text{k}$ values are given.

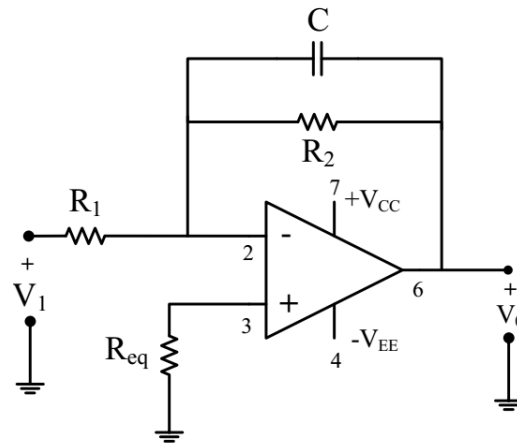


Figure 5: Integrator

Apply square pulse with 500 mV amplitude and 1 kHz frequency for integrator circuit. Observe and note V_i and V_o . Discuss if the circuit operates as an integrator.